

THOMAS FLOYD

1. A silicon diode is in series with 1.0 k Ω resistor and a 5 V battery. If the anode is connected to the positive battery terminal, the cathode voltage with respect to the negative battery terminal is
 - A. 0.7 V
 - B. 5.7 V
 - C. 0.3 V
 - D. **4.3 V**
2. The average value of a half-wave rectified voltage with a peak value of 200 V is
 - A. 127.3 V
 - B. 141 V
 - C. 0 V
 - D. **63.7 V**
3. The peak value of the input to a half-wave rectifier is 10 V. The approximate peak value of the output is
 - A. 10.7 V
 - B. **9.3 V**
 - C. 10 V
 - D. 3.18 V
4. For the circuit in Question in Question 3, the diode must be able to withstand a reverse voltage of
 - A. 5 V
 - B. **10 V**
 - C. 20 V
 - D. 3.18 V
5. The average value of a full-wave rectified voltage with a peak value of 75 V is
 - A. 37.5 V
 - B. 23.9 V
 - C. 53 V
 - D. **47.8 V**
6. When the peak output voltage is 100 V, the PIV for each diode in a center-tapped full-wave rectifier is (neglecting the diode drop)
 - A. 100 V
 - B. 141 V
 - C. **200 V**
 - D. 50 V
7. When the rms output voltage of a bridge full wave rectifier is 20 V, the peak inverse voltage across the diodes is (neglecting the diode drop)
 - A. **28.3 V**
 - B. 20 V
 - C. 40 V
 - D. 56.6 V
8. A certain power supply filter produces an output with a ripple of 100 mV peak-to-peak and a dc value of 20 V. The ripple factor is
 - A. **0.005**
 - B. 0.05
 - C. 0.02
 - D. 0.00005
9. A 60 V peak full-wave rectified voltage is applied to a capacitor-input filter. If $f = 120$ Hz, $R_L = 10$ k Ω and $C = 10$ μ F, the ripple voltage is
 - A. 0.6 V
 - B. **5.0 V**
 - C. 6 mV
 - D. 2.88 V
10. If the input voltage to a voltage tripler has an rms value of 12 V, the dc output voltage is approximately
 - A. 36 V
 - B. 33.9 V
 - C. 32.4 V
 - D. **50.9 V**
11. For a certain 12 V zener diode, a 10 mA change in zener current produces a 0.1 V change in zener voltage. The zener impedance for this current ranges is
 - A. 0.1 Ω
 - B. 100 Ω
 - C. **10 Ω**
 - D. 1 Ω
12. The data sheet for a particular zener gives $V_Z = 10$ V at $I_{ZT} = 500$ mA. Z_Z for these conditions is
 - A. **20 Ω**
 - B. 50 Ω
 - C. 10 Ω
 - D. unknown
13. If the output of a transistor amplifier is 5 V rms and the input is 100 mV rms, the voltage gain is
 - A. **50**
 - B. 500
 - C. 5
 - D. 100
14. In a certain voltage-divider biased npn transistor, V_B is 2.95 V. The dc emitter voltage is approximately
 - A. 2.95 V
 - B. **2.25 V**
 - C. 0.7 V
 - D. 3.65 V
15. In an emitter bias circuit, $R_E = 2.7$ k Ω and $V_{EE} = 15$ V. The emitter current
 - A. is 180 mA
 - B. is 2.7 mA
 - C. **is 5.3 mA**

D. cannot be determined

16. If the dc emitter current in a certain transistor amplifier is 3 mA, the approximate value of r'_e is

- A. 3 Ω
- B. 3 k Ω
- C. 0.33 k Ω
- D. **8.33 Ω**

17. For a common-collector amplifier, $R_E = 100 \Omega$, $r'_e = 10 \Omega$, and $\beta_{AC} = 150$. The ac input resistance at the base is

- A. **16.5 Ω**
- B. 15 k Ω
- C. 110 Ω
- D. 1500 Ω

18. If a 10 mV signal is applied to the base of the emitter-follower circuit in Question 5, the output signal is approximately

- A. 1.5 mV
- B. **10 mV**
- C. 100 mV
- D. 150 mV

19. For a common-emitter amplifier, $R_C = 1.0 \text{ k}\Omega$, $R_E = 390 \Omega$, and $\beta_{ac} = 75$. Assuming the R_E is completely bypassed at the operating frequency, the voltage gain is

- A. 2.56
- B. **66.7**
- C. 2.47
- D. 75

20. In the circuit of Question 7, if the frequency is reduced to the point where $X_{C(\text{bypass})} = R_E$, the voltage gain

- A. remains the same
- B. **is less**
- C. is greater

21. In a darlington pair configuration, each transistor has an ac beta of 125. If R_E is 560 Ω , the input resistance is

- A. 560 Ω
- B. 70 Ω
- C. 140 k Ω
- D. **8.75 M Ω**

22. In a common-emitter amplifier with voltage-divider bias, $R_{in(\text{base})} = 68 \text{ k}\Omega$, $R_1 = 33 \text{ k}\Omega$, and $R_2 = 15 \text{ k}\Omega$. The total input resistance is

- A. 22.2 k Ω
- B. 68 k Ω
- C. **8.95 k Ω**
- D. 12.3 k Ω

23. A CE amplifier is driving a 10 k Ω load. If $R_C = 2.2 \text{ k}\Omega$ and $r'_e = 10 \Omega$, the voltage gain is approximately

- A. **180**
- B. 220
- C. 10
- D. 1000

24. The overall gain found in Question 14 can be expressed in decibels as

- A. 47.0 dB
- B. 35.6 dB
- C. **94.1 dB**
- D. 69.8 dB

25. In a certain FET circuit, $V_{GS} = 0 \text{ V}$, $V_{DD} = 15 \text{ V}$, $I_{DSS} = 15 \text{ mA}$, and $R_D = 470 \Omega$. If R_D is decreased to 330 Ω , I_{DSS} is

- A. 1 mA
- B. 10.5 mA
- C. 19.5 mA
- D. **15 mA**

26. For a certain JFET, $I_{GSS} = 10 \text{ nA}$ at $V_{GS} = 10 \text{ V}$. The input resistance is

- A. 1 M Ω
- B. **1000 M Ω**
- C. 100 M Ω
- D. 1000 m Ω

27. For a certain p-channel JFET, $V_{GS(\text{off})} = 8 \text{ V}$. The value of V_{GS} for an approximately midpoint bias is

- A. **2.34 V**
- B. 0 V
- C. 4 V
- D. 1.25 V

28. In a certain common-source (CS) amplifier, $V_{DS} = 3.2 \text{ V rms}$ and $V_{GS} = 280 \text{ mV rms}$. The voltage gain is

- A. 1
- B. **11.4**
- C. 8.75
- D. 3.2

29. In a certain CS amplifier, $R_D = 1.0 \text{ k}\Omega$, $R_S = 560 \Omega$, $V_{DD} = 10 \text{ V}$, and $g_m = 4500 \mu\text{S}$. If the source resistor is completely bypassed, the voltage gain is

- A. 450
- B. 45
- C. **4.5**
- D. 2.52

30. A CS amplifier has a load resistance of 10 k Ω and $R_D = 820 \Omega$. If $g_m = 5 \text{ mS}$ and $V_{in} = 500 \text{ mV}$, the output signal voltage is

- A. **1.89 V**
- B. 2.05 V
- C. 25 V
- D. 0.5 V

31. If the load resistance in Question 7 is removed, the output voltage will

- A. stay the same
- B. decrease
- C. **increase**
- D. be zero

32. A certain common-drain (CD) amplifier with $R_S = 1.0 \text{ k}\Omega$ has a transconductance of $6000 \text{ }\mu\text{S}$. The voltage gain is

- A. 1
- B. **0.86**
- C. 0.98
- D. 6

33. The data sheet for the transistor used in a CD amplifier specifies $I_{GSS} = 5 \text{ nA}$ at $V_{GS} = 10 \text{ V}$. If the resistor from gate to ground, R_G , is $50 \text{ M}\Omega$, the total input resistance is approximately.

- A. $50 \text{ M}\Omega$
- B. $200 \text{ M}\Omega$
- C. $40 \text{ M}\Omega$
- D. $20.5 \text{ M}\Omega$

34. Two FET amplifier are cascaded. The first stage has a voltage gain of 5 and the second stage has a voltage gain of 7. The overall voltage gain is

- A. **35**
- B. 12

C. dependent on the second stage loading

35. A certain class A power amplifier delivers 5 W to a load with an input signal power of 100 mW . The power gain is

- A. 100
- B. **50**
- C. 250
- D. 5

36. A certain class A power amplifier has $V_{CEQ} = 12 \text{ V}$ and $I_{CQ} = 1 \text{ A}$. The maximum signal power output is

- A. 6 W
- B. 12 W
- C. 1 W
- D. 0.707 W

37. The output of a certain two-supply class B push pull amplifier has a V_{CC} of 20 V . If the load resistance is $50 \text{ }\Omega$, the value of $I_{C(sat)}$ is

- A. 5 mA
- B. **0.4 A**
- C. 4 mA
- D. 40 mA

38. The gain of a certain amplifier decrease by 6 dB when the frequency is reduced from 1 kHz to 10 Hz . The roll-off is

- A. -3 dB/decade
- B. -6 dB/decade
- C. -3 dB/octave
- D. **-6 dB/octave**

39. The gain of a particular amplifier at a given frequency decreases by 6 dB when the frequency is doubled. The roll-off is

- A. -12 dB/decade
- B. -20 dB/decade
- C. -6 dB/octave
- D. **answer b and c**

40. An amplifier has the following critical frequencies: 1.2 kHz , 950 Hz , 8 kHz , and 8.5 kHz . The bandwidth is

- A. 7550 Hz
- B. 7300 Hz
- C. **6800 Hz**
- D. 7050 Hz

41. If the f_r of the transistor used in a certain amplifier is 75 MHz and the bandwidth is 10 MHz , the voltage gain must be

- A. 750
- B. **7.5**
- C. 10
- D. 1

42. In the midrange of an amplifier's bandwidth, the peak output voltage is 6 V . At the lower critical frequency, the peak output voltage is

- A. 3 V
- B. 3.82 V
- C. 8.48 V
- D. **4.24 V**

43. At the upper critical frequency, the peak output voltage of a certain amplifier is 10 V . The peak voltage in the midrange of the amplifier is

- A. 7.07 V
- B. 6.37 V
- C. **14.14 V**
- D. 10 V

44. If $A_{v(d)} = 3500$ and $A_{cm} = 0.35$, the CMRR is

- A. 1225
- B. 10,000
- C. 80 dB
- D. **answers b and c**

45. A certain op-amp has a bias current of $50 \text{ }\mu\text{A}$ and $49.3 \text{ }\mu\text{A}$. The input offset current is

- A. 700 nA

- B. **99.3 μ A**
 C. 49.7 μ A
 D. none of these
- D. **0.02**

46. The output of a particular op-amp increases 8 V in 12 μ s. The slew rate is

- A. 96 V/ μ s
 B. 0.67 V/ μ s
 C. **1.5 V/ μ s**
 D. none of the above

47. A certain inverting amplifier has an R_i of 0.1 k Ω and an R_f of 100 k Ω . The closed loop gain is

- A. 100,000
 B. 1000
 C. **101**
 D. 100

48. If the feedback resistor in Question 17 is open, the voltage gain is

- A. **increases**
 B. decreases
 C. is not affected
 D. depends on R_i

49. A certain inverting amplifier has a closed-loop gain of 25. The op-amp has an open-loop gain of 100,000. If another op-amp with an open loop gain of 200,000 is substituted in the configuration, the closed-loop gain

- A. doubles
 B. drops to 12.5
 C. **remains at 25**
 D. increases slightly

50. If a certain op-amp has a midrange open-loop gain of 200,000 and a unity gain frequency of 5 MHz, the gain-bandwidth product is

- A. 200,000 Hz
 B. 1×10^{12} Hz
 C. **5,000,000 Hz**
 D. not determinable from the information

51. If a certain op-amp has a closed-loop gain of 20 and an upper critical frequency of 10 MHz, the gain-bandwidth product is

- A. 200 MHz
 B. 10 MHz
 C. the unity-gain frequency
 D. **answer a and c**

52. In a certain oscillator, $A_v = 50$. The attenuation of the feedback circuit must be

- A. 1
 B. 0.01
 C. 10