



# IES MASTER

Institute for Engineers (IES/GATE/PSUs)

**GATE  
2017**

**Detailed  
Solution**

**ELECTRONICS &  
COMMUNICATION ENGINEERING  
SESSION - 1**

**Office Address:** F-126, Katwaria Sarai, New Delhi - 110 016  
**Telephone:** 011-41013406, **Mobile:** 8130909220, 9711853908

**Web:** [www.iesmaster.org](http://www.iesmaster.org)

**E-mail:** [info@iesmaster.org](mailto:info@iesmaster.org)

# GATE—2017

## Electronics & Communication Engineering

### Questions and Detailed Solution

### Session-1

1. Three fair cubical dice are thrown simultaneously. The probability that all three dice have the same number on the faces showing up is (up to third decimal place)

**Sol. (0.0278)**

The total no. of outcomes,  $n(s) = 6 \times 6 \times 6 = 216$

The favourable outcomes,  $n(E)$  are (1, 1, 1), (2, 2, 2), ..... (6, 6, 6)

So,  $n(E) = 6$

$$\begin{aligned} \therefore \text{required probability} &= \frac{n(E)}{n(s)} = \frac{6}{216} \\ &= 0.0278 \end{aligned}$$

2. Consider the following statements about the linear dependence of the real valued functions  $y_1 = 1$ ,  $y_2 = x$  and  $y_3 = x^2$ , over the field of real numbers.

- I.  $y_1, y_2$  and  $y_3$  are linearly independent on  $-1 \leq x \leq 0$
- II.  $y_1, y_2$  and  $y_3$  are linearly dependent on  $0 \leq x \leq 1$
- III.  $y_1, y_2$  and  $y_3$  are linearly dependent on  $0 \leq x \leq 1$
- IV.  $y_1, y_2$  and  $y_3$  are linearly independent on  $-1 \leq x \leq 1$

Which one among the following is correct?

- (a) Both I and II are true
- (b) Both I and III are true
- (c) Both II and IV are true
- (d) Both III and IV are true

**Sol. (a)**

$$y_1 = 1, y_2 = x, y_3 = x^2$$

Linear combination is given by

$$ay_1 + by_2 + cy_3 = 0, \quad a, b, c \in \mathbb{R}$$

$$\Rightarrow a + bx + cx^2 = 0, \quad a, b, c \in \mathbb{R}$$

**Case : 1**

If  $x \in [0, 1]$

$$a + bx + cx^2 = 0$$

$$\text{At } x = 0 \Rightarrow a = 0 \quad \dots(1)$$

$$\text{At } x = \frac{1}{2}; \frac{b}{2} + \frac{c}{4} = 0 \quad \dots(2)$$

$$\text{At } x = 1, \quad b + c = 0$$

From equation (1) and (2), we get

$$b = c = 0$$

$$\therefore a = b = c = 0$$

$\Rightarrow y_1, y_2$  and  $y_3$  are linearly independent for  $0 \leq x \leq 1$ .

**Case II :**

If  $x \in [-1, 0]$

$$a + bx + cx^2 = 0$$

$$\text{At } x = 0 \Rightarrow a = 0$$

$$\text{At } x = -1 \Rightarrow -b + c = 0 \quad \dots(4)$$

$$\text{At } x = -\frac{1}{2} \Rightarrow -\frac{b}{2} + \frac{c}{4} = 0 \quad \dots(5)$$

From equation (4) and (5), we get

$$b = c = 0$$

$$\therefore a = b = c = 0$$

$\Rightarrow y_1, y_2$  and  $y_3$  are linearly independent for  $-1 \leq x \leq 0$ .

3. Consider a wireless communication link between a transmitter and a receiver located in free space with finite and strictly positive capacity. If the effective areas of the transmitter and the receiver antenna and the distance between them are all doubled and everything else remains unchanged, the maximum capacity of the wireless link

- (a) increases by a factor of 2
- (b) decrease by a factor of 2
- (c) remains unchanged
- (d) decreases by a factor of  $\sqrt{2}$

Sol. (c)

As per Friis free space propagation equation

$$P_r = \frac{P_t \cdot A_{er} \cdot A_{et}}{(\lambda R)^2}$$

where,

$P_r$  = Received power

$P_t$  = Transmitted power

$A_{er}$  = Aperture area of receiver

$A_{et}$  = Aperture area of transmitter

$\lambda$  = Wave length

$R$  = Distance between receiver and transmitter

Now, if  $A_{er}$ ,  $A_{et}$  and  $R$  are doubled, then

$$P'_r = \frac{P_t (2A_{er}) (2A_{et})}{(\lambda 2R)^2}$$

$$P'_r = \frac{P_t A_{er} A_{et}}{(\lambda R)^2}$$

$$P'_r = P_r$$

Hence, maximum capacity of the wireless link will be the same.

4. A periodic signal  $x(t)$  has a trigonometric Fourier series expansion

$$x(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

If  $x(t) = -x(-t) = -x(t - \pi/\omega_0)$ . We can conclude that

- (a)  $a_n$  are zero for all  $n$  and  $b_n$  are zero for  $n$  even
- (b)  $a_n$  are zero for all  $n$  and  $b_n$  are zero for  $n$  odd
- (c)  $a_n$  are zero for  $n$  even and  $b_n$  are zero for  $n$  odd
- (d)  $a_n$  are zero for  $n$  odd and  $b_n$  are zero for  $n$  even

Sol. (a)

Given,  $x(t) = -x(-t) = -x(t - \frac{\pi}{\omega_0})$

The given signal has

1. odd function symmetry

$$a_n = 0$$

2. Half-wave symmetry

$$a_n = 0 \text{ and contains only}$$

odd harmonics

$\therefore a_n$  are zero for all  $n$  and  $b_n$  are zero for  $n$  even.

5. A bar of Gallium Arsenide (GaAs) is doped with Silicon such that the Silicon atoms occupy Gallium and Arsenic sites in the GaAs crystal. Which one of the following statement is true?

- (a) Silicon atoms act as p-type dopants in Arsenic sites and n-type dopants in Gallium sites.
- (b) Silicon atoms act as n-type dopants in Arsenic sites and p-type dopants in Gallium sites.
- (c) Silicon atoms act as p-type dopants in Arsenic as well as Gallium sites.
- (d) Silicon atoms act as n-type dopants in Arsenic as well as Gallium sites.

Sol. (a)

When GaAs is doped with Silicon, the two possibilities arise

- (i) Silicon can replace Gallium
- (ii) Silicon can replace Arsenic

So, if the Silicon replaces Gallium then Silicon has one more electron. So, the extra electron is available for conduction. It will make it n-type.

On the other hand, Silicon replaces Arsenic it has one less electron and it will make it p-type.

6. The miller effect in the context of a common Emitter amplifier explains :
- (a) an increase in the low-frequency cutoff frequency
  - (b) an increase in the high-frequency cutoff frequency
  - (c) a decrease in the low-frequency cutoff frequency
  - (d) a decrease in the high-frequency cutoff frequency

**Sol. (d)**

A common emitter amplifier has a capacitance between the collector and the base, and the gain of CE amplifier is negative, so the Miller effect will occur which reduce the high-frequency response of the amplifier.

7. An  $n^+ - n$  Silicon device is fabricated with uniform and non-degenerate donor doping concentrations of  $N_{D1} = 1 \times 10^{18} \text{ cm}^{-3}$  and  $N_{D2} = 1 \times 10^{15} \text{ cm}^{-3}$  corresponding to the  $n^+$  and  $n$  regions respectively. At the operational temperature  $T$ , assume complete impurity ionization  $kT/q = 25\text{mV}$  and intrinsic carrier concentration to be  $n_i = 1 \times 10^{10} \text{ cm}^{-3}$ . What is the magnitude of the built-in potential of this device ?
- (a) 0.748 V
  - (b) 0.460 V
  - (c) 0.288 V
  - (d) 0.173 V

**Sol. (a)**

The junction built-in voltage

$$V_0 = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right)$$

$$= 25 \times 10^{-3} \ln \left[ \frac{10^{18} \times 10^{15}}{(1 \times 10^{10})^2} \right]$$

$$= 25 \times 10^{-3} \times 29.9336 \text{ V}$$

$$= 0.748 \text{ Volts.}$$

8. Consider a stable system with transfer function

$$G(s) = \frac{s^p + b_1 s^{p-1} + \dots + b_p}{s^q + a_1 s^{q-1} + \dots + a_q}$$


where  $b_1, \dots, b_p$  and  $a_1, \dots, a_q$  are real valued constants. The slope of the Bode log magnitude curve of  $G(s)$  converges to  $-60 \text{ dB/decade}$  as  $\omega \rightarrow \infty$ . A possible pair of values for  $p$  and  $q$  is:

- (a)  $p = 0$  and  $q = 3$
- (b)  $p = 1$  and  $q = 7$
- (c)  $p = 2$  and  $q = 3$
- (d)  $p = 3$  and  $q = 5$

**Sol. (a)**


Final slope =  $-60 \text{ dB/decade}$ , which indicates that  $p - q = 3$ . option (a) satisfies this condition.

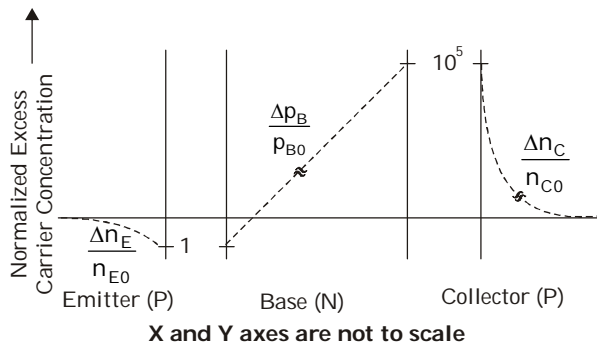9. For a narrow base PNP BJT, the excess minority carrier concentrations ( $\Delta n_E$  for emitter,  $\Delta p_B$  for base,  $\Delta n_C$  for collector) normalized to equilibrium minority carrier concentrations ( $n_{E0}$  for emitter,  $p_{B0}$  for base,  $n_{C0}$  for collector) in the quasi-neutral emitter, base and collector regions are shown below. Which one of the following biasing modes is the transistor operating in?



- (a) Forward active
- (b) Saturation
- (c) Inverse active
- (d) Cutoff

**Sol. (c)**

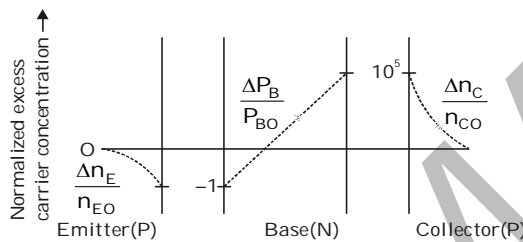

where,

$\Delta n_E, \Delta P_B, \Delta n_C$  are excess minority carrier concentration of emitter, base and collector region respectively.

$n_{EO}, P_{BO}, n_{CO}$  are thermally generated minority carrier of emitter, base and collector region.

At collector – Base region ratio of excess minority carrier concentration to equilibrium minority carrier concentration is in order of  $10^5$ (very high). This is possible when the junction is forward bias (injection).

At emitter – Base region, ratio of excess minority carrier concentration to equilibrium minority carrier concentration is in order of 1 (negligible). This is possible, when junction is reverse bias (no injection).

Hence, collector-base junction is forward biased and emitter base junction is reverse biased. So it in inverse active mode.

10. Consider the following statements for continuous-time linear time invariant (LTI) system :

- I. There is no bounded input bounded output (BIBO) stable system with a pole in the right half of the complex plane.
- II. There is no casual and BIBO stable system with a pole in the right half of the complex plane.

Which one among the following is correct ?

- (a) Both I and II are true
- (b) Both I and II are not true
- (c) Only I is true
- (d) Only II is true

**Sol. (d)**

For stable system, ROC of pole must contain  $j\omega$ -axis. It is not compulsory that right sided signal is stable. So statement (i) is wrong.

There is non-causal system, its pole start from left side of s-plane and for BIBO stable system, its pole must contain  $j\omega$ -axis and it go right side. So statement (ii) is correct.

11. The clock frequency of an 8085 microprocessor is 5 MHz. If the time required to execute an instruction is  $1.4 \mu s$ , then the number of T-states needed for executing the instruction is

- (a) 1
- (b) 6
- (c) 7
- (d) 8

**Sol. (c)**


The number of T-states needed for executing the instruction = (Execution time of instruction) × (Clock frequency)

$$= 1.4 \times 10^{-6} \times 5 \times 10^6$$


$$= 7$$

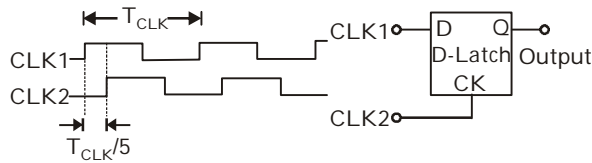12. Consider the D-Latch shown in the figure which is transparent when its clock input CK is high and has zero propagation delay.

In the figure, the clock signal CLK1 has a 50% duty cycle and CLK2 is a one-fifth period delayed version of CLK1. The duty cycle at the output of the latch in percentage is



Sol. (30)

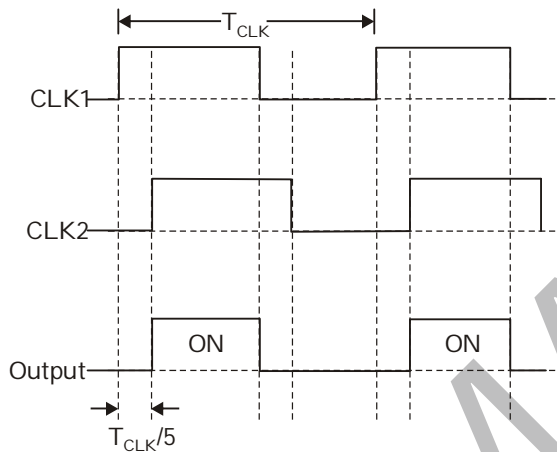

The output will be high only when both CLK1 and CLK2 are high:

$$\begin{aligned} \text{So, Duty cycle} &= \frac{\text{ON time}}{\text{Time Period}} \\ &= \frac{\left(\frac{T_{\text{CLK}}}{2} - \frac{T_{\text{CLK}}}{5}\right)}{T_{\text{CLK}}} \\ &= \frac{5-2}{10} \\ &= 0.3 \text{ i.e., } 30\% \end{aligned}$$

13. Which one of the following statements about differential pulse code modulation (DPCM) is true?

- (a) The sum of message signal with its prediction is quantized
- (b) The message signal sample is directly quantized and its prediction is not used
- (c) The difference of message signal sample and a random signal is quantized

(d) The difference of message signal with its prediction is quantized.

Sol. (d)

Differential Pulse Code Modulation (DPCM) is a procedure of converting an analog into a digital signal in which an analog signal is sampled and then the difference between the actual sample value and its predicted value (predicted value is based on previous sample or samples) is quantized and then encoded forming a digital value.

14. The rank of the matrix  $M = \begin{bmatrix} 5 & 10 & 10 \\ 1 & 0 & 2 \\ 3 & 6 & 6 \end{bmatrix}$  is

- (a) 0
- (b) 1
- (c) 2
- (d) 3

Sol. (c)

$$M = \begin{bmatrix} 5 & 10 & 10 \\ 1 & 0 & 2 \\ 3 & 6 & 6 \end{bmatrix}$$

$$\det \{M\} = 5(0-12) - 1(60-60) + 3(20-0) = -60 - 0 + 60 = 0$$


The one of the minor of matrix M has non zero determinant value. e.g.

$$M_{11} = \begin{bmatrix} 0 & 2 \\ 6 & 6 \end{bmatrix} \text{ and } |M_{11}| = -12$$

Hence rank of M is 2.

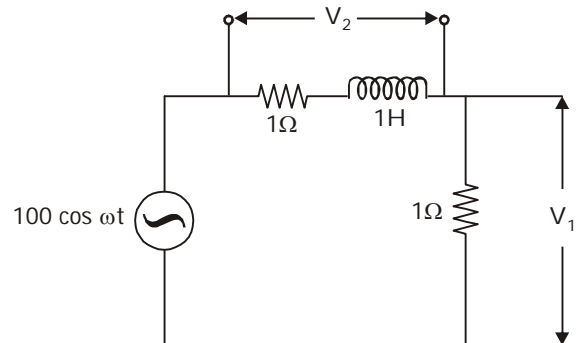15. In the circuit shown the positive angular frequency  $\omega$  (in radians per second) at which the magnitude of the phase difference

between the voltage  $V_1$  and  $V_2$  equals  $\frac{\pi}{4}$  radians is \_\_\_\_\_





**IES MASTER**.org  
Institute for Engineers (IES/GATE/PSUs)

## ANNOUNCES NEW BATCHES FOR **IES/GATE/PSUs**


### BRANCHES ▶




**CIVIL ENGG**



**MECHANICAL  
ENGG**

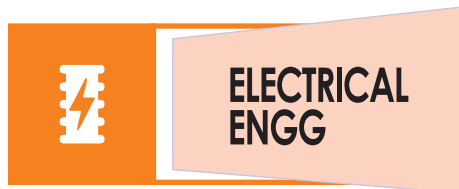

**ELECTRICAL  
ENGG**

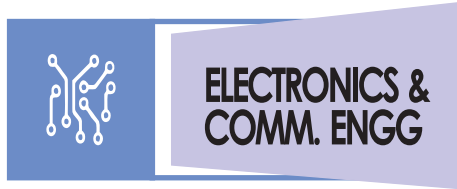

**ELECTRONICS &  
COMM. ENGG**

**Regular Morning  
Batches Start**

**2<sup>nd</sup> Mar'17**

For  
Civil Engineering

**Weekend  
Batches Start**

**25<sup>th</sup> Feb'17**

For  
Civil Engineering

**Weekend  
Batches Start**

**18<sup>th</sup> Feb'17**

For  
ME, EE, ECE

**Regular Evening  
Batches Start**

**15<sup>th</sup> Feb'17**

**ADMISSION  
OPEN FOR**


**SESSION  
2017-18**

**F-126, Katwaria Sarai, New Delhi - 16**

**8010009955, 9711853908**

Sol. (1)

The given circuit can be redrawn as

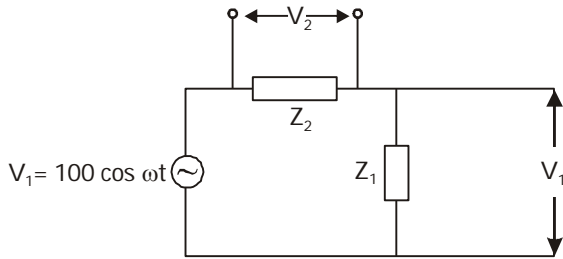

Where,  $Z_1 = 1 \Omega$  and  $Z_2 = 1 + j\omega 1$

and  $V_1 = \frac{Z_1}{Z_1 + Z_2} V_i$  and  $V_2 = \frac{Z_2}{Z_1 + Z_2} V_i$

Or  $V_1 = \frac{1}{1 + 1 + j\omega} V_i$  and

$$V_2 = \frac{1 + j\omega}{1 + 1 + j\omega} V_i$$

The magnitude of phase difference between  $V_1$  and  $V_2$

$$\left| -\tan^{-1} \frac{\omega}{2} - \left( \tan^{-1} \omega - \tan^{-1} \frac{\omega}{2} \right) \right| = \frac{\pi}{2}$$

Or  $\tan^{-1} = \frac{\pi}{4}$

Or  $\omega = 1 \text{ rad/sec.}$

16. The voltage of an electromagnetic wave propagating in a coaxial cable with uniform characteristic impedance is

$V(l) = e^{-\gamma l + j\omega t}$  volts, where  $l$  is the distance along the length of the cable in metres.

$\gamma = (0.1 + j40) \text{ m}^{-1}$  is the complex propagation constant and  $\omega = 2\pi \times 10^9 \text{ rad/s}$  is the angular frequency. The absolute value of the attenuation in dB/metre is \_\_\_\_\_

Sol. (0.8686)

Given,  $\gamma = (0.1 + j40) \text{ m}^{-1}$

The propagation constant,  $\gamma = \alpha + j\beta$

Where,  $\alpha =$  attenuation constant

$\beta =$  phase constant

$$\begin{aligned} \therefore \alpha &= 0.1 \text{ Np/m} \\ &= 8.686 \times 0.1 \text{ dB/m} \\ &= 0.8686 \text{ dB/m} \end{aligned}$$

17. A good transconductance amplifier should have

- (a) high input resistance and low output resistance
- (b) low input resistance and high output resistance
- (c) high input and output resistances
- (d) low input and output resistances

Sol. (c)

For a transconductance amplifier

Input resistance,  $R'_i = \frac{R_i}{1 + \beta A}$

and output resistance,

$$R'_o = \frac{R_o}{1 + \beta A}$$


$\therefore$  for an ideal or good transconductance amplifier (where  $\beta A \approx -1$ )

$R'_i \rightarrow \infty$  and  $R'_o \rightarrow \infty$

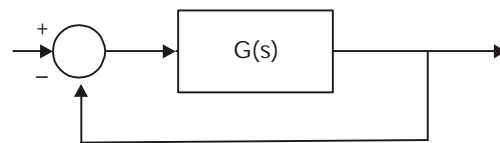18. The open loop transfer function

$$G(s) = \frac{(s+1)}{s^p(s+2)(s+3)}$$

where  $p$  is an integer is connected in unity feedback configuration as shown in the figure



Given that the steady state error is zero for unit step input and is 6 for unit ramp input. The value of the parameter  $p$  is \_\_\_\_\_

Sol. (1)

Steady state error,



$$e_{ss} = \lim_{s \rightarrow 0} s.R(s) \frac{1}{1+G(s)H(s)}$$

For unit ramp input

$$6 = \lim_{s \rightarrow 0} s \cdot \frac{1}{s^2} \cdot \frac{1}{1 + \frac{(s+1)}{s^p(s+2)(s+3)}}$$





Or 
$$6 = \lim_{s \rightarrow 0} \frac{1}{s + \frac{(s+1)}{s^{p-1}(s+2)(s+3)}}$$

Or 
$$6 = \lim_{s \rightarrow 0} \frac{1}{0 + \frac{1}{6s^{p-1}}}$$

$\therefore p = 1$

No need to verify for unit step input.

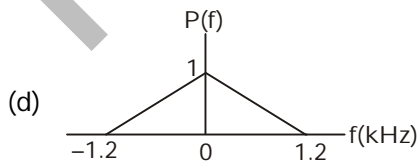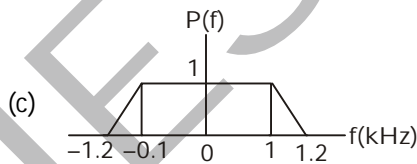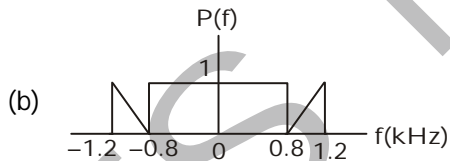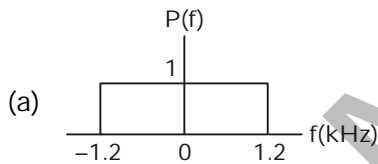19. In a digital communication system, the overall pulse shape  $p(t)$  at the receiver before the sampler has the fourier transform  $P(f)$ . If the symbols are transmitted at the rate of 2000 symbols per second, for which of the following cases is the inter symbol interference zero ?



Sol.19 (b)

Condition for zero inter symbol interference



$$\frac{1}{T_s} \sum_{k=-\infty}^{\infty} P\left(f - \frac{k}{T_s}\right) = 1 \quad \forall f$$

$P(f)$  is fourier transform of  $P(t)$


$$f_s = 2000 \text{ symbols/sec.}$$

$$= 2k \text{ symbols/sec.}$$

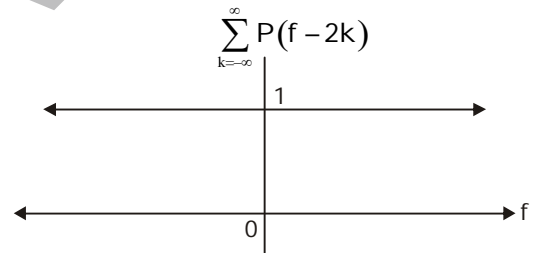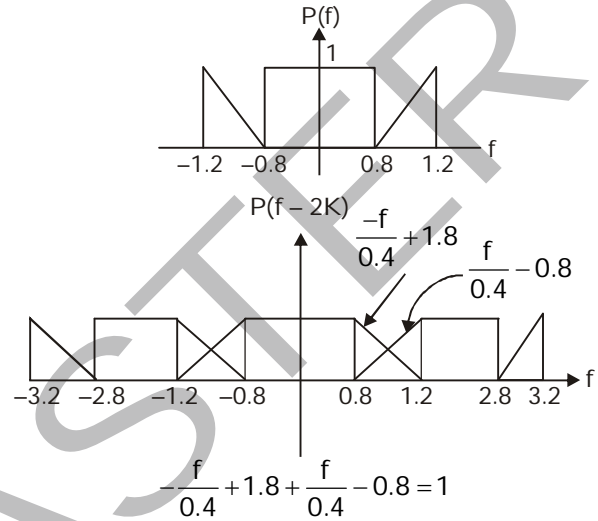The above condition is satisfied by only option (b).



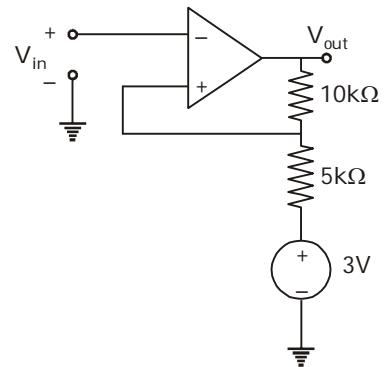20. For the operational amplifier circuit shown, the output saturation voltages are  $\pm 15 \text{ V}$ . The upper and lower threshold voltages for the circuit are respectively.



(a)  $+5 \text{ V}$  and  $-5 \text{ V}$

(b)  $+7 \text{ V}$  and  $-3 \text{ V}$

- (c) -3 V and + 7V
- (d) +3 V and - 3V

**Sol. (b)**

For the given circuit, the upper and lower threshold voltage are given by

$$UTP = \frac{R_2}{R_1 + R_2} \cdot V_{sat} + \frac{R_1}{R_1 + R_2} V_r$$

and 
$$LTP = -\frac{R_2}{R_1 + R_2} V_{sat} + \frac{R_1}{R_1 + R_2} V_r$$

Here,  $R_1 = 10k\Omega$ ,  $R_2 = 5k\Omega$ ,  $V_r = 3V$  and  $V_{sat} = 15V$

$$\therefore UTP = \frac{5}{5+10} \times 15 + \frac{10}{5+10} \times 3 = 5 + 2 = 7V$$

and 
$$LTP = -\frac{5}{5+10} \times 15 + \frac{10}{5+10} \times 3 = -5 + 2 = -3V$$

21. Consider the  $5 \times 5$  matrix

$$A = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 \\ 5 & 1 & 2 & 3 & 4 \\ 4 & 5 & 1 & 2 & 3 \\ 3 & 4 & 5 & 1 & 2 \\ 2 & 3 & 4 & 5 & 1 \end{bmatrix}$$

It is given that A has only one real eigenvalue. Then the real eigenvalue of A is

- (a) -25
- (b) 0
- (c) 15
- (d) 25

**Sol. (c)**


Characteristic equation is  $|A - \lambda I| = 0$

$$\begin{bmatrix} 1-\lambda & 2 & 3 & 4 & 5 \\ 5 & 1-\lambda & 2 & 3 & 4 \\ 4 & 5 & 1-\lambda & 2 & 3 \\ 3 & 4 & 5 & 1-\lambda & 2 \\ 2 & 3 & 4 & 5 & 1-\lambda \end{bmatrix}$$

For real eigen value, sum of either one row or column must be zero.


$$\Rightarrow 1 - \lambda + 2 + 3 + 4 + 5 = 0, \therefore \lambda = 15$$

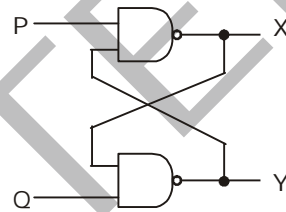22. In the latch circuit shown, the NAND gates have non-zero but unequal propagation delays. The present input condition is  $P = Q = '0'$ . if the input condition is changed simultaneously to  $P = Q = '1'$  the outputs X and Y are



- (a)  $X = 1, Y = 1$
- (b) either  $X = 1, Y = '0'$  or  $X = '0', Y = 1$
- (c) either  $X = 1, Y = '1'$  or  $X = '0', Y = '0'$
- (d)  $X = '0', Y = '0'$

**Sol. (b)**

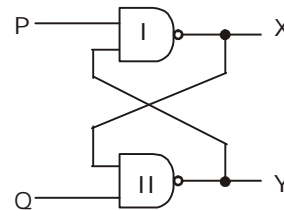

NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Given,

Present input  $P = Q = 0$

then,  $X = Y = 1$

Now,  $P = Q = 1,$

then output X and Y will change as  $X = 0, Y = 1$  or,  $X = 1, Y = 0$  as per the propagation

delay of NAND Gate.

If  $P = Q = 1$ , then  $X = 0, Y = 1$  if propagation delay of NAND Gate-I is less than NAND Gate-II, because both the input of NAND Gate-I are 1.

If  $P = Q = 1$ , then  $X = 1, Y = 0$  if propagation delay of NAND Gate-II is less than NAND Gate-I because both the input of NAND Gate-II are 1.

So, option (b)

23. Consider a single input single output discrete-time system with  $x[n]$  as input and  $y[n]$  as output, where the two are related as

$$y(n) = \begin{cases} n|x[n]|, & \text{for } 0 \leq n \leq 10 \\ x[n] - x[n-1], & \text{Otherwise} \end{cases}$$

which one of the following statements is true about the system.



- (a) It is causal and stable
- (b) It is causal but not stable
- (c) It is not causal but stable
- (d) It is neither causal not stable

Sol. (a)

$$y[n] = \begin{cases} n|x[n]| & \text{for } 0 \leq n \leq 10 \\ x[n] - x[n-1] & \text{otherwise} \end{cases}$$

- Present output depends on present input and past input, so it is a causal system.
- For a bounded input, bounded output yields, so it is a stable system.

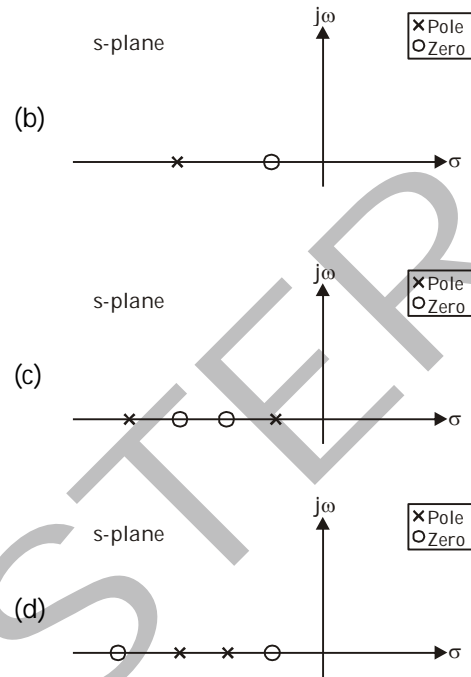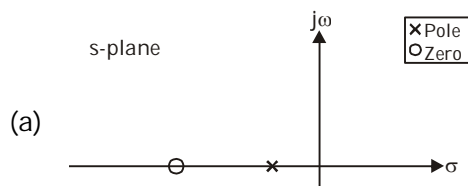24. Which of the following can be the pole-zero configuration of a phase-lag controller (lag compensation)?




Sol. (a)

For phase-lag controller, the transfer function is

$$G(s) = \frac{1+sT}{1+s\beta T}$$

Where,  $\beta > 1$

∴ The pole-zero configuration will be

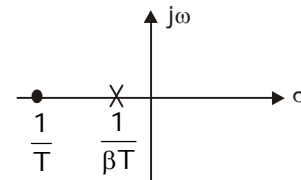

25. Let  $(X_1, X_2)$  be independent random variables,  $X_1$  has mean 0 and variance 1, while  $X_2$  has mean 1 and variance 4. The mutual information  $I(X_1; X_2)$  between  $X_1$  and  $X_2$  in bits is.....

Sol. (0)

Mutual information of two discrete random variable  $X_1$  and  $X_2$  can be defined as:

$$I(X_1, X_2)$$

**Announcing  
New  
Batches**



**IES MASTER**  
Institute for Engineers (IES/GATE/PSUs)

for

**IES | GATE | PSUs**

Branches



**Weekend  
Batches Start**

**18<sup>th</sup>**  
**February 2017**  
Timings  
**8:30 am to 5:30 pm**

**Regular  
Batches Start**

**15<sup>th</sup>**  
**February 2017**  
Timings  
**6:00 pm to 9:30 pm**

### *Special Offers*

**25%  
OFF**

Early Bird discount for  
first 50 students

**40%  
OFF**

Group discount for  
three or more students

**FREE  
DEMO  
CLASSES**

Attend two free classes  
and experience our  
commitment to the  
classroom programs

**Add:** F-126, Katwaria Sarai, New Delhi - 110016  
**Cont:** 011-41013406, 8010009955, 9711853908  
[www.facebook.com/iesmaster01](http://www.facebook.com/iesmaster01)

[www.iesmaster.org](http://www.iesmaster.org)

$$= \sum_{x_2 \in X_2} \sum_{x_1 \in X_1} P(x_1, x_2) \log \left[ \frac{P(x_1, x_2)}{P(x_1) P(x_2)} \right]$$

If  $X_1$  and  $X_2$  are independent then  $P(x_1, x_2) = P(x_1)P(x_2)$

$$\log \left[ \frac{P(x_1, x_2)}{P(x_1)P(x_2)} \right] = \log \left[ \frac{P(x_1) P(x_2)}{P(x_1) P(x_2)} \right]$$

$$= \log 1 = 0$$

$$I(X_1, X_2) = 0$$

26. In binary frequency shift keying (FSK), the given signal wavefonus are

$$u_0(t) = 5 \cos(20000\pi t); 0 \leq t \leq T, \text{ and}$$

$$u_1(t) = 5 \cos(22000\pi t); 0 \leq t \leq T,$$

where  $T$  is the bit-duration interval and  $t$  is in seconds. Both  $u_0(t)$  and  $u_1(t)$  are zero outside the interval  $0 \leq t \leq T$ . With a matched filter (correlator) based receiver, the smallest positive value of  $T$  (in milli seconds) required to have  $u_0(t)$  and  $u_1(t)$  uncorrelated is

- (a) 0.25 ms                      (b) 0.5 ms  
(c) 0.75 ms                      (d) 1.0 ms

Sol. (b)

$$u_0(t) = 5 \cos(20000\pi t); 0 \leq t \leq T$$

$$u_1(t) = 5 \cos(22000\pi t); 0 \leq t \leq T$$

$$f_1 = 11000 \text{ Hz}$$

$$f_2 = 10000 \text{ Hz}$$

For FSK wave form to be uncorrelated.

$$f_1 - f_2 = \frac{nR_b}{2}; n = 1, 2, 3, \dots$$

$$R_b = \frac{2(f_1 - f_2)}{n}$$

$$= \frac{2000}{n} \text{ bit/sec.}$$

$$R_{b(\text{max.})} = 2000 \text{ bit/sec.}$$

$\therefore$  minimum value of  $n = 1$ ,

$$T_{b(\text{min.})} = \frac{1}{R_{b(\text{max.})}} = 0.5 \text{ ms}$$

27. Two discrete-time signals  $x[n]$  and  $h[n]$  are both non-zero only for  $n = 0, 1, 2$  and are zero otherwise. It is given that

$$x[0] = 1, x[1] = 2, x[2] = 1, h[0] = 1$$

Let  $y[n]$  be the linear convolution of  $x[n]$  and  $h[n]$ . Given that  $y[1] = 3$  and  $y[2] = 4$ , the value of the expression  $(10y[3] + y[4])$  is.....

Sol. (31)

Given,

$$x[n] = [1, 2, 1]$$

$$\text{and } h[n] = [1, a, b]$$

We know that,

$$y[n] = x[n] * h[n]$$

$$= \begin{array}{c|ccc} & 1 & 2 & 1 \\ \hline 1 & 1 & 2 & 1 \\ a & a & 2a & a \\ b & b & 2b & b \end{array}$$

$$y[n] = [1, (2+a), (2a+b+1), (a+2b), b]$$

Given,

$$y[1] = 3 = 2 + a$$

$$\text{Or } a = 1$$

$$y[2] = 4 = 2a + b + 1$$

$$\text{Or } b = 1$$


$$y[3] = a + 2b = 1 + 2 = 3$$

$$y[4] = b = 1$$

$$\therefore (10y[3] + y[4]) = 10 \times 3 + 1 = 31$$

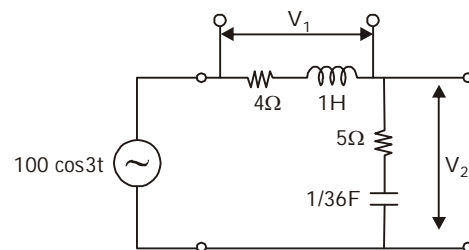
28. The figure shows an RLC circuit excited by the sumoidal voltage  $100 \cos(3t)$  Volts, where  $t$  is in seconds. The ratio

$\frac{\text{amplitude of } v_2}{\text{amplitude of } v_1}$  is .....



Sol. (0.3846)

The given circuit can be redrawn as

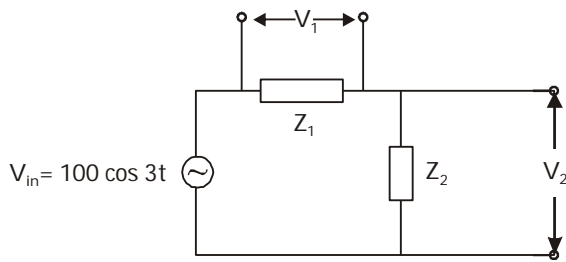

Where,  $Z_1 = 4 + j\omega 1$

and  $Z_2 = 5 + \frac{36}{j\omega}$

Given,  $\omega = 3 \text{ rad/sec.}$

$\therefore Z_1 = 4 + j3$

and  $Z_2 = 5 + \frac{36}{j3} = 5 - j12$

From voltage division rule

$$V_1 = \frac{Z_1}{Z_1 + Z_2} V_{in}$$


and  $V_2 = \frac{Z_2}{Z_1 + Z_2} V_{in}$

$$\therefore \frac{|V_1|}{|V_2|} = \frac{|Z_1|}{|Z_2|} = \frac{\sqrt{16+9}}{\sqrt{25+144}} = \frac{5}{13} = 0.3846$$

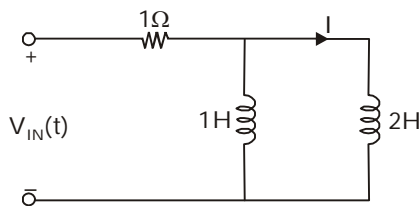29. In the circuit shown the voltage  $V_{IN}(t)$  is described by

$$V_{IN}(t) = \begin{cases} 0, & \text{for } t \leq 0 \\ 15 \text{Volts,} & \text{for } t \geq 0 \end{cases}$$

Where  $t$  is in seconds. The time (in seconds) at which the current  $I$  in the circuit will reach the value 2 Amperes is .....



Sol. (0.0954)

Equivalent inductance,  $L_{eq} = \frac{2 \times 1}{2+1} = \frac{2}{3} \text{H}$

and equivalent resistance,  $R_{eq} = 1 \Omega$

$\therefore$  Time constant,  $\tau = \frac{L}{R} = \frac{2}{3} \text{sec.}$

and current at time,  $t$ ,

$$i(t) = \frac{V_{in}}{R} [1 - e^{-t/\tau}]$$

$$= \frac{15}{1} [1 - e^{-3t/2}]$$

$$= 15 (1 - e^{-1.5t})$$

$$i(t_0) = 2 = 15 (1 - e^{-1.5t_0})$$

Or  $e^{-1.5t_0} = 0.8667$

$\therefore t_0 = 0.0954 \text{ sec.}$

30. As shown, two Silicon (Si) abrupt p-n junction diodes are fabricated with uniform donor doping concentrations of  $N_{D1} = 10^{14} \text{ cm}^{-3}$  and  $N_{D2} = 10^{16} \text{ cm}^{-3}$  in the n-regions of the diodes, and uniform acceptor doping concentration of  $N_{A1} = 10^{14} \text{ cm}^{-3}$  and  $N_{A2} = 10^{16} \text{ cm}^{-3}$  in the p-regions of the diodes, respectively. Assuming that the reverse bias voltage is in built-in potentials of the diodes, the ratio  $C_2/C_1$  of their reverse bias capacitances for the same applied reverse bias is .....

p	n	p	n
$10^{14} \text{ cm}^{-3}$	$10^{14} \text{ cm}^{-3}$	$10^{16} \text{ cm}^{-3}$	$10^{16} \text{ cm}^{-3}$
$C_1$ Diode 1		$C_2$ Diode 2	

Sol. (10)

Given that:

Donor doping concentration,

$$N_{D1} = 10^{14} \text{ cm}^{-3}$$

$$N_{D2} = 10^{16} \text{ cm}^{-3}$$

Acceptor doping concentration,

$$N_{A1} = 10^{14} \text{ cm}^{-3}$$

$$N_{A2} = 10^{16} \text{ cm}^{-3}$$

Since,  $V_0 \ll V_R$   
 $\Rightarrow V_0 + V_R = V_R$

$$C = \frac{\epsilon A}{W}$$

$$\frac{C_2}{C_1} = \frac{\frac{\epsilon A}{W_2}}{\frac{\epsilon A}{W_1}} = \frac{W_1}{W_2}$$

$$= \sqrt{\frac{2 \epsilon V_R}{q} \left[ \frac{1}{N_{A1}} + \frac{1}{N_{D1}} \right]}$$

$$= \sqrt{\frac{2 \epsilon V_R}{q} \left[ \frac{1}{N_{A2}} + \frac{1}{N_{D2}} \right]}$$

$$= \sqrt{\frac{N_{D1} + N_{A1}}{N_{A1} \cdot N_{D1}}}$$

$$= \sqrt{\frac{N_{D2} + N_{A2}}{N_{D2} \cdot N_{A2}}}$$

$$= \sqrt{\frac{10^{14} + 10^{14}}{10^{14} \cdot 10^{14}}}$$

$$= \sqrt{\frac{10^{16} + 10^{16}}{10^{16} \cdot 10^{16}}}$$

$$= \sqrt{\frac{2 \times 10^{14}}{10^{28}}}$$

$$= \sqrt{\frac{2(10^{16})}{10^{32}}}$$

$$= \sqrt{\frac{2 \times 10^{14}}{10^{28}} \times \frac{10^{32}}{2(10^{16})}}$$

$$= \sqrt{\frac{10^{46}}{10^{44}}}$$

$$= \sqrt{10^2} = 10$$

31. Let  $x(t)$  be a continuous time periodic signal with fundamental period  $T = 1$  seconds. Let  $\{a_k\}$  be the complex Fourier series

coefficients of  $x(t)$ . Where  $k$  is integer valued. Consider the following statements about  $x(3t)$ .

- I. The complex Fourier series coefficients of  $x(3t)$  are  $\{a_k\}$  where  $k$  is integer valued
  - II. The complex Fourier series coefficients of  $x(3t)$  are  $\{3a_k\}$  where  $k$  is integer valued
  - III. The fundamental angular frequency of  $x(3t)$  is  $6\pi$  rad/s
- For the three statements above, which one of the following is correct?
- (a) Only II and III are true
  - (b) Only I and III are true
  - (c) Only III is true
  - (d) Only I is true

Sol. (b)

$x(t)$  be a continuous time periodic signal, Fundamental time period ( $T$ ) = 1

So,  $\omega_0 = 2\pi$  rad/sec.


We know,  $x(at) \rightarrow a_k, a\omega_0$

So, when  $x(t)$  is compressed by 3, frequency will expand by 3.

$$x(3t) \rightarrow a_k, 3\omega_0 = 6\pi$$

So, both statement I and II are correct.


32. For the DC analysis of the Common-Emitter amplifier shown, neglect the base current and assume that the emitter and collector currents are equal. Given that  $V_T = 25\text{mV}$ ,  $V_{BE} = 0.7\text{V}$ , and the BJT output resistance  $r_o$  is practically infinite. Under these conditions the midband voltage gain magnitude  $A_v = |v_o/v_1|$  V/V, is.....

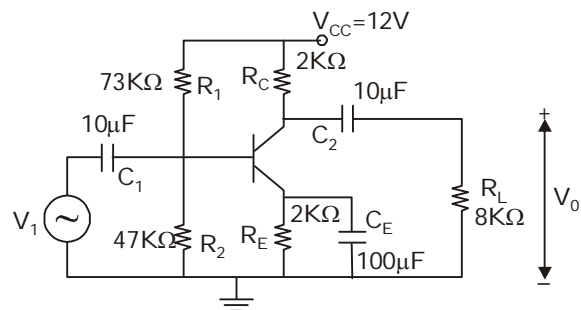

Sol. (128)

DC analysis: all capacitor are open circuit.

Now, Redrawing circuit,

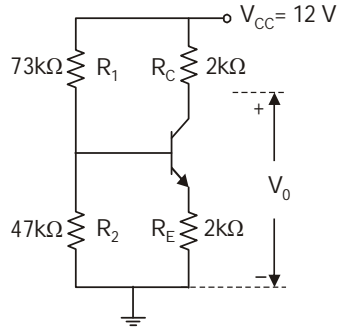

$$V_{th} = \frac{12 \times 47}{73 + 47} = 4.7V$$

$$R_{th} = \frac{73 \times 47}{47 + 73} = 28.59k\Omega$$

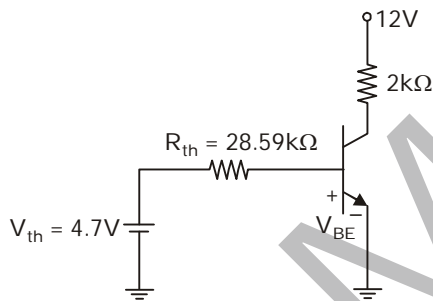


Fig.: DC Analysis

$$I_B = 0 \text{ (Given)}$$

then

$$I_C = I_E$$

Applying KVL in loop1

$$4.7 - 28.59K \cdot I_B - 0.7 - 2K \cdot I_E = 0$$

$$\Rightarrow 4.7 - 0.7 - 2K \cdot I_E = 0$$

$$I_E = \frac{4.7 - 0.7}{2K}$$

$$= \frac{4}{2K} = 2 \text{ m Amp.}$$

∴

$$I_C = I_E = 2 \text{ m Amp.}$$

$$g_m = \frac{I_C}{V_T}$$

$$= \frac{2m}{25m} = 80 \text{ V}$$

Now from AC analysis,

$$\begin{aligned} A_V &= -g_m \cdot R'_L \\ &= -80(2 || 8) \\ &= -80 \left( \frac{2 \times 8}{2 + 8} \right) \\ &= \frac{-80 \times 16}{10} = -128 \\ |A_V| &= 128 \end{aligned}$$

33. A continuous time signal  $x(t) = 4 \cos(200\pi t) + 8 \cos(400\pi t)$ , where  $t$  is in seconds, is the input to a linear time invariant (LTI) filter with the impulse response

$$h(t) = \begin{cases} \frac{2 \sin(300\pi t)}{\pi t} & t \neq 0 \\ 600, & t = 0 \end{cases}$$

Let  $y(t)$  be the output of this filter. The maximum value of  $|y(t)|$  is .....

Sol. (8)


Given continuous time signal,

$$X(t) = 4 \cos(200\pi t) + 8 \cos(400\pi t)$$

Impulse response,  $h(t) =$

$$\begin{cases} \frac{2 \sin(300\pi t)}{\pi t} & ; t \neq 0 \\ 600 & ; t = 0 \end{cases}$$

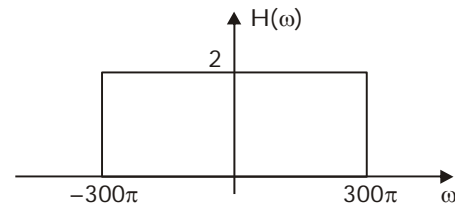So, its fourier transform  $\rightarrow H(\omega)$



Given input signal frequencies are 100, 200Hz.

So, the o/p signal

$$\begin{aligned} y(t) &= 2 \times 4 \cos(200\pi t) \\ &= 8 \cos(200\pi t) \end{aligned}$$

So, maximum value  $|y(t)| = 8$



# Conventional Question Practice Program for ESE - 2017 Mains Exam



**IES MASTER**  
Institute for Engineers (IES/GATE/PSUs)

**Cash Prize**  
for  
**Top 10**  
Students in Every  
Conventional  
Test

## Complete Package

Conventional Practice Test  
+  
Classroom Program

RANK	1 <sup>st</sup>	2 <sup>nd</sup>	3 <sup>rd</sup>	4 <sup>th</sup>	5 <sup>th</sup>	6-10 <sup>th</sup>
Prize	3000/-	2500/-	2000/-	1500/-	1000/-	500/-

Every  
Sunday

19<sup>th</sup> Feb  
to  
7<sup>th</sup> May

### Conventional Practice Test

- a) New Topics
- b) Revision Topics

11

Conventional  
Tests

2

Full length  
Tests

- ◆ Classroom Solutions + Discussion
- ◆ Improve Question Selection Ability
- ◆ Cover all Concepts in Various Topics
- ◆ Improve Time Management
- ◆ Under Simulated Classroom Exam Env.
- ◆ Unique Approach : Test on New Topics + Revision Topics

- ◆ Subject wise Practice, Discussion and Test
- ◆ Practice Booklets with Solution Outlines
- ◆ How to Write Answer- Test & Counselling Session
- ◆ Discussion and Practice Session of 250-300 hrs
- ◆ Under Guidance of Mr. Kanchan Kr. Thakur

### Classroom Program

250-300 hrs  
1:00 pm to 5:30 pm

Monday  
to  
Saturday

23<sup>rd</sup> Feb  
to  
6<sup>th</sup> May

10

Subject wise  
Tests

## Branches

Complete Course Conventional Test + Classroom Program  
only for CE and ME

Conventional Test Series  
CE, ME, EE, ECE

**Admissions Open**

For Query

For details about fees & class schedule visit <http://iesmaster.org>

8010009955, 9711853908

F-126, Katwaria Sarai, New Delhi - 110016

34. Which one of the following is the general solution of the first order differential equation

$$\frac{dy}{dx} = (x + y - 1)^2,$$

where x, y are real?

- (a)  $y = 1 + x + \tan^{-1}(x + c)$ , where c is a constant
- (b)  $y = 1 + x + \tan(x + c)$ , where c is a constant
- (c)  $y = 1 - x + \tan^{-1}(x + c)$ , where c is a constant
- (d)  $y = 1 - x + \tan(x + c)$ , where c is a constant

Sol. (c)

Given,

$$\frac{dy}{dx} = (x + y - 1)^2 \quad \dots (1)$$

Let,  $x + y - 1 = t$

$$\text{Then, } 1 + \frac{dy}{dx} - 0 = \frac{dt}{dx}$$

$$\text{Or } \frac{dy}{dx} = \frac{dt}{dx} - 1$$

From equation (1)

$$\frac{dt}{dx} - 1 = t^2$$

$$\text{Or } \frac{dt}{1 + t^2} = dx$$

$$\text{Or } \int \frac{dt}{1 + t^2} = \int dx$$


$$\text{Or } \tan^{-1} t = x + c$$

$$\text{Or } t = \tan(x + c)$$

$$\text{Or } x + y - 1 = \tan(x + c)$$

$$\text{Or } y = 1 - x + \tan(x + c)$$

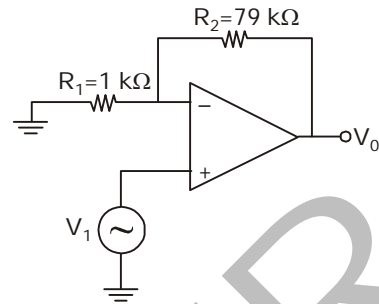35. The amplifier circuit shown in the figure is implemented using a compensated operational amplifier (Op-amp) and has an open-loop voltage gain  $A_0 = 10^5 \text{ V/V}$  and an open-loop cut-off frequency,  $f_c = 8 \text{ Hz}$ . The voltage gain of the amplifier at 15 kHz in V/V is.....



Sol. (44.4)

In the given circuit

Feed back factor,

$$\begin{aligned} \beta &= \frac{R_1}{R_1 + R_2} \\ &= \frac{1}{1 + 79} \\ &= \frac{1}{80} \end{aligned}$$

$$\text{Closeloop gain, } A_{of} = \frac{A_0}{1 + A_0\beta} \cong 80$$

$$\begin{aligned} f_c' &= f_c(1 + A_0\beta) \\ &= 8 \left( 1 + \frac{10^5}{80} \right) \text{ Hz} \\ &= 10,008 \text{ Hz.} \end{aligned}$$

Voltage gain at frequency


$f = 15 \text{ kHz}$  is

$$\begin{aligned} A_f &= \frac{A_{of}}{\sqrt{1 + \left(\frac{f}{f_c'}\right)^2}} \\ &= \frac{80}{\sqrt{1 + \left(\frac{15000}{10,008}\right)^2}} \\ &= 44.4 \end{aligned}$$

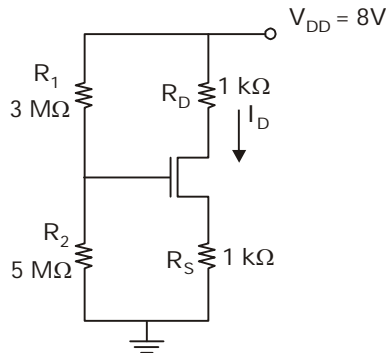36. For the circuit shown, assume that the NMOS transistor is in saturation. Its threshold voltage  $V_{in} = 1 \text{ V}$  and its transconductance parameter

$$\mu_n C_{ox} \left( \frac{W}{L} \right) = 1 \text{ mA/V}^2. \text{ Neglect channel}$$

length modulation and body bias effects. Under these conditions, the drain current  $I_D$  in mA is .....



**Sol. (2)**

Given,

Threshold voltage,  $V_{th} = 1V$

Transconductance parameter,

$$\mu_n C_{ox} \left( \frac{W}{L} \right) = 1 \text{ mA/V}^2$$


NMOS Transistor is in saturation,

$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) \cdot (V_{GS} - V_T)^2 \quad \dots(i)$$

From circuit,

$$V_G = V_{th} = \frac{8 \times 5}{3 + 5} = 5V$$
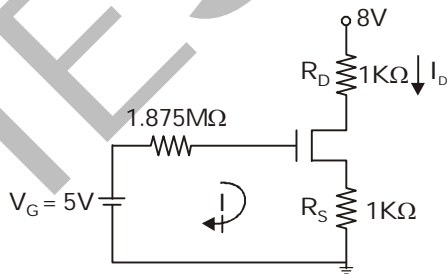
$$R_G = R_{th} = \frac{3 \times 5}{3 + 5} = 1.875M\Omega$$



Applying KVL in LOOP I.

$$\Rightarrow 5 - 1.875M \cdot I_G - V_{GS} - 1 \cdot I_D = 0 \quad [ \because I_G = 0 ]$$

$$\Rightarrow 5 - V_{GS} - 1 \cdot I_D = 0$$

$$I_D = 5 - V_{GS} \quad \dots(ii)$$

Put the value of (ii) in (i),

$$5 - V_{GS} = \frac{1}{2} (V_{GS} - 1)^2$$

$$\Rightarrow 10 - 2V_{GS} = V_{GS}^2 + 1 - 2V_{GS}$$

$$\Rightarrow V_{GS}^2 = 10 - 1$$

$$= 9$$

$$V_{GS} = 3V$$


So, from equation (ii),

$$I_D = 5 - V_{GS} = 5 - 3 = 2V$$

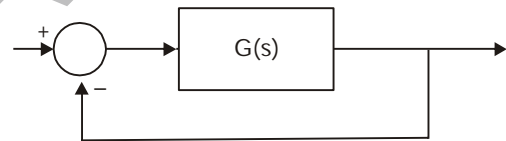**37.** A linear time invariant (LTI) system with the transfer function

$$G(s) = \frac{K(s^2 + 2s + 2)}{(s^2 - 3s + 2)}$$

is connected in unity feedback configuration as shown in the figure



For the closed loop system shown, the root locus for  $0 < K < \infty$  intersects the imaginary axis for  $K = 1.5$ . The closed loop system is stable for

- (a)  $K > 1.5$
- (b)  $1 < K < 1.5$
- (c)  $0 < K < 1$
- (d) no positive value of  $K$

**Sol. (a)**

The characteristic equation of given feedback system is

$$1 + \frac{k(s^2 + 2s + 2)}{(s^2 - 3s + 2)} = 0$$

$$\text{Or } s^2(k+1) + s(2k-3) + 2(k+1) = 0$$

The Routh Hurwitz table is

$$s^2 \quad k+1 \quad 2(k+1)$$

$$s^1 \quad 2k-3 \quad 0$$

$$s^0 \quad 2(k+1)$$

For system to be stable

$$k+1 > 0 \text{ and } 2k-3 > 0$$


Or  $k > -1$  and  $k > 1.5$

$\therefore k > 1.5$

38. Let  $X(t)$  be a wide sense stationary random process with the power spectral density  $S_x(f)$  as shown in Figure (a), where  $f$  is in Hertz (Hz). The random process  $X(t)$  is input to an ideal lowpass filter with the frequency response

$$H(f) = \begin{cases} 1 & |f| \leq \frac{1}{2} \text{ Hz} \\ 0 & |f| > \frac{1}{2} \text{ Hz} \end{cases}$$

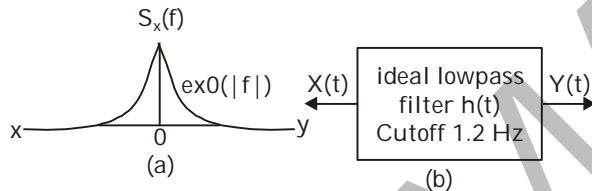as shown in Figure (b). The output of the lowpass filter is  $Y(t)$ .



Let  $E$  be the expectation operator and consider the following statements

I.  $E(X(t)) = E(Y(t))$

II.  $E(X^2(t)) = E(Y^2(t))$


III.  $E(Y^2(t)) = 2$

Select the correct option

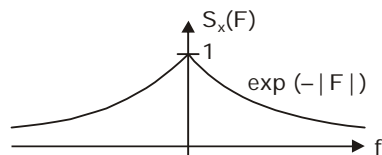
- (a) only I is true
- (b) only II and III are true
- (c) only I and II are true
- (d) only I and III are true

Sol. (a)

Given input power spectral density  $S_x(f)$



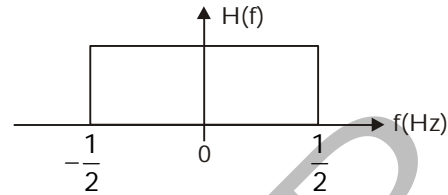Ideal low pass filter have frequency response.



(I)  $E[x(t)] = E[y(t)]$

$\therefore E[y(t)] = H(0) E[X(t)]$

and  $H(0) = 1$

so,  $E[y(t)] = E[x(t)]$

(II)  $E[x^2(t)] = E[y^2(t)]$

Since, Ideal LPF does not allow total power from input to output.

So,  $E[x^2(t)] \neq E[y^2(t)]$

(III)  $E[y^2(t)] = 2$

$$E[y^2(t)] = \int_0^{\infty} S_x(f) df$$

$$= 2$$


$\therefore$  from (II),

$$E[x^2(t)] \neq E[y^2(t)]$$

So,  $E[y^2(t)] \neq 2$

Hence, only statement-(I) is correct.

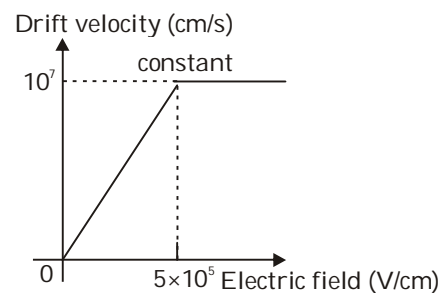39. The dependence of drift velocity of electrons on electric field in a semiconductor is shown below. The semiconductor has a uniform electron concentration of  $n = 1 \times 10^{16} \text{ cm}^{-3}$  and electronic charge  $q = 1.6 \times 10^{-19} \text{ C}$ . If a bias of 5 V is applied across a 1 mm region of this semiconductor, the resulting current density in this region in  $\text{kA/cm}^2$ , is .....



Sol. (1.6)

Electric field in the semiconductor

$$E = \frac{V}{t} = \frac{5}{1 \times 10^{-4}} = 5 \times 10^4 \text{ V/cm}$$

Now,

$$\text{Mobility} = \frac{\text{Drift velocity}}{\text{Electric field Intensity}}$$

$$= \frac{10^7 \text{ cm/s}}{5 \times 10^5 \text{ V/cm}}$$

$$\left[ \because E < 5 \times 10^5 \text{ V/cm} \right]$$

$$= 20 \text{ cm}^2/\text{V}\cdot\text{sec}$$

Conductivity,  $\sigma = ne\mu$

$$= 10^{16} \times 1.6 \times 10^{-19} \times 20$$

$$= 32 \times 10^{-3}$$

So, current density

$$J = \sigma E$$

$$= 32 \times 10^{-3} \times 5 \times 10^4 \text{ A/cm}^2$$

$$= 1600 \text{ A/cm}^2$$

$$= 1.6 \text{ kA/cm}^2$$

40. Let  $f(x) = e^{x+x^2}$  for real  $x$ . From among the following, choose the Taylor series approximation of  $f(x)$  around  $x = 0$ , which includes all powers of  $x$  less than or equal to 3.

(a)  $1 + x + x^2 + x^3$

(b)  $1 + x + \frac{3}{2}x^2 + x^3$

(c)  $1 + x + \frac{3}{2}x^2 + \frac{7}{6}x^3$

(d)  $1 + x + 3x^2 + 7x^3$

Sol. (c)

Given,  $f(x) = e^{x+x^2}$

$$f'(x) = e^{x+x^2} (1 + 2x)$$

$$f''(x) = (1 + 2x)^2 e^{x+x^2} + e^{x+x^2} \times 2$$

$$= e^{x+x^2} (3 + 4x^2 + 4x)$$

$$f'''(x) = (3 + 4x + 4x^2)(1 + 2x)$$

$$e^{x+x^2} + e^{x+x^2} (4 + 8x)$$

Now,  $f'(0) = 1, f''(0) = 3,$

$$f'''(0) = 3 + 4 = 7$$


Taylor series of  $f(x)$  around  $x = 0$  is

$$f(x) = f(0) + \frac{f'(0)}{1!}x + \frac{f''(0)}{2!}x^2$$

$$+ \frac{f'''(0)}{3!}x^3 + \dots$$


$$\therefore f(x) = 1 + x + \frac{3}{2}x^2 + \frac{7}{6}x^3$$

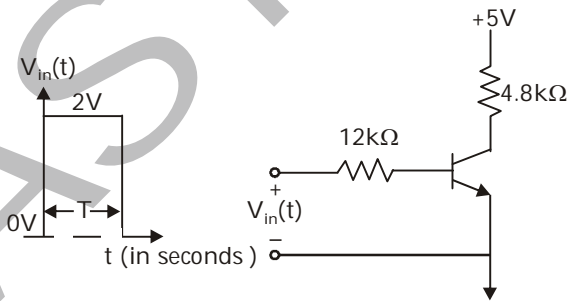41. In the figure shown the upon transistor acts as a switch



For the input  $V_m(t)$  as shown in the figure, the transistor switches between the cut-off and saturation regions of operation. When  $T$  is large, Assume collector-to-emitter voltage at saturation  $V_{CE(sat)} = 0.2\text{V}$  and base-to-emitter voltage  $V_{BE} = 0.7\text{V}$ . The minimum value of the common-base current gain ( $\alpha$ ) of the transistor for the switching should be

Sol. (0.902)

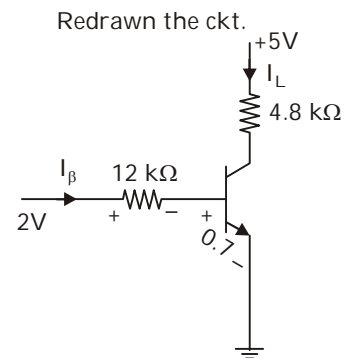



# IES MASTER

Institute for Engineers (IES/GATE/PSUs)

## ESE-2017 Conventional Test Schedule, Electronics Engineering

Date	Topic
5th Mar 2017	N.T. : BEE-1, MI-1, CS-1
	R.T. :
11th Mar 2017	N.T. : BEX-1, NT-1, EMT-1
	R.T. : BEE-1, CS-1, MI-1
19th Mar 2017	N.T. : BEE-2, NT-2, EMT-2, CO-1
	R.T. : BEX-1, EMT-1, NT-1
26th Mar 2017	N.T. : MI-2, NT-3, MAT-1, CS-2
	R.T. : BEE-2, NT-2, CS-1, EMT-2
2nd Apr 2017	N.T. : BEX-2, CS-3, CO-2
	R.T. : MI-2, CO-1, MAT-1, NT-2
9th Apr 2017	N.T. : ADC-1, EMT-3, COMM-1
	R.T. : CS-2, NT-1, EMT-1, BEX-1, EMT-2
16th Apr 2017	N.T. : ADC-2 BEX-3, ACT-1
	R.T. : BEE-2, MI-2, EMT-3, ADC-1, NT-2, CS-2, CS-3
23rd Apr 2017	N.T. : AET-1, MAT-2, ADC-3
	R.T. : ADC-2, BEX-2, BEE-1, MI-1, CS-2, ACT-1, NT-3, CO-2, COMM-1
30th Apr 2017	N.T. : AET-2, ACT-2, COMM-2
	R.T. : ADC-1, ADC-3, AET-1, CS-3, BEX-1, MAT-2, MAT-1
3rd May 2017	N.T. : COMM-3, MI-3, CO-3
	R.T. : ADC-3, AET-2, ACT-1, CO-1, CO-3, COMM-2, NT-3, MAT-2, ACT-2, MI-3
7th May 2017	N.T. : AET-3, ADC-4, MAT-3
	R.T. : CO-3, ACT-2, MAT-3, BEX-2, CS-2, EMT-3, BEX-3, AET-1 AET-2, COMM-2, ADC-4
9th May 2017	Full Length (Test Paper-1 + Test Paper-2)

### Test Type

### Timing

### Day

Conventional Test	10:00 A.M. to 1:00 P.M.	Sunday
Conventional Full Length Test Paper-1	10:00 A.M. to 1:00 P.M.	Tuesday
Conventional Full Length Test Paper-2	02:00 P.M. to 5:00 P.M.	Tuesday

Note : The timing of the test may change on certain dates. Prior information will be given in this regard.

\*N.T. : New Topic. \*R.T. : Revision Topic

Call us : 8010009955, 011-41013406 or Mail us : info@iesmaster.org

## Subject Code Details

<b>Basic Electronics Engineering (BEX)</b>	<b>BEX-1</b>	<b>BEX-2</b>	<b>BEX-3</b>	
	<ul style="list-style-type: none"> <li>◆ Basics of Semiconductors</li> <li>◆ Diode : Basics, Characteristics &amp; its types</li> <li>◆ BJT, JFET, MOSFET-Basic Structure &amp; Characteristics</li> </ul>	<ul style="list-style-type: none"> <li>◆ Transistor Amplifiers</li> <li>◆ Oscillators &amp; Other circuits</li> <li>◆ Basic of Linear ICs</li> <li>◆ Operational Amplifier &amp; their applications</li> </ul>	<ul style="list-style-type: none"> <li>◆ Basics of ICs; Bipolar, MOS &amp; CMOS ICs</li> <li>◆ Optical Sources / Detectors</li> <li>◆ Basics of Optoelectronics &amp; Applications</li> </ul>	
<b>Basic Electrical Engineering (BEE)</b>	<b>BEE-1</b>		<b>BEE-2</b>	
	<ul style="list-style-type: none"> <li>◆ Basics of Circuit Theory and Electromagnetic Field Theory</li> <li>◆ Single Phase AC circuits ◆ Transformer ◆ DC Machine</li> </ul>		<ul style="list-style-type: none"> <li>◆ Induction Machine ◆ Synchronous Machine</li> <li>◆ Electrical Power Sources, Basics of Batteries &amp; its uses</li> </ul>	
<b>Material Science (MAT)</b>	<b>MAT-1</b>	<b>MAT-2</b>		<b>MAT-3</b>
	<ul style="list-style-type: none"> <li>◆ Crystalline Structure</li> <li>◆ Dielectric properties of matter</li> <li>◆ Ceramic materials</li> </ul>	<ul style="list-style-type: none"> <li>◆ Magnetic properties of materials</li> <li>◆ Insulating laminates for electronics</li> <li>◆ Conductors &amp; Superconductors</li> </ul>		<ul style="list-style-type: none"> <li>◆ Semiconductor &amp; Optical materials</li> <li>◆ Nano materials Nano-optical / Magnetic / Electronic materials</li> </ul>
<b>Electronic Measurement and Instrumentation (MI)</b>	<b>MI-1</b>	<b>MI-2</b>		<b>MI-3</b>
	<ul style="list-style-type: none"> <li>◆ Error analysis &amp; basics of measurement</li> <li>◆ Basic measuring instruments</li> <li>◆ Measurement of Energy &amp; Power</li> </ul>	<ul style="list-style-type: none"> <li>◆ Measurement of Resistance</li> <li>◆ AC Bridges ◆ Potentiometer</li> <li>◆ Cathode Ray Oscilloscope (CRO)</li> <li>◆ Q-meter</li> </ul>		<ul style="list-style-type: none"> <li>◆ Basics of electronic measurements</li> <li>◆ Digital &amp; electronic voltmeter ◆ Digital frequency meter ◆ Transducers &amp; Displays</li> <li>◆ Basics of Telemetry</li> <li>◆ Data Acquisition System</li> </ul>
<b>Network Theory (NT)</b>	<b>NT-1</b>		<b>NT-2</b>	
	<ul style="list-style-type: none"> <li>◆ Network elements ◆ Network theorems</li> <li>◆ 2-port networks</li> </ul>		<ul style="list-style-type: none"> <li>◆ Transient and Steady State Response</li> <li>◆ Steady State Sinusoidal analysis</li> <li>◆ Resonance</li> </ul>	
<b>Analog and Digital Circuits (ADC)</b>	<b>ADC-1</b>	<b>ADC-2</b>	<b>ADC-3</b>	<b>ADC-4</b>
	<ul style="list-style-type: none"> <li>◆ Small Signal equivalent of Diodes, BJTs and FETs</li> <li>◆ Different Diode Circuits</li> <li>◆ Biasing and Stability of BJTs &amp; JFET amplifier circuits</li> </ul>	<ul style="list-style-type: none"> <li>◆ Analysis / Design of amplifiers signal &amp; multi-stage</li> <li>◆ Feedback &amp; its uses</li> <li>◆ Active filters, timers, multipliers, wave shaping, A/D &amp; D/A converters</li> </ul>	<ul style="list-style-type: none"> <li>◆ Boolean Algebra &amp; Logic Gates</li> <li>◆ Combinational circuits : Design &amp; Applications</li> <li>◆ Memories and Microprocessor : Design &amp; Applications</li> </ul>	<ul style="list-style-type: none"> <li>◆ Sequential circuits : Design &amp; Applications</li> <li>◆ Design IC Logic families</li> </ul>
<b>Among and Digital Communication (COMM)</b>	<b>COMM-1</b>		<b>COMM-2</b>	
	<ul style="list-style-type: none"> <li>◆ Probability Theory</li> <li>◆ Analog Communication Systems</li> </ul>		<ul style="list-style-type: none"> <li>◆ Random Signals and Noise</li> <li>◆ Digital Communication Systems</li> </ul>	
<b>Control Systems (CS)</b>	<b>CS-1</b>		<b>CS-2</b>	
	<ul style="list-style-type: none"> <li>◆ Signals and Systems</li> <li>◆ System Realization</li> <li>◆ Transforms &amp; their Applications</li> </ul>		<ul style="list-style-type: none"> <li>◆ Basics of Control Systems</li> <li>◆ Block Diagram &amp; Signal Flow Graphs</li> <li>◆ Time Response Analysis</li> <li>◆ Routh Hurwitz criteria &amp; Root Locus Technique</li> </ul>	
<b>Computer Organization and Architecture (CO)</b>	<b>CO-1</b>		<b>CO-2</b>	
	<ul style="list-style-type: none"> <li>◆ Basics of Computer Organization</li> </ul>		<ul style="list-style-type: none"> <li>◆ Operating Systems</li> </ul>	
<b>Electromagnetics (EMT)</b>	<b>EMT-1</b>		<b>EMT-2</b>	
	<ul style="list-style-type: none"> <li>◆ Elements of Vector Calculus</li> <li>◆ Electrostatics</li> <li>◆ Magnetostatics</li> </ul>		<ul style="list-style-type: none"> <li>◆ Maxwell's Equations</li> <li>◆ Electromagnetic Wave propagation through different media</li> <li>◆ Transmission Lines</li> </ul>	
<b>Advanced Electronics Topics (AET)</b>	<b>AET-1</b>		<b>AET-2</b>	
	<ul style="list-style-type: none"> <li>◆ VLSI Technology ◆ VLSI Design</li> <li>◆ Mealy and Moore circuit design</li> <li>◆ Pipeline concept and functions</li> <li>◆ Designs for testability and examples</li> </ul>		<ul style="list-style-type: none"> <li>◆ Digital Signals Processing</li> <li>◆ Digital Filters</li> <li>◆ Speech / Audio / Radar Signal Processing</li> </ul>	
<b>Advanced communication Topics (ACT)</b>	<b>ACT-1</b>		<b>ACT-2</b>	
	<ul style="list-style-type: none"> <li>◆ Communication Networks : Principles / Practices / Technologies / Uses / OSI Model / Security</li> <li>◆ Basic packet multiplexed streams / scheduling</li> <li>◆ Protocols (TCP / TCP-IP)</li> </ul>		<ul style="list-style-type: none"> <li>◆ Microwave &amp; Satellite Communication</li> <li>◆ Fiber Optic Communication</li> <li>◆ Cellular Networks : Types, Analysis</li> </ul>	

In base loop;

$$-2V + 12I_B + 0.7 = 0$$

$$\Rightarrow I_B = \frac{2-0.7}{12} = \frac{1.3}{12} = 0.10833 \text{ mA}$$

From collector loop,

Transistor is in saturation region

$$-5V + 4.8I_C + 0.2 = 0$$

$$I_C = \frac{5-0.2}{4.8 \times 10^3} = \frac{4.8}{4.8 \times 10^3} = 1 \text{ mA}$$

We know that,

In saturation,

$$I_B \geq I_{B \text{ min.}} = \frac{I_{C \text{ sat}}}{\beta}$$

$$\Rightarrow I_B \geq \frac{1 \text{ mA}}{\beta}$$

$$\Rightarrow \beta \geq \frac{1}{0.10833}$$

$$\text{and, } \beta_{\text{min}} = 9.23$$

$$\alpha_{\text{min}} = \frac{\beta_{\text{min.}}}{1 + \beta_{\text{min.}}} = 0.902$$

$$\alpha_{\text{min}} = 0.902$$

42. The expression for an electric field in free space is

$E = E_0(\hat{x} + \hat{y} + j2\hat{z})e^{-j(\omega t - kx + ky)}$  where  $x, y, z$  represent the spatial coordinates,  $t$  represents time and  $\omega, k$  are constants. This electric field

- (a) does not represent a plane wave
- (b) represents a circularly polarized plane wave propagating normal to the  $z$ -axis
- (c) represents and elliptically polarized plane wave propagating along the  $x$ - $y$  plane

(d) represents a linearly polarized plane wave

Sol. (c)

$$E = E_0(\hat{x} + \hat{y} + j2\hat{z})e^{-j(\omega t - kx + ky)}$$

We know,

$$e^{-jkr} = e^{-j(-kx + ky)}$$

$$\therefore kr = k(-x + y)$$

Propagation vector  $\hat{a}_p$

$$= \frac{\nabla(kr)}{|\nabla(kr)|}$$

$$\nabla(kr) = k(-\hat{x} + \hat{y})$$

$$|\nabla(kr)| = k\sqrt{2}$$

$$\therefore \hat{a}_p = \frac{\nabla(kr)}{|\nabla(kr)|}$$

$$= \frac{-\hat{x} + \hat{y}}{\sqrt{2}}$$

For plane wave,

$$\hat{a}_p \hat{E} = \left[ \frac{-\hat{x} + \hat{y}}{\sqrt{2}} \right] \cdot E_0[\hat{x} + \hat{y} + j2\hat{z}]$$

$$\hat{a}_p E_p = 0$$

$\therefore$  Given is a plane wave,

$$\text{As, } E = E_0(\hat{x} + \hat{y} + j2\hat{z})e^{-j(\omega t - kx + ky)}$$

For the given, plane of incidence is  $xy$  plane  $E$  in  $xy$  plane is parallel polarized,

$E_{||} = |E|_{xy} = \sqrt{1+1} = \sqrt{2}$  and along  $z$  is perpendicular polarize  $E_{\perp} = |E_z|_z = \sqrt{2^2} = 2$ .

$$|E_T| = |E_{||}| + |E_r|$$

$$= \sqrt{2} + 2$$

$$|E_{||}| \neq |E_r|$$

and phase difference is  $90^\circ$ ; i.e., given is a elliptically polarized plane wave.

43. The following FIVE instructions were executed on an 8085 microprocessor

MVI A, 33H



MVI B, 78H

ADD B

CMA

ANI 32H

The Accumulator value immediately after the execution of the fifth instruction is

- (a) 00H
- (b) 10H
- (c) 11H
- (d) 32H

**Sol. (b)**

MVI A 33H  $\Rightarrow [A] = 33 H$

MVI B 78H  $\Rightarrow [B] = 78H$

ADD B  $\Rightarrow [A] \leftarrow [A]+[B]$

$$\begin{array}{r} \Rightarrow 0011 \ 0011 \\ +0111 \ 1000 \\ \hline \underbrace{1010}_A \ \underbrace{1011}_B \Rightarrow AB H \end{array}$$

i.e.  $[A] = AB H$

CMA  $\Rightarrow$  complement accumulator

i.e.  $[A] \leftarrow \bar{A}$

where,  $\bar{A} = \overline{1010 \ 1011} = 0101 \ 0100$

ANI 32H  $\Rightarrow \begin{array}{r} 0011 \ 0010 \\ 0101 \ 0100 \\ \hline 0001 \ 0000 \Rightarrow 10H \end{array}$

$[A] = 10H$

i.e. option (B)

44. Which one of the following options correctly describes the location of the roots of the equation  $s^4 + s^2 + 1 = 0$  on the complex plane?

- (a) Four left half plane (LHP) roots
- (b) One right half plane (RHP) root, one LHP root and two roots on the imaginary axis
- (c) Two RHP roots and two LHP roots
- (d) All four roots are on the imaginary axis

**Sol. (c)**

Given equation is,

$$s^4 + s^2 + 1 = 0$$

Let  $s^2 = y$

$$\text{then } y^2 + y + 1 = 0$$

$$\Rightarrow y = \frac{-1 \pm \sqrt{1-4}}{2} = \frac{-1 \pm j\sqrt{3}}{2}$$


$$\Rightarrow y = 1 \angle 120^\circ \text{ and } 1 \angle -120^\circ$$

$$\text{for } y = s^2 = 1 \angle 120^\circ$$

$$\Rightarrow s = \pm (1 \angle 60^\circ)$$

$$\text{and, for } y = s^2 = 1 \angle -120^\circ$$
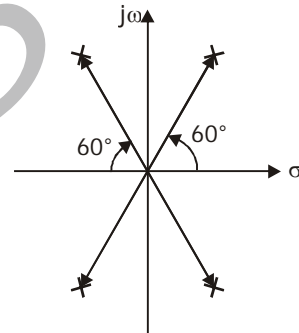
$$\Rightarrow s = \pm (1 \angle -60^\circ)$$




i.e. equation has two right half plane (RHP) roots and two left half plane (LHP) roots. i.e. option (c).

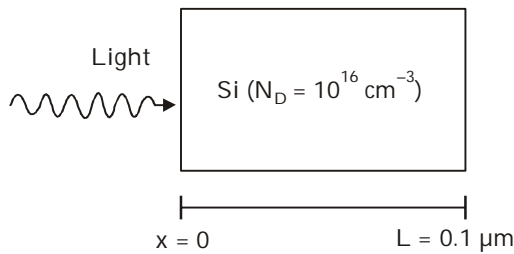45. As shown a uniformly doped Silicon (Si) bar of length  $L = 0.1 \mu m$  with a donor concentration  $N_D = 10^{16} cm^{-3}$  is illuminated at  $x = 0$  such that electron and hole pairs are generated at the rate of  $G_L = G_{L0}$

$$\left(1 - \frac{x}{L}\right), 0 \leq x \leq L. \text{ where, } G_{L0} = 10^{17} cm^{-3}/s.$$

Hole lifetime  $10^{-4}s$ , electronic charge  $q = 1.6 \times 10^{-19} C$ , hole diffusion coefficient  $D_p = 100 cm^2/s$  and low level injection condition prevails. Assuming a linearly decaying steady state excess hole concentration that goes to 0 at  $x = L$ , the magnitude of the diffusion current density at  $x = L/2$ , in  $A/cm^2$ , is \_\_\_\_.



**Sol. (16)**

Given,  $L = 0.1 \mu\text{m}$   
 so,  $N_D = 10^{16}/\text{cm}^3$  at  $x = 0$   
 Hole pair generated rate,

$$G_L = G_{L_0} \left(1 - \frac{x}{L}\right)$$

$0 \leq x \leq L$

Where,  $G_{L_0} = 10^{17} \text{ cm}^{-3} \text{ s}^{-1}$ ,  
 $\tau = 10^{-4} \text{ s}$ ,  
 $q = 1.6 \times 10^{-19} \text{ C}$ ,  
 $D_p = 100 \text{ cm}^2/\text{s}$

$$J_{p\text{diff}} = ?$$

$\therefore$  Net hole density varying in the direction of  $x$  is:

$$\begin{aligned} P_n(x) &= P_{n_0} + PP \\ &= P_{n_0} + G_L I_p \\ &= P_{n_0} + G_{L_0} I_p \left(1 - \frac{x}{L}\right) \end{aligned}$$

$$\begin{aligned} J_{p\text{diff}} &= -eD_p \frac{dp}{dx} \\ &= -eD_p \frac{dp}{dx} \\ &= -eD_p \left[ \frac{-G_{L_0} \cdot I_p}{L} \right] \end{aligned}$$

$$\begin{aligned} &= \frac{1.6 \times 10^{-19} \times 100 \times 10^{17} \times 10^{-4}}{0.1 \times 10^{-4}} \\ &= 16 \text{ A/cm}^2 \end{aligned}$$

46. Let  $I = \int_C (2z dx + 2y dy + 2x dz)$  where  $x, y, z$  are real and let  $C$  be the straight line segment from point A: (0, 2, 1) to point B: (4, 1, -1). The value of  $I$  is \_\_\_\_\_

**Sol. (-11)**

$$I = \int_C (2z dx + 2y dy + 2x dz)$$

The equation of straight line joining A(0, 2, 1) and B (4, 1, -1) is given by

$$\begin{aligned} \frac{x-0}{4-0} &= \frac{y-2}{1-2} = \frac{z-1}{-1-1} \\ \Rightarrow \frac{x}{4} &= \frac{y-2}{-1} = \frac{z-1}{-2} \\ x &= -4y + 8 = -2z + 2 \end{aligned}$$

$$\Rightarrow y = \frac{8-x}{4}$$

$$\therefore dy = \frac{-1}{4} dx$$

$$\text{and, } z = \frac{2-x}{2}$$

$$\therefore dz = \frac{-1}{2} dx$$

$$\begin{aligned} \text{then, } I &= \int_0^4 \left[ 2 \left( \frac{2-x}{2} \right) dx + 2 \left( \frac{8-x}{4} \right) \left( \frac{-1}{4} dx \right) \right. \\ &\quad \left. + 2x \left( \frac{-1}{2} dx \right) \right] \end{aligned}$$

$$= \int_0^4 \left( 2-x-1 + \frac{x}{8} - x \right) dx$$

$$= \int_0^4 \left( 1 - \frac{15}{8}x \right) dx = \left[ x - \frac{15}{16}x^2 \right]_0^4$$

$$= 4 - 15 = -11$$

47. An optical fiber is kept along the  $z$  direction. The refractive indices for the electric fields along  $\hat{x}$  and  $\hat{y}$  directions in the fiber are  $n_x = 1.50000$  and  $n_y = 1.5001$ , respectively ( $n_x \neq n_y$  due to the imperfection in the fiber cross-section). The free space wavelength of a light wave propagating in the fiber is  $1.5 \mu\text{m}$ . If the lightwave is circularly polarized at the input of the fiber, the minimum propagation distance after which it becomes linearly polarized in centimeters, is \_\_\_\_\_

# OUR TOP RESULTS IN ESE-2016



## IES MASTER

Institute for Engineers (IES/GATE/PSUs)

AIR 1 CE		AIR 3 CE		AIR 4 CE		AIR 6 CE		AIR 7 CE		AIR 8 CE		AIR 9 CE	
JATIN KUMAR		RACHIT JAIN		ADARSH R. SRIVASTAV		NITISH GARG		SHIVAM DWIVEDI		AMRIT ANAND		AVDHESH MEENA	

AIR 10 CE		AIR 11 CE		AIR 12 CE		AIR 14 CE		AIR 15 CE		AIR 16 CE		AIR 17 CE	
HIMANSHU TIWARI		PRAKHAR TRIPATHI		NITIN KR. AGARWAL		MITARPAL TANWAR		ASHISH GUPTA		SIDDHARTH MAHAJAN		DEVKISHAN KUMHAR	

AIR 22 CE		AIR 24 CE		AIR 26 CE		AIR 28 CE		AIR 29 CE		AIR 31 CE		AIR 33 CE	
BHARAT BHUSHAN DIXIT		HISAM UDDIN		PRASHANT TRIPATHI		SHUBHANSHU JAIN		MANISH KR. SHARMA		ABHISHEK MITTAL		SPARSH BHARDWAJ	

AIR 1 ME		AIR 3 ME		AIR 5 ME		AIR 12 ME		AIR 13 ME		AIR 14 ME		AIR 17 ME	
MOHAMMAD IDUL AHMED		CHIRAG SRIVASTAV		DEEPAK VIJAY		SACHIN JAIN		KHILENDRA SINGH CHAUHAN		VINAY KUMAR		SAMARTH AGARWAL	

AIR 18 ME		AIR 40 ME		AIR 51 ME		AIR 63 ME		AIR 71 ME		AIR 106 ME		AIR 108 ME		AIR 131 ME		AIR 132 ME		AIR 156 ME		AIR 38 EE		AIR 94 EE	
ROOPAK TIWARI		ANIL KUMAR		ANKUR SINGH CHAUHAN		NIMIT AGRAWAL		SURYANK GUPTA		ARPIT KUMAR		P.S. MANI KUMAR		RAHUL RAJPAL SINGH		SACHINI KUMAR		ARVIND KUMAR		VIDYA		RITA NAGDEVE	
AIR 106 EE		AIR 35 CE		AIR 37 CE		AIR 38 CE		AIR 39 CE		AIR 40 CE		AIR 43 CE		AIR 44 CE		AIR 46 CE		AIR 47 CE		AIR 48 CE		AIR 51 CE	
RAJIV DAS		RAVI MITTAL		CHANDAN SINGH		K.M.N.V.S. RAVI TEJA		MAHAMMED USAD		J.K. KUMAR REDDY		SHWET KUMAR		GAURAV SINGLA		VAIBHAV PODDAR		AJIT KR. PALSANIA		VIKRAM MITTU		HARSHIT CHOUHAN	
AIR 52 CE		AIR 53 CE		AIR 55 CE		AIR 59 CE		AIR 61 CE		AIR 62 CE		AIR 63 CE		AIR 65 CE		AIR 66 CE		AIR 67 CE		AIR 68 CE		AIR 69 CE	
VIKAS KR. SEHRA		AYUSH TIWARI		SAGAR MAHESHWARI		AKHILESH		ABHIPREEMA AWANA		MAYANK AGRAWAL		THATI SONY		SUSHIL KR. SINGH		ANANT YADAV		P. JAMSHEER		AVINASH SAHANI		PAYAL GOYAL	
AIR 70 CE		AIR 71 CE		AIR 72 CE		AIR 74 CE		AIR 75 CE		AIR 76 CE		AIR 77 CE		AIR 78 CE		AIR 80 CE		AIR 81 CE		AIR 87 CE		AIR 88 CE	
PRANAV		DEEPAK NEGI		KULDEEP SINGH		NAVEEN YADAV		VIVEK RANJAN PANDEY		ANKUR GOYAL		VIPUL KUMAR		AMIT GUPTA		DHAWAL SRIVASTAVA		NITIN MANGWAL		SHYAMAL KUMAR		RAJAT KOTHARI	
AIR 93 CE		AIR 95 CE		AIR 97 CE		AIR 99 CE		AIR 105 CE		AIR 106 CE		AIR 108 CE		AIR 109 CE		AIR 110 CE		AIR 112 CE		AIR 113 CE		AIR 115 CE	
AJAY KR. CHAUDHARY		MADHURIMA BHATTACHARYA		DIGVIJAY CHAUHAN		ABHISHEK		CHITRANSHU		NITESH		PRIYANK GUPTA		MAHOJ KUMAR MISHRA		SHIVAM PRATAP SINGH		MILIN MITTAL		ANKIT		KUNWAR CHRAYA	
AIR 116 CE		AIR 119 CE		AIR 120 CE		AIR 121 CE		AIR 122 CE		AIR 125 CE		AIR 126 CE		AIR 130 CE		AIR 132 CE		AIR 136 CE		AIR 137 CE		AIR 138 CE	
SIDDHARTH SONI		AJAY SHARMA		ASHISH PANDEY		DANISH KHAN		OM NATH BIHARI		GOPAL PATRALEKH		AKASH ROUT		RANVIJAY AZAD		GYANPRAKASH SONI		MOHIT KUMAR		NIKAJ KUMAR YADAV		MOHISH KR. SINHA	
AIR 142 CE		AIR 143 CE		AIR 145 CE		AIR 147 CE		AIR 150 CE		AIR 151 CE		AIR 153 CE		AIR 154 CE		AIR 161 CE		AIR 165 CE		AIR 166 CE		AIR 168 CE	
ABHISHEK KUMAR YADAV		VIJAY ANAND VERMA		DIVIJ SAHANI		MANSHA K. MEENA		SATYAPAL SANJU		AHTESHAMUL HAQ		SURAJ PRATAP SINGH		ALOK KUMAR VERMA		JAY KARAN YADAV		PRASANT KUMAR		PUKHA RAM		MAHENDRA SINGH JATAV	
AIR 169 CE		AIR 171 CE		AIR 173 CE		AIR 174 CE		AIR 175 CE		AIR 179 CE		AIR 180 CE		AIR 183 CE		AIR 184 CE		AIR 187 CE		AIR 188 CE		AIR 189 CE	
ABHISHEK		BUDDI PRAKASH MEENA		DHEERESH KR.		VINITA		SAURAV SHIVHARE		LALIT KUMAR		NAVALPREET KAUR		SANTOSH KR. MEENA		ABHISHEK KUMAR		RAHUL JAJORIA		BHARTI MEENA		JITENDRA KR. MEENA	
AIR 190 CE		AIR 193 CE		AIR 194 CE		AIR 199 CE		AIR 203 CE		AIR 207 CE		AIR 210 CE		AIR 212 CE		AIR 213 CE		AIR 216 CE		AIR 221 CE		AIR 224 CE	
SAURAV DEO		PRADEEP KR. MEENA		NITESH KR. SINGH		AMIT KR. MEENA		ACHAL KUMAR		LALIT MOHAN MEENA		SUNIL KR. MEENA		AKASH CHANDRA		MAHENDRA KR. MEENA		SUMAN JEE		ALOK OJHA		ANKIT KR. SHUKLA	

Received so far.... [ If found any discrepancy please bring it to our notice. ]

Sol. (0.375)

For to have linear polarization, phase difference has to be  $0^\circ$  or  $180^\circ$ . Given the light wave is circularly polarized that is initial phase difference is  $90^\circ$ .

$$\begin{aligned} \text{so, } \beta_1 z \sim \beta_2 z &= \frac{\pi}{2} \\ \Rightarrow \frac{w}{V_{Px}} z \sim \frac{w}{V_{Py}} z &= \frac{\pi}{2} \\ \Rightarrow \frac{2\pi f}{c} (\eta_x \sim \eta_y) z &= \frac{\pi}{2} \\ \Rightarrow \frac{2\pi}{\lambda} (\eta_x \sim \eta_y) z &= \frac{\pi}{2} \\ \Rightarrow z &= \frac{\pi}{2} \times \frac{\lambda}{2\pi(\eta_x \sim \eta_y)} \\ &= \frac{\lambda}{4(\eta_x \sim \eta_y)} \\ &= \frac{1.5 \times 10^{-6}}{4 \times 0.0001} \\ &= 0.375 \text{ cm} \end{aligned}$$

48. The Nyquist plot of the transfer function

$$G(s) = \frac{K}{(s^2 + 2s + 2)(s + 2)}$$

does not encircle the point  $(-1 + j0)$  for  $K = 10$  but does encircle the point  $(-1 + j0)$  for  $K = 100$ . Then the closed loop system (having unity gain feedback) is

- (a) stable for  $K = 10$  and stable for  $K = 100$
- (b) stable for  $K = 10$  and unstable for  $K = 100$
- (c) unstable for  $K = 10$  and stable for  $K = 100$
- (d) unstable for  $K = 10$  and unstable for  $K = 100$

Sol. (b)

Given open-loop transfer function

$$G(s) = \frac{k}{(s^2 + 2s + 2)(s + 2)}$$

poles:  $s^2 + 2s + 2 = 0$

$$s = \frac{-2 \pm \sqrt{4 - 8}}{2} = \frac{-2 \pm j2}{2} = -1 \pm j$$

and  $s = -2$

i.e. none of the poles of open-loop system lies on right half of s-plane.

i.e.  $P = 0$ .

Now, for  $k = 10$ :

No. of encirclement = 0

i.e.  $N = 0$

since,  $Z = N + P = 0 + 0 = 0$

i.e. none of the poles of closed loop system lies in right half of s-plane. So, system will be stable.

For  $K = 100$ :

No. of encirclement = 1

i.e.  $N = 1$

since,  $Z = N + P = 1 + 0 = 1$ .

i.e. one pole of closed loop system lies in right half of s-plane. So, system will be unstable.

i.e. option (b).

49. A three dimensional region R of finite volume is described by

$$x^2 + y^2 \leq z^3; 0 \leq z \leq 1.$$

where  $x, y, z$  are real. The volume of R (upto two decimal place) is \_\_\_\_\_

Sol.  $\left(\frac{\pi}{4}\right)$

$$\because 0 \leq z \leq 1$$

$$\Rightarrow z_{\min} = 0$$

$$\& z_{\max} = 1$$

$$\text{so, } x^2 + y^2 \leq z^3 \Rightarrow \begin{cases} \text{Min}(x^2 + y^2) = 0 \\ \text{Max}(x^2 + y^2) = 0 \end{cases}$$

$$\Rightarrow \min x = 0 \text{ \& \; } \min y = 0$$

$$\max y = \sqrt{1-x^2} \text{ \& \; } \max x = 1$$

so,  $0 \leq z \leq 1, 0 \leq y \leq \sqrt{1-x^2}, 0 \leq x \leq 1$

so, Volume =  $\iiint (1) dx dy dz$

$$= \int_{x=0}^1 \int_{z=0}^1 \int_{y=0}^{\sqrt{1-x^2}} (1) dy dx dz$$

$$= \int_{z=0}^1 \left[ \int_{x=0}^1 \sqrt{1-x^2} dx \right] dz$$

$$= \int_{z=0}^1 \left( \frac{\pi}{4} \right) dz$$

$$= \frac{\pi}{4}$$

Method II: In cylindrical coordinates (x, y, z)  $\approx$  (r,  $\theta$ , z)

Where  $x^2 + y^2 \leq z^2 = 0 \leq z \leq 1$

$$0 \leq \theta \leq 2\pi$$

$$0 \leq r \leq z^{\frac{3}{2}}$$

$[\because x^2 + y^2 = r^2]$

$$V = \iiint (1) dx dy dz$$

$$= \iiint r dr d\theta dz$$

$$= \int_{z=0}^1 \int_{\theta=0}^{2\pi} \int_{r=0}^{z^{3/2}} r \cdot dr \cdot d\theta dz$$

$$= \int_{z=0}^1 \int_{\theta=0}^{2\pi} \left( \frac{z^3}{2} \right) d\theta dz$$

$$= \int_{\theta=0}^{2\pi} \left( \frac{z^4}{8} \right)_0^1 d\theta$$

$$= \frac{1}{8} \int_0^{2\pi} (1) d\theta$$

$$= \frac{\pi}{4}$$

50. Which one of the following gives the simplified sum of products expression for the Boolean function  $F = m_0 + m_2 + m_3 + m_5$ , where  $m_0, m_2, m_3$  and  $m_5$  are minterms corresponding to the inputs A, B and C with A is the MSB and C as the LSB?

- (a)  $\bar{A}B + \bar{A}\bar{B}\bar{C} + \bar{A}BC$
- (b)  $\bar{A}\bar{C} + \bar{A}B + \bar{A}\bar{B}C$
- (c)  $\bar{A}\bar{C} + \bar{A}\bar{B} + \bar{A}\bar{B}C$
- (d)  $\bar{A}BC + \bar{A}\bar{C} + \bar{A}\bar{B}C$


Sol. (b)

	BC			
A	00	01	11	10
0	$m_0$	$m_1$	$m_3$	$m_2$
1	$m_4$	$m_5$	$m_7$	$m_6$

$$F = (m_0 + m_2) + (m_2 + m_3) + m_5$$

$$= \bar{A}\bar{C} + \bar{A}B + \bar{A}\bar{B}C$$

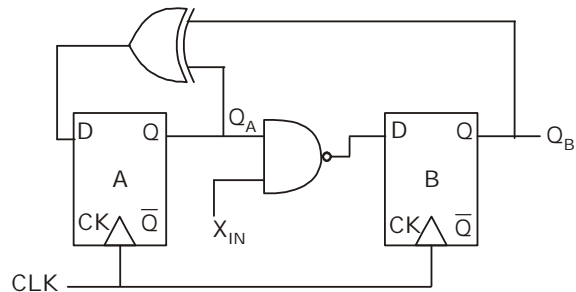51. A finite state machine (FSM) is implemented using the D flip-flops A and B and logic gates as shown in the figure below. The four possible states of the FSM are  $Q_A Q_B = 00, 01, 10,$  and  $11$



Assume that  $X_{IN}$  is held at a constant logic level throughout the operation of the FSM. When the FSM is initialized to the state  $Q_A Q_B = 00$  and clocked, after a few clock cycle, it starts cycling through

- (a) all of the four possible states if  $X_{IN} = 1$
- (b) three of the four possible states if  $X_{IN} = 0$
- (c) only two of the four possible states if  $X_{IN} = 1$

(d) only two of the four possible states if  $X_{IN} = 0$

**Sol. (d)**

When  $X_{IN} = 0$ :

	$Q_A$	$Q_B$	$D_A$	$D_B$
CLK 0	0	0	0	1
CLK 1	0	1	1	1
CLK 2	1	1	0	1
CLK 3	0	1	1	1
$\vdots$	$\vdots$	$\vdots$	$\vdots$	$\vdots$

i.e. output  $Q_A Q_B$  starts cycling through only two of the four possible states.

When  $X_{IN} = 1$ :

	$Q_A$	$Q_B$	$D_A$	$D_B$
CLK 0	0	0	0	1
CLK 1	0	1	1	1
CLK 2	1	1	0	0
CLK 3	0	0	0	1
$\vdots$	$\vdots$	$\vdots$	$\vdots$	$\vdots$

i.e. output  $Q_A Q_B$  starts cycling through three of the four possible states.

52. Let  $h[n]$  be the impulse response of a discrete-time linear time invariant (LTI) filter. The impulse response is given by

$$h[0] = \frac{1}{3}; h[1] = \frac{1}{3}; h[2] = \frac{1}{3}; \text{ and } h[n] = 0 \text{ for } n < 0 \text{ and } n > 2.$$

let  $H(\omega)$  be the discrete-time Fourier transform (DTFT) of  $h[n]$ . where  $\omega$  is the normalized angular frequency in radians. Given that  $H(\omega_0) = 0$  and  $0 < \omega_0 < \pi$ , the value of  $\omega_0$  (in radian) is equal to \_\_\_\_\_

**Sol. (2.094)**

$$h(0) = \frac{1}{3};$$

$$h(1) = \frac{1}{3};$$

$$h(2) = \frac{1}{3};$$

and  $h[n] = 0$

for and also given that  $H(\omega_0) = 0$  and  $0 < \omega_0 < \pi$

$$h[n] = \left[ \frac{1}{3}, \frac{1}{3}, \frac{1}{3} \right]$$

Since,  $h[n] = \frac{1}{3}\delta[n] + \frac{1}{3}\delta[n-1] + \frac{1}{3}\delta[n-2]$

So,  $H(e^{j\omega}) = \frac{1}{3} + \frac{1}{3}e^{-j\omega} + \frac{1}{3}e^{-2j\omega}$

$$= \frac{1}{3}e^{-j\omega} + \frac{1}{3}e^{-j\omega}(e^{j\omega} + e^{-j\omega})$$

$$\left[ \frac{e^{j\omega} + e^{-j\omega}}{2} = \cos \omega \right]$$

$$H(e^{j\omega}) = \frac{1}{3}e^{-j\omega}[1 + 2\cos \omega]$$

$$H(e^{j\omega_0}) = 0 \quad \text{when}$$

$$\Rightarrow 1 + 2\cos \omega_0 = 0$$

$$\Rightarrow \cos \omega_0 = \frac{-1}{2}$$

$$\Rightarrow \omega_0 = \cos^{-1}\left(\frac{1}{2}\right) = 120^\circ$$

$$= \frac{2\pi}{3} = 2.094 \text{ rad.}$$


53. A half wavelength dipole is kept in the x-y plane and oriented along  $45^\circ$  from the x-axis. Determine the direction of null in the radiation pattern for  $0 \leq \phi \leq \pi$ . Here the angle  $\theta$  ( $0 \leq \theta \leq \pi$ ) is measured from the z-axis, and the angle  $\phi$  ( $0 \leq \phi \leq 2\pi$ ) is measured from the x-axis in the x-y plane.

- (a)  $\theta = 90^\circ, \phi = 45^\circ$
- (b)  $\theta = 45^\circ, \phi = 90^\circ$
- (c)  $\theta = 90^\circ, \phi = 135^\circ$
- (d)  $\theta = 45^\circ, \phi = 135^\circ$

Sol. (a)

As the antenna is placed in xy-plane which is horizontal plane

$$\text{i.e., } \theta = \frac{\pi}{2}$$

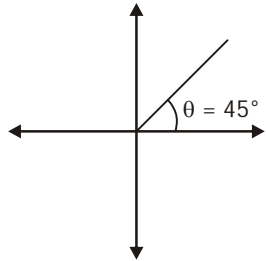

As there is no field along antenna i.e. null along antenna,

$$\theta = 45^\circ$$

as  $0 \leq \phi \leq \pi$  given

$\therefore$  for the given antenna null is at  $\theta = 90^\circ$ ,  
 $\phi = 45^\circ$ .

54. Starting with  $x = 1$ , the solution of the equation  $x^3 + x = 1$ , after two iterations of Newton-Raphson's method (upto two decimal places) is \_\_\_\_\_

Sol. (0.686)

Let,

$$f(x) = x^3 + x - 1$$

$$f'(x) = 3x^2 + 1$$

Using Newton - Raphson formula

$$x_{n+1} = x_n - \frac{f(x_n)}{f'(x_n)}$$

Starting with  $x_n = 1$

$$x_{n+1} = 1 - \frac{f(1)}{f'(1)} = 1 - \frac{1+1-1}{3 \times 1 + 1}$$

$$= 1 - \frac{1}{4} = 0.75$$

Now,  $x'_n = 0.75$


$$x'_{n+1} = 0.75 - \frac{f(0.75)}{f'(0.75)}$$

$$= 0.75 - \frac{(0.75)^3 + (0.75) - 1}{3 \times (0.75)^2 + 1}$$

$$= 0.75 - \frac{0.171875}{2.6875}$$

$$= 0.686$$

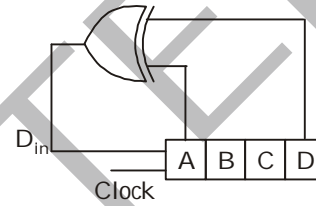55. A 4-bit shift register circuit configured for right-shift operation i.e.  $D_{in} \rightarrow A, A \rightarrow B, B \rightarrow C, C \rightarrow D$ , is shown. If the present state of the shift register is  $ABCD = 1101$ , the number of clock cycles required to reach the state  $ABCD = 1111$  is \_\_\_\_\_



Sol. (10)

CLK	A	B	C	D	$D_{in} = A \oplus D$
0	1	1	0	1	0
1	0	1	1	0	0
2	0	0	1	1	1
3	1	0	0	1	0
4	0	1	0	0	0
5	0	0	1	0	0
6	0	0	0	1	1
7	1	0	0	0	1
8	1	1	0	0	1
9	1	1	1	0	1
10	1	1	1	1	0

← Required State

$\therefore$  The number of Clock Cycles required = 10.

### Aptitude

1. 40% of deaths on city roads may be attributed to drunken driving. The number of degrees needs to represent this as a slice of a pie chart is
- (a) 120  
 (b) 144  
 (c) 160  
 (d) 212

Sol. (b)


In pie-chart, 100% represents  $360^\circ$

$$\therefore 40\% = \frac{40}{100} \times 360 = 144^\circ$$

2. Some tables are shelves. Some shelves are chairs. All chairs are benches. Which of the following conclusions can be deduced from the preceding sentences?

- (I) At least one bench is a table  
 (II) At least one shelf is a bench  
 (III) At least one shelf is a table  
 (IV) All benches are chairs  
 (a) Only I  
 (b) Only II  
 (c) Only II and III  
 (d) Only IV

Sol. (b)

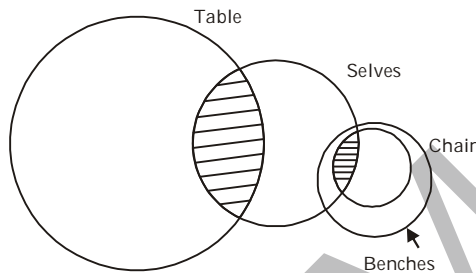

i.e. at least one shelf is a bench.

3. In the summer, water consumption is known to decrease overall by 25%. A Water Board official states that in the summer household consumption decreases by 20% while other consumption increased by 70%.

Which of the following statements is correct?

- (a) The ratio of household to other consumption is 8/17  
 (b) The ratio of household to other consumption is 1/17  
 (c) The ratio of household to other consumption is 17/8  
 (d) There are errors in the official's statement.

Sol. (d)

As the household consumption decreases by 20% and other consumption increase by 70% then the overall decrease must be less than 20%.

Hence, there are errors in the official's statement.

4. She has a sharp tongue and it can occasionally turn \_\_\_\_\_

- (a) hurtful (b) left  
 (c) methodical (d) vital

Sol. (a)

**Have a sharp tongue:** To be someone who often criticizes and speaks in a severe way.

So, it can occasionally turn hurtful.

5. I \_\_\_\_\_ made arrangements had I \_\_\_\_\_ informed earlier.

- (a) could have, been  
 (b) would have, being  
 (c) had, have  
 (d) had been, been

Sol. (a)

6. Truck (10 m long) and cars (5 m long) go on a single lane bridge. There must be gap of at least 20 m after each truck and a gap of at least 15 m after each car. Truck and cars travel at a speed of 36 km/h. If cars and trucks go alternately, what is the maximum number of vehicles that can use the bridge in one hour?

- (a) 1440 (b) 1200  
 (c) 720 (d) 600

Sol. (a)

Let the number of vehicles that can use the bridge in one hour are  $2x$  (i.e.  $x$  cars and  $x$  trucks).

Speed of Cars and Trucks = 36 Km/h

$$= \frac{36 \times 5}{18} = 10 \text{ m / sec.}$$

$\therefore$  In one hour,  
 $10 \times 60 \times 60 = (\text{length of Cars} + \text{gap after each cars}) \times x + (\text{length of Truck} + \text{gap after each Truck}) \times x$


$$\text{Or } 36000 = (5+15)x + (10+20)x$$

$$\text{Or } 50x = 36000$$

$$\text{Or } 2x = 1440$$



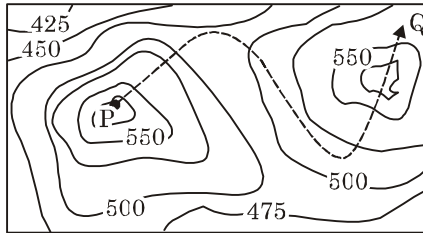
7. A contour line joins locations having the same height above the mean sea level. The following is a contour plot of a geographical region. Contour lines are shown at 25 m intervals in this plot.



The path from P to Q is best described by

- (a) Up-Down-Up-Down
- (b) Down-Up-Down-Up
- (c) Down-Up-Down
- (d) Up-Down-Up

**Sol. (c)**

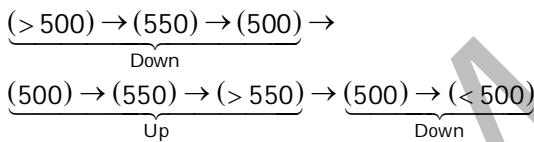

8. "If you are looking for a history of India or for an account of the rise and fall of the British Raj, or for the reason of the cleaving of the subcontinent into two mutually antagonistic parts and the effects this mutilation will have in the respective sections, and ultimately on Asia, you will not find it in these pages for though I have spent a lifetime in the country. I lived too near the seat of events, and was too intimately associated with the actors, to get the perspective needed for the impartial recording of these matters".

Here, the word 'antagonistic' is closest in meaning to

- (a) impartial
- (b) argumentative
- (c) separated
- (d) hostile


**Sol. (\*)**

9. S, T, U, V, W, X, Y, and Z are seated around a circular table. T's neighbours are Y and V, Z is seated third to the left of T and second to the right of S. U's neighbours are S and Y; and T and W are not seated opposite each other. Who is third to the left of V?

- (a) X
- (b) W
- (c) U
- (d) T

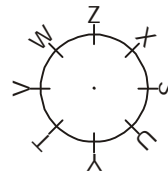**Sol. (a)**

The seating arrangement of different people according to questions is shown below



∴ X is third to the left of V.

10. There are 3 Indians and 3 Chinese in a group of 6 people. How many subgroups of this group can we choose so that every subgroup has at least one Indian?
- (a) 56
  - (b) 52
  - (c) 48
  - (d) 44

**Sol. (a)**

$$\begin{aligned}
 &\text{The total number of required subgroups} \\
 &= ({}^3C_1 + {}^3C_2 + {}^3C_3) \times ({}^3C_0 + {}^3C_1 + {}^3C_2 + {}^3C_3) \\
 &= (2^3 - 1) (2^3) \\
 &= 7 \times 8 \\
 &= 56.
 \end{aligned}$$