

**#420436****Topic:** Purely inductive circuit

A 44 mH inductor is connected to 220 V, 50 Hz ac supply. Determine the rms value of the current in the circuit.

**Solution**

We know that  $X_L = \omega L = 2\pi fL = 2 \times 3.14 \times 50 \times 44 \times 10^{-3} = 13.82\Omega$

Therefore,  $I_{rms} = \frac{E}{X_L} = \frac{220}{13.82} = 15.92A$

**#420521****Topic:** LCR circuits

A coil of inductance 0.50 H and resistance  $100\Omega$  is connected to a 240 V, 50 Hz ac supply.

- (a) What is the maximum current in the coil?  
(b) What is the time lag between the voltage maximum and the current maximum?

**Solution**

(a)

Peak velocity  $V_0 = \sqrt{2}V = 339.41$

$\omega = 2\pi f = 100\pi \text{ rad/s}$

$I_o = \frac{V_o}{\sqrt{R^2 + \omega^2 L^2}} = 1.82 A$

(b)

The voltage is given as  $V = V_o \cos \omega t$

The current is given as  $I = I_o \cos(\omega t - \phi)$

$\phi$  is the phase angle between the voltage and current.

The time lag is given as  $\phi/\omega$ .

Now phase angle is given as  $\tan \phi = \omega L/R = 2\pi \times 50 \times 0.5/100 = 1.57$

So  $\phi = \tan^{-1} 1.57 = 57.5^\circ = 57.5\pi/180 \text{ radians}$

time lag is  $t = \phi/\omega = 57.5\pi/180 \times 2\pi \times 50 = 3.19 \times 10^{-3} s$