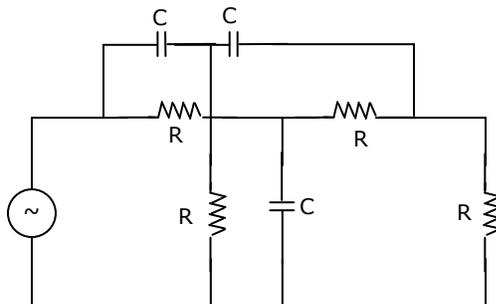


**Q.1 – Q.30 Carry One Mark Each**

1. The minimum number of equations required to analyze the circuit shown in Fig.Q.1 is




- (a) 3                      (b) 4                      (c) 6                      (d) 7
2. A source of angular frequency 1 rad/sec has a source impedance consisting of  $1\Omega$  resistance in series with 1 H inductance. The load that will obtain the maximum power transfer is
- (a)  $1\Omega$  resistance  
 (b)  $1\Omega$  resistance in parallel with 1 H inductance  
 (c)  $1\Omega$  resistance in series with 1 F capacitor  
 (d)  $1\Omega$  resistance in parallel with 1 F capacitor

3. A series RLC circuit has a resonance frequency of 1 kHz and a quality factor  $Q = 100$ . If each R, L and C is doubled from its original value, the new Q of the circuit is
- (a) 25                      (b) 50                      (c) 100                      (d) 200

4. The Laplace transform of  $i(t)$  is given by  $I(s) = \frac{2}{s(1+s)}$
- As  $t \rightarrow \infty$ , the value of  $i(t)$  tends to
- (a) 0                      (b) 1                      (c) 2                      (d)  $\infty$

5. The differential equation for the current  $i(t)$  in the circuit of Figure Q.5 is

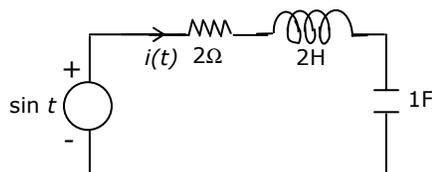- (a)  $2 \frac{d^2i}{dt^2} + 2 \frac{di}{dt} + i(t) = \sin t$   
 (b)  $\frac{d^2i}{dt^2} + 2 \frac{di}{dt} + 2i(t) = \cos t$   
 (c)  $2 \frac{d^2i}{dt^2} + 2 \frac{di}{dt} + i(t) = \cos t$   
 (d)  $\frac{d^2i}{dt^2} + 2 \frac{di}{dt} + 2i(t) = \sin t$




6. n-type silicon is obtained by doping silicon with  
 (a) Germanium (b) Aluminum (c) Boron (d) Phosphorus
7. The bandgap of silicon at 300 K is  
 (a) 1.36 eV (b) 1.10 eV (c) 0.80 eV (d) 0.67 eV
8. The intrinsic carrier concentration of silicon sample of 300 K is  $1.5 \times 10^{16}/\text{m}^3$ . If after doping, the number of majority carriers is  $5 \times 10^{20}/\text{m}^3$ , the minority carrier density is  
 (a)  $4.50 \times 10^{11}/\text{m}^3$  (b)  $3.33 \times 10^4/\text{m}^3$   
 (c)  $5.00 \times 10^{20}/\text{m}^3$  (d)  $3.00 \times 10^{-5}/\text{m}^3$
9. Choose proper substitutes for X and Y to make the following statement correct Tunnel diode and Avalanche photodiode are operated in X bias and Y bias respectively.  
 (a) X: reverse, Y: reverse (b) X: reverse, Y: forward  
 (c) X: forward, Y: reverse (d) X: forward, Y: forward
10. For an n-channel enhancement type MOSFET, if the source is connected at a higher potential than that of the bulk (i.e.  $V_{SB} > 0$ ), the threshold voltage  $V_T$  of the MOSFET will  
 (a) remain unchanged (b) decrease  
 (c) change polarity (d) increase
11. Choose the correct match for input resistance of various amplifier configurations shown below.


Configuration	Input resistance
CB: Common Base	LO: Low
CC: Common Collector	MO: Moderate
CE: Common Emitter	HI: High

- (a) CB-LO, CC-MO, CE-HI (b) CB-LO, CC-HI, CE-MO  
 (c) CB-MO, CC-HI, CE-LO (d) CB-HI, CC-LO, CE-MO

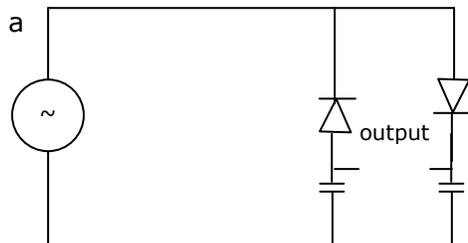12. The circuit shown in figure is best described as a  
 (a) bridge rectifier  
 (b) ring modulator  
 (c) frequency discriminatory  
 (d) voltage doubler



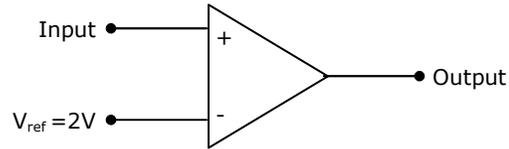
13. If the input to the ideal comparator shown in figure is a sinusoidal signal of 8V (peak to peak) without any DC component, then the output of the comparator has a duty cycle of



- (a)  $\frac{1}{2}$                       (b)  $\frac{1}{3}$                       (c)  $\frac{1}{6}$                       (d)  $\frac{q}{12}$
14. If the differential voltage gain and the common mode voltage gain of a differential amplifier are 48 dB and 2 dB respectively, then its common mode rejection ratio is  
(a) 23 dB                      (b) 25 dB                      (c) 46 dB                      (d) 50 dB
15. Generally, the gain of a transistor amplifier falls at high frequencies due to the  
(a) internal capacitances of the device  
(b) coupling capacitor at the input  
(c) skin effect  
(d) coupling capacitor at the output
16. The number of distinct Boolean expression of 4 variables is  
(a) 16                      (b) 256                      (c) 1024                      (d) 65536
17. The minimum number of comparators required to build an 8 bit flash ADC is  
(a) 8                      (b) 63                      (c) 255                      (d) 256
18. The output of the 74 series of TTL gates is taken from a BJT in  
(a) totem pole and common collector configuration  
(b) either totem pole or open collector configuration  
(c) common base configuration  
(d) common collector configuration
19. Without any additional circuitry, an 8:1 MUX can be used to obtain  
(a) some but not all Boolean functions of 3 variables  
(b) all function of 3 variables but none of 4 variables  
(c) all functions of 3 variables and some but not all of 4 variables  
(d) all functions of 4 variables

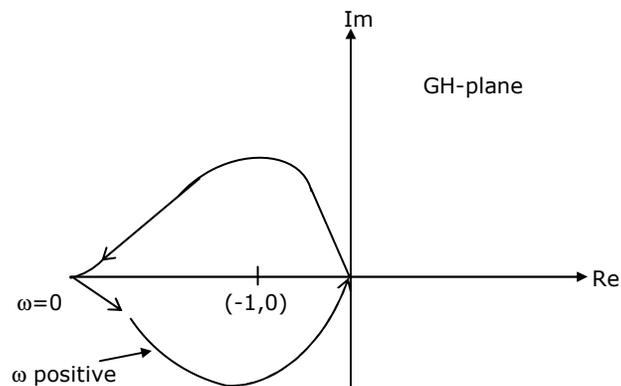20. A 0 to 6 counter consists of 3 flip flops and a combination circuit of 2 input gate(s). The combination circuit consists of  
 (a) one AND gate (b) one OR gate  
 (c) one AND gate and one OR gate (d) two AND gates
21. The Fourier series expansion of a real periodic signal with fundamental frequency  $f_0$  is given by  $g_p(t) = \sum_{n=-\infty}^{\infty} c_n e^{j2\pi n f_0 t}$  it is given that  $C_3 = 3 + j5$ . Then  $C_{-3}$  is  
 (a)  $5+j3$  (b)  $-3-j5$  (c)  $-5+j3$  (d)  $3-j5$
22. Let  $x(t)$  be the input to a linear, time-invariant system. The required output is  $4x(t-2)$ . The transfer function of the system should be  
 (a)  $4e^{j4\pi f}$  (b)  $2e^{-j8\pi f}$  (c)  $4e^{-j4\pi f}$  (d)  $2e^{j8\pi f}$
23. A sequence  $x(n)$  with the z-transform  $X(z) = z^4 + z^2 - 2z + 2 - 3z^{-4}$  is applied as an input to a linear, time-invariant system with the impulse response  $h(n) = 2\delta(n-3)$  where  

$$\delta(n) = \begin{cases} 1, n = 0 \\ 0, \text{ otherwise} \end{cases}$$
  
 The output at  $n = 4$  is  
 (a) -6 (b) zero (c) 2 (d) -4
24. Figure shows the Nyquist plot of the open-loop transfer function  $G(s)H(s)$  of a system. If  $G(s)H(s)$  has one right hand pole, the closed loop system is




- (a) always stable  
 (b) unstable with one closed loop right hand pole  
 (c) unstable with two closed loop right hand poles  
 (d) unstable with three closed loop right hand poles

25. A PD controller is used to compensate a system. Compared to the uncompensated system, the compensated system has  
 (a) a higher type number (b) reduced damping  
 (c) higher noise amplification (d) larger transient overshoot
26. The input to a coherent detector is DSB-SC signal plus noise. The noise at the detector output is  
 (a) the in-phase component (b) the quadrature-component  
 (c) zero (d) the envelope
27. The noise at the input to an ideal frequency detector is white. The detector is operating above threshold. The power spectral density of the noise at the output is  
 (a) raised cosine (b) flat (c) parabolic (d) Gaussian
28. At a given probability of error, binary coherent FSK is inferior to binary coherent PSK by  
 (a) 6 dB (b) 3 dB (c) 2 dB (d) 0 dB
29. The unit of  $\nabla \times H$  is  
 (a) Ampere (b) Ampere/meter  
 (c) Ampere/meter<sup>2</sup> (d) Ampere-meter
30. The depth of penetration of electromagnetic wave in a medium having conductivity  $\sigma$  at a frequency of 1 MHz is 25 cm. The depth of penetration at a frequency of 4 MHz will be  
 (a) 6.25 cm (b) 12.50 cm (c) 50.00 cm (d) 100.00 cm


**Q.31 – Q.90 Carry Two Marks Each**

31. Twelve  $1\Omega$  resistances are used as edges to form a cube. The resistance between two diagonally opposite corners of the cube is  
 (a)  $\frac{5}{6}\Omega$  (b)  $\frac{1}{6}\Omega$  (c)  $\frac{6}{5}\Omega$  (d)  $\frac{3}{2}\Omega$
32. The current flowing through the resistance R in the circuit in figure has the form  $P \cos 4t$ , where P is

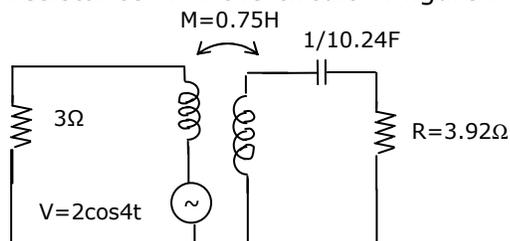- (a)  $(0.18+j0.72)$   
 (b)  $(0.46+j1.90)$   
 (c)  $-(0.18+j1.90)$   
 (d)  $-(0.192+j0.144)$



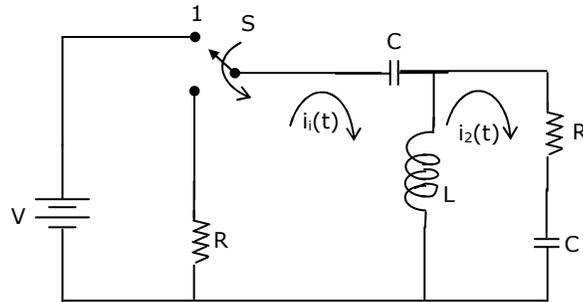The circuit for **Q.33-34** is given in figure. For both the questions, assume that the switch S is in position 1 for a long time and thrown to position 2 at  $t = 0$ .



33. At  $t = 0^+$ , the current  $i_1$  is
- (a)  $\frac{-V}{2R}$                       (b)  $\frac{-V}{R}$                       (c)  $\frac{-V}{4R}$                       (d) zero
34.  $I_1(s)$  and  $I_2(s)$  are the Laplace transforms of  $i_1(t)$  and  $i_2(t)$  respectively. The equations for the loop currents  $I_1(s)$  and  $I_2(s)$  for the circuit shown in figure Q.33-34, after the switch is brought from position 1 to position 2 at  $t = 0$ , are

(a) 
$$\begin{bmatrix} R + Ls + \frac{1}{Cs} & -Ls \\ -Ls & R + \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} \frac{V}{s} \\ 0 \end{bmatrix}$$

(b) 
$$\begin{bmatrix} R + Ls + \frac{1}{Cs} & -Ls \\ -Ls & R + \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} -\frac{V}{s} \\ 0 \end{bmatrix}$$

(c) 
$$\begin{bmatrix} R + Ls + \frac{1}{Cs} & -Ls \\ -Ls & R + Ls + \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} \frac{V}{s} \\ 0 \end{bmatrix}$$


(d) 
$$\begin{bmatrix} R + Ls + \frac{1}{Cs} & -Ls \\ -Ls & R + Ls + \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} -\frac{V}{s} \\ 0 \end{bmatrix}$$

35. An input voltage  $v(t) = 10\sqrt{2} \cos(t + 10^\circ) + 10\sqrt{3} \cos(2t + 10^\circ)V$  is applied to a series combination of resistance  $R = 1\Omega$  and an inductance  $L = 1H$ . The resulting steady state current  $i(t)$  in ampere is
-

- (a)  $10 \cos(t + 55^\circ) + 10 \cos(2t + 10^\circ + \tan^{-1} 2)$   
 (b)  $10 \cos(t + 55^\circ) + 10\sqrt{\frac{3}{2}} \cos(2t + 55^\circ)$   
 (c)  $10 \cos(t - 35^\circ) + 10 \cos(2t + 10^\circ - \tan^{-1} 2)$   
 (d)  $10 \cos(t - 35^\circ) + 10\sqrt{\frac{3}{2}} \cos(2t - 35^\circ)$


36. The driving point impedance  $Z(s)$  of a network has the pole-zero locations as shown in figure. If  $Z(0) = 3$ , then  $Z(s)$  is

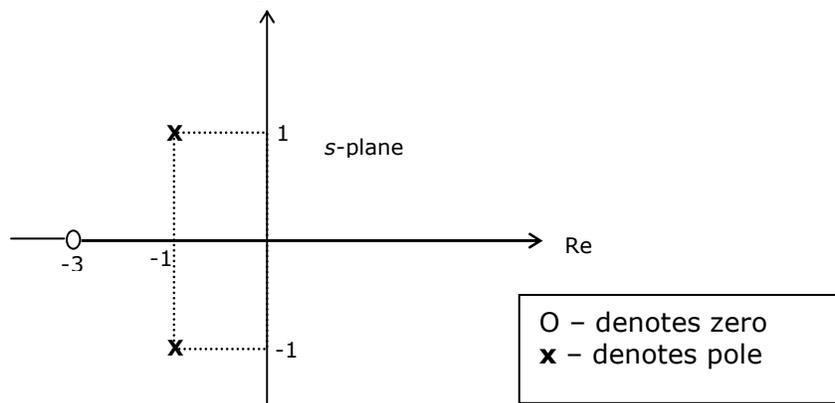- (a)  $\frac{3(s+3)}{s^2+2s+3}$   
 (b)  $\frac{2(s+3)}{s^2+2s+2}$   
 (c)  $\frac{3(s-3)}{s^2-2s-2}$   
 (d)  $\frac{2(s-3)}{s^2-2s-3}$



37. The impedance parameters  $Z_{11}$  and  $Z_{12}$  of the two-port network in figure are

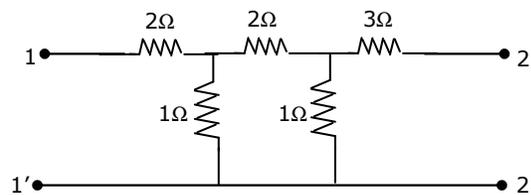- (a)  $Z_{11} = 2.75\Omega$  and  $Z_{12} = 0.25\Omega$   
 (b)  $Z_{11} = 3\Omega$  and  $Z_{12} = 0.5\Omega$   
 (c)  $Z_{11} = 3\Omega$  and  $Z_{12} = 0.25\Omega$   
 (d)  $Z_{11} = 2.25\Omega$  and  $Z_{12} = 0.5\Omega$



38. An  $n$ -type silicon bar 0.1 cm long and  $\mu\text{m}^2$  in cross-sectional area has a majority carrier concentration of  $5 \times 10^{20}/\text{m}^3$  and the carrier mobility is  $0.13\text{m}^2/\text{V}\cdot\text{s}$  at 300K. if the charge of an electron is  $1.6 \times 10^{-19}$  coulomb, then the resistance of the bar is

- (a)  $10^6$  ohm      (b)  $10^4$  ohm      (c)  $10^{-1}$  ohm      (d)  $10^{-4}$  ohm

39. The electron concentration in a sample of uniformly doped  $n$ -type silicon at 300 K varies linearly from  $10^{17}/\text{cm}^3$  at  $x = 0$  to  $6 \times 10^{16}/\text{cm}^3$  at  $x = 2\mu\text{m}$ . Assume a situation that electrons are supplied to keep this concentration gradient constant with time. If electronic charge is  $1.6 \times 10^{-19}$  coulomb and the diffusion constant  $D_n = 35 \text{ cm}^2/\text{s}$ , the current density in the silicon, if no electric field is present, is

- (a) zero      (b)  $-112 \text{ A}/\text{cm}^2$   
 (c)  $+1120 \text{ A}/\text{cm}^2$       (d)  $-1112 \text{ A}/\text{cm}^2$

40. Match items in Group 1 with items in Group 2, most suitably.

<b>Group 1</b>		<b>Group 2</b>	
P	LED	1	Heavy doping
Q	Avalanche photodiode	2	Coherent radiation
R	Tunnel diode	3	Spontaneous emission
S	LASER	4	Current gain

- (a) P – 1 Q – 2 R – 4 S – 3                      (b) P – 2 Q – 3 R – 1 S – 4  
(c) P – 3 Q – 4 R – 1 S – 2                      (d) P – 2 Q – 1 R – 4 S – 3

41. At 300 K, for a diode current of 1 mA, a certain germanium diode requires a forward bias of 0.1435V, whereas a certain silicon diode requires a forward bias of 0.718V. Under the conditions stated above, the closest approximation of the ratio of reverse saturation current in germanium diode to that in silicon diode is

- (a) 1                      (b) 5                      (c)  $4 \times 10^3$                       (d)  $8 \times 10^3$

42. A particular green LED emits light of wavelength 5490Å. The energy bandgap of the semiconductor material used there is (Planck's constant =  $6.626 \times 10^{-34}$ J-s)

- (a) 2.26 eV                      (b) 1.98 eV                      (c) 1.17 eV                      (d) 0.74 eV

43. When the gate-to-source voltage ( $V_{GS}$ ) of a MOSFET with threshold voltage of 400mV, working in saturation is 900 mV, the drain current is observed to be 1 mA. Neglecting the channel width modulation effect and assuming that the MOSFET is operating at saturation, the drain current for an applied  $V_{GS}$  of 1400 mV is

- (a) 0.5 mA                      (b) 2.0 mA                      (c) 3.5 mA                      (d) 4.0 mA

44. If P is Passivation, Q is n-well implant, R is metallization and S is source/drain diffusion, then the order in which they are carried out in a standard n-well CMOS fabrication process, is


- (a) P-Q-R-S                      (b) Q-S-R-P                      (c) R-P-S-Q                      (d) S-R-Q-P

45. An amplifier without feedback has a voltage gain of 50, input resistance of 1 KΩ and output resistance of 2.5 KΩ. The input resistance of the current-shunt negative feedback amplifier using the above amplifier with a feedback factor of 0.2, is


- (a)  $\frac{1}{11} K\Omega$                       (b)  $\frac{1}{5} K\Omega$                       (c) 5 KΩ                      (d) 11 KΩ

46. In the amplifier circuit shown in figure, the values of  $R_1$  and  $R_2$  are such that the transistor is operating at  $V_{CE} = 3V$  and  $I_C = 1.5mA$  when its  $\beta$  is 150. For a transistor with  $\beta$  of 200, the operating point ( $V_{CE}, I_C$ ) is

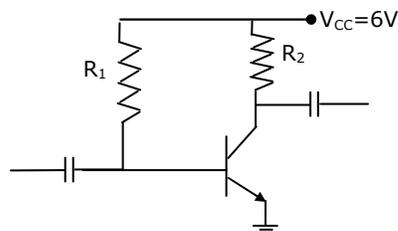- (a) (2V, 2 mA)  
 (b) (3V, 2 mA)  
 (c) (4V, 2 mA)  
 (d) (4V, 1 mA)




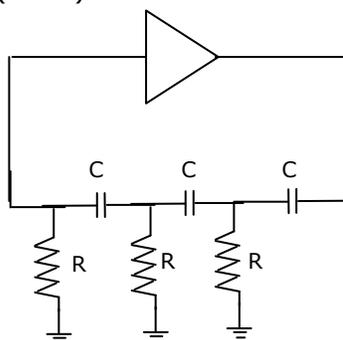47. The oscillator circuit shown in figure has an ideal inverting amplifier. Its frequency of oscillation (in Hz) is



- (a)  $\frac{1}{(2\pi\sqrt{6}RC)}$       (b)  $\frac{1}{(2\pi RC)}$       (c)  $\frac{1}{(\sqrt{6}RC)}$       (d)  $\frac{\sqrt{6}}{(2\pi RC)}$

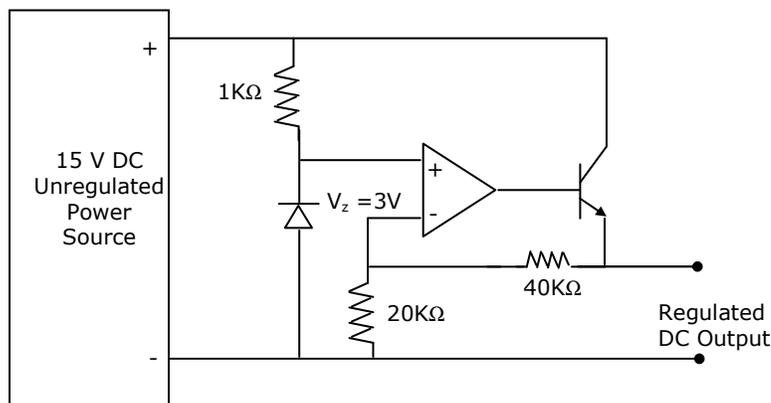
48. The output voltage of the regulated power supply shown in figure is



- (a) 3V      (b) 6V      (c) 9V      (d) 12V

49. The action of a JFET in its equivalent circuit can best be represented as a
- (a) Current Controlled Current Source
  - (b) Current Controlled Voltage Source
  - (c) Voltage Controlled Voltage Source
  - (d) Voltage Controlled Current Source

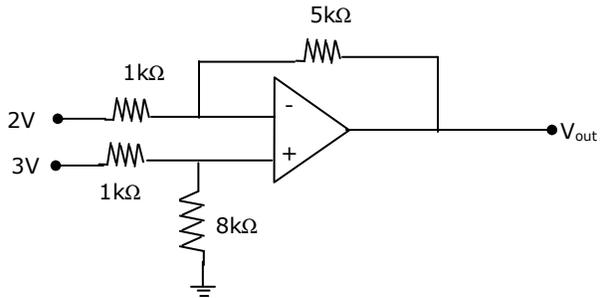50. If the op-amp in figure is ideal, the output voltage  $V_{out}$  will be equal to



- (a) 1V
- (b) 6V
- (c) 14V
- (d) 17V

51. Three identical amplifiers with each one having a voltage gain of 50, input resistance of  $1\text{ K}\Omega$  and output resistance of  $250\Omega$ , are cascaded. The open circuit voltage gain of the combined amplifier is

- (a) 49 dB
- (b) 51 dB
- (c) 98 dB
- (d) 102 dB


52. An ideal sawtooth voltage waveform of frequency 500 Hz and amplitude 3V is generated by charging a capacitor of  $2\ \mu\text{F}$  in every cycle. The charging requires

- (a) constant voltage source of 3 V for 1 ms
- (b) constant voltage source of 3 V for 2 ms
- (c) constant current source of 3 mA for 1 ms
- (d) constant current source of 3 mA for 2 ms

53. The circuit shown in figure has 4 boxes each described by inputs P, Q, R and outputs Y, Z with

$$Y = P \oplus Q \oplus R$$

$$Z = RQ + \bar{P}R + Q\bar{P}$$

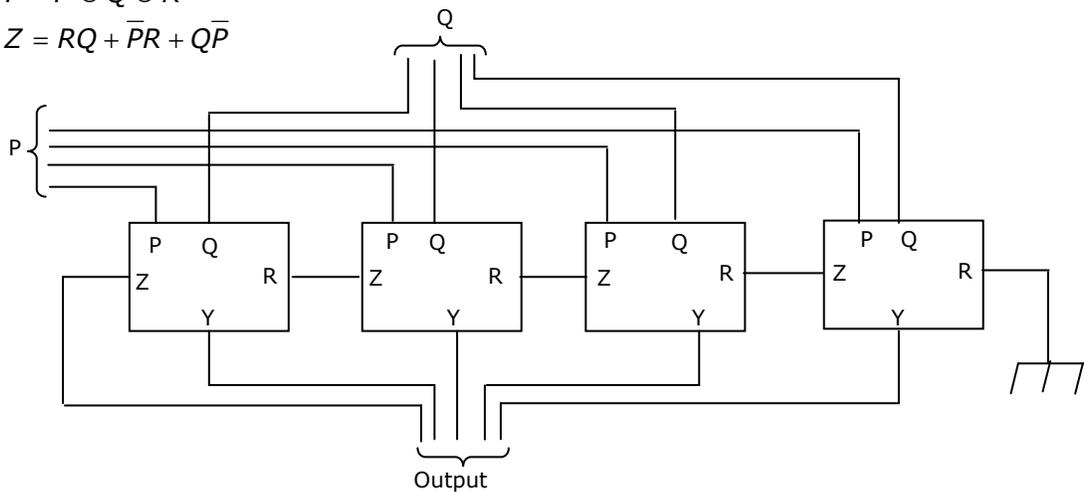







Data for **Q.65 - 66** are given below. Solve the problems and choose the correct answers.

$X(t)$  is a random process with a constant mean value of 2 and the autocorrelation function  $R_x(\tau) = 4[e^{-0.2|\tau|} + 1]$ .

65. Let  $X$  be the Gaussian random variable obtained by sampling the process at  $t = t_i$  and let  $Q(\alpha) = \int_{\alpha}^{\infty} \frac{1}{\sqrt{2\pi}} e^{-\frac{y^2}{2}} dy$ .


The probability that  $[x \leq 1]$  is

- (a)  $1 - Q(0.5)$       (b)  $Q(0.5)$       (c)  $Q\left(\frac{1}{2\sqrt{2}}\right)$       (d)  $1 - Q\left(\frac{1}{2\sqrt{2}}\right)$

66. Let  $Y$  and  $Z$  be the random variables obtained by sampling  $X(t)$  at  $t = 2$  and  $t = 4$  respectively. Let  $W = Y - Z$ . The variance of  $W$  is


- (a) 13.36      (b) 9.36      (c) 2.64      (d) 8.00

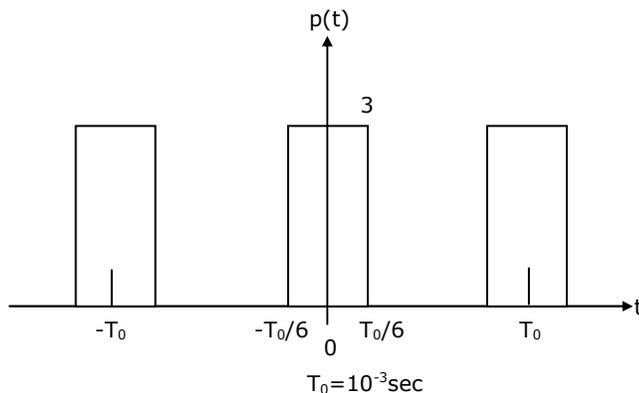67. Let  $x(t) = 2\cos(800\pi t) + \cos(1400\pi t)$ .  $x(t)$  is sampled with the rectangular pulse train shown in figure. The only spectral components (in kHz) present in the sampled signal in the frequency range 2.5 kHz to 3.5 kHz are



- (a) 2.7, 3.4      (b) 3.3, 3.6  
(c) 2.6, 2.7, 3.3, 3.4, 3.6      (d) 2.7, 3.3

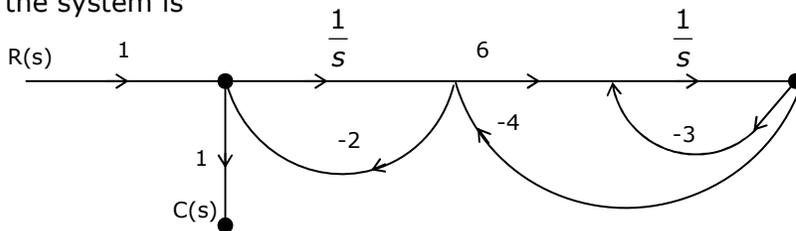68. The signal flow graph of a system is shown in figure. The transfer function  $\frac{C(s)}{R(s)}$  of the system is




(a)  $\frac{6}{s^2 + 29s + 6}$       (b)  $\frac{6s}{s^2 + 29s + 6}$       (c)  $\frac{s(s+2)}{s^2 + 29s + 6}$       (d)  $\frac{s(s+27)}{s^2 + 29s + 6}$

69. The root locus of the system  $G(s)H(s) = \frac{K}{s(s+2)(s+3)}$  has the break-away point

located at

- (a) (-0.5,0)      (b) (-2.548,0)      (c) (-4,0)      (d) (-0.784,0)


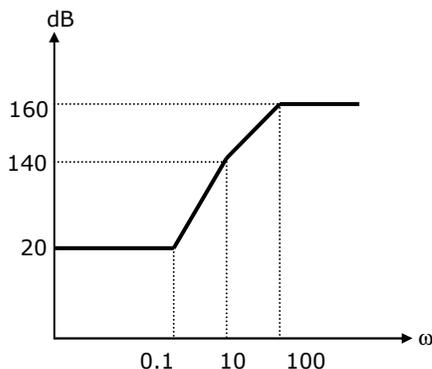
70. The approximate Bode magnitude plot of a minimum-phase system is shown in figure. The transfer function of the system is





(a)  $10^8 \frac{(s+0.1)^3}{(s+10)^2 (s+100)}$       (b)  $10^7 \frac{(s+0.1)^3}{(s+10)(s+100)}$   
 (c)  $10^8 \frac{(s+0.1)^2}{(s+10)^2 (s+100)}$       (d)  $10^9 \frac{(s+0.1)^3}{(s+10)(s+100)^2}$

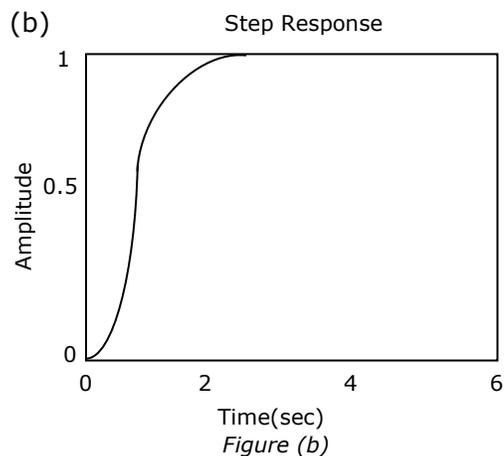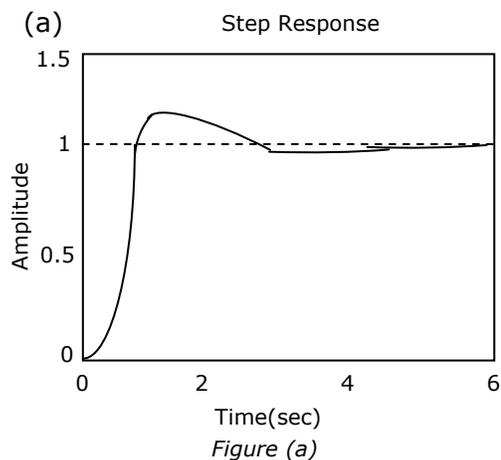71. A second-order system has the transfer function  $\frac{C(s)}{R(s)} = \frac{4}{s^2 + 4s + 4}$ .

with  $r(t)$  as the unit-step function, the response  $c(t)$  of the system is represented by



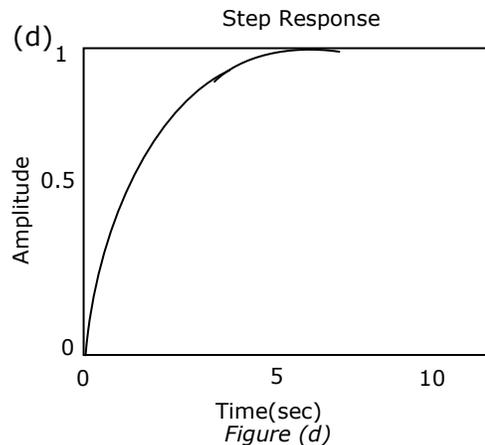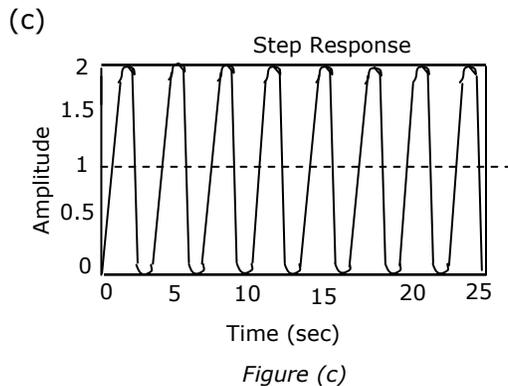

- (a) Figure (a)      (b) Figure (b)      (c) Figure (c)      (d) Figure (d)

72. The gain margin and the phase margin of a feedback system with  $G(s)H(s) = \frac{s}{(s+100)^3}$  are
- (a) 0 dB,  $0^\circ$       (b)  $\infty$ ,  $\infty$       (c)  $\infty$ ,  $0^\circ$       (d) 88.5 dB,  $\infty$

73. The zero-input response of a system given by the state-space equation

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} \text{ and } \begin{bmatrix} x_1(0) \\ x_2(0) \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} \text{ is}$$

- (a)  $\begin{bmatrix} te^t \\ t \end{bmatrix}$       (b)  $\begin{bmatrix} e^t \\ t \end{bmatrix}$       (c)  $\begin{bmatrix} e^t \\ te^t \end{bmatrix}$       (d)  $\begin{bmatrix} t \\ te^t \end{bmatrix}$

74. A DSB-SC signal is to be generated with a carrier frequency  $f_c = 1\text{MHz}$  using a nonlinear device with the input-output characteristic

$$v_o = a_0 v_i + a_1 v_i^3$$

where  $a_0$  and  $a_1$  are constants. The output of the nonlinear device can be filtered by an appropriate band-pass filter.

Let  $v_i = A_c' \cos(2\pi f_c' t) + m(t)$  where  $m(t)$  is the message signal. Then the value of  $f_c'$  (in MHz) is

- (a) 1.0      (b) 0.333      (c) 0.5      (d) 3.0

The data for **Q.75 – 76** are given below. Solve the problems and choose the correct answers.

Let  $m(t) = \cos\left[(4\pi \times 10^3)t\right]$  be the message signal and  $c(t) = 5 \cos\left[(2\pi \times 10^6)t\right]$  be the carrier.

75.  $c(t)$  and  $m(t)$  are used to generate an AM signal. The modulation index of the generated AM signal is 0.5. Then the quantity  $\frac{\text{Total sideband power}}{\text{Carrier power}}$  is

- (a)  $\frac{1}{2}$                       (b)  $\frac{1}{4}$                       (c)  $\frac{1}{3}$                       (d)  $\frac{1}{8}$

76.  $c(t)$  and  $m(t)$  are used to generate an FM signal. If the peak frequency deviation of the generated FM signal is three times the transmission bandwidth of the AM signal, then the coefficient of the term  $\cos\left[2\pi(1008 \times 10^3)t\right]$  in the FM signal (in terms of the Bessel coefficients) is

- (a)  $5J_4(3)$                       (b)  $\frac{5}{2}J_8(3)$                       (c)  $\frac{5}{2}J_8(4)$                       (d)  $5J_4(6)$

77. Choose the correct one from among the alternatives A, B, C, D after matching an item in Group 1 with the most appropriate item in Group 2.

**Group 1**

- P Ring modulator  
Q VCO  
R Foster-Seely discriminator  
S Mixer

**Group 2**

- 1 Clock recovery  
2 Demodulation of FM  
3 Frequency conversion  
4 Summing the two inputs  
5 Generation of FM  
6 Generation of DSB-Sc


- (a) P – 1 Q – 3 R – 2 S – 4                      (b) P – 6 Q – 5 R – 2 S – 3  
(c) P – 6 Q – 1 R – 3 S – 2                      (d) P – 5 Q – 6 R – 1 S – 3

78. A superheterodyne receiver is to operate in the frequency range 550 kHz – 1650 kHz, with the intermediate frequency of 450 kHz. Let  $R = \frac{C_{\max}}{C_{\min}}$  denote the required capacitance ratio of the local oscillator and I denote the image frequency (in kHz) of the incoming signal. If the receiver is tuned to 700 kHz, then

- (a)  $R = 4.41, I = 1600$                       (b)  $R = 2.10, I = 1150$   
(c)  $R = 3.0, I = 1600$                       (d)  $R = 9.0, I = 1150$
-


79. A sinusoidal signal with peak-to-peak amplitude of 1.536 V is quantized into 128 levels using a mid-rise uniform quantizer. The quantization noise power is  
(a) 0.768 V                      (b)  $48 \times 10^{-6} \text{V}^2$                       (c)  $12 \times 10^{-6} \text{V}^2$                       (d) 3.072 V
80. If  $E_b$ , the energy per bit of a binary digital signal, is  $10^{-6}$  watt-sec and the one-sided power spectral density of the white noise,  $N_0 = 10^{-5}$  W/Hz, then the output SNR of the matched filter is  
(a) 26 dB                      (b) 10 dB                      (c) 20 dB                      (d) 13 dB
81. The input to a linear delta modulator having a step-size  $\Delta = 0.628$  is a sine wave with frequency  $f_m$  and peak amplitude  $E_m$ . If the sampling frequency  $f_s = 40$  kHz, the combination of the sine-wave frequency and the peak amplitude, where slope overload will take place is
- | $E_m$     | $f_m$ |
|-----------|-------|
| (a) 0.3 V | 8 kHz |
| (b) 1.5 V | 4 kHz |
| (c) 1.5 V | 2 kHz |
| (d) 3.0 V | 1 kHz |
82. If  $S$  represents the carrier synchronization at the receiver and  $\rho$  represents the bandwidth efficiency, then the correct statement for the coherent binary PSK is  
(a)  $\rho = 0.5$ ,  $S$  is required                      (b)  $\rho = 1.0$ ,  $S$  is required  
(c)  $\rho = 0.5$ ,  $S$  is not required                      (d)  $\rho = 1.0$ ,  $S$  is not required
83. A signal is sampled at 8 kHz and is quantized using 8-bit uniform quantizer. Assuming  $\text{SNR}_q$  for a sinusoidal signal, the correct statement for PCM signal with a bit rate of  $R$  is  
(a)  $R = 32$  kbps,  $\text{SNR}_q = 25.8$  dB                      (b)  $R = 64$  kbps,  $\text{SNR}_q = 49.8$  dB  
(c)  $R = 64$  kbps,  $\text{SNR}_q = 55.8$  dB                      (d)  $R = 32$  kbps,  $\text{SNR}_q = 49.8$  dB
84. Medium 1 has the electrical permittivity  $\epsilon_1 = 1.5 \epsilon_0$  farad/m and occupies the region to the left of  $x = 0$  plane. Medium 2 has the electrical permittivity  $\epsilon_2 = 2.5 \epsilon_0$  farad/m and occupies the region to the right of  $x = 0$  plane. If  $E_1$  in medium 1 is  $E_1 = (2u_x - 3u_y + 1u_z)$  volt/m, then  $E_2$  in medium 2 is  
(a)  $(2.0u_x - 7.5u_y + 2.5u_z)$  volt/m                      (b)  $(2.0u_x - 2.0u_y + 0.6u_z)$  volt/m  
(c)  $(1.2u_x - 3.0u_y + 1.0u_z)$  volt/m                      (d)  $(1.2u_x - 2.0u_y + 0.6u_z)$  volt/m
85. If the electric field intensity is given by  $E = (xu_x + yu_y + zu_z)$  volt/m, the potential difference between  $X(20,0)$  and  $Y(1,2,3)$  is
-

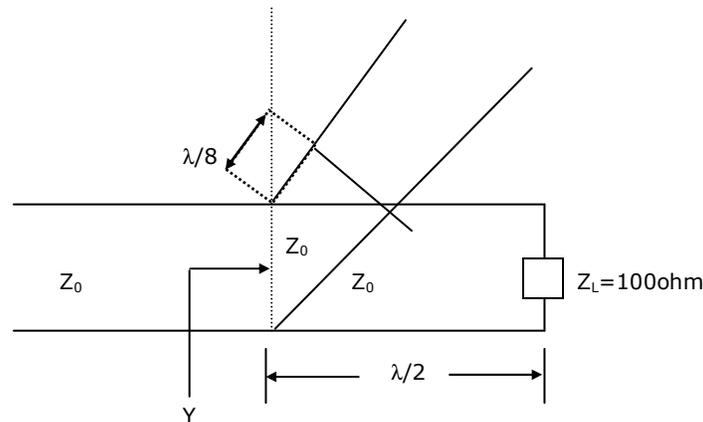- (a) +1 volt                      (b) -1 volt                      (c) +5 volt                      (d) +6 volt
86. A uniform plane wave traveling in air is incident on the plane boundary between air and another dielectric medium with  $\epsilon_r = 4$ . The reflection coefficient for the normal incidence, is  
 (a) zero                      (b)  $0.5\angle 180^\circ$                       (c)  $0.333\angle 0^\circ$                       (d)  $0.333\angle 180^\circ$
87. If the electric field intensity associated with a uniform plane electromagnetic wave traveling in a perfect dielectric medium is give by  
 $E(z,t) = 10 \cos(2\pi \times 10^7 t - 0.1\pi z)$  volt/m, then the velocity of the traveling wave is  
 (a)  $3.00 \times 10^8$  m/sec                      (b)  $2.00 \times 10^8$  m/sec  
 (c)  $6.28 \times 10^7$  m/sec                      (d)  $2.00 \times 10^7$  m/sec
88. A short-circuited stub is shunt connected to a transmission line as shown in Figure. If  $Z_0 = 50$  ohm, the admittance  $Y$  seen at the junction of the stub and the transmission line is



- (a)  $(0.01 - j0.02)$  ohm                      (b)  $(0.02 - j0.01)$  ohm  
 (c)  $(0.04 - j0.02)$  ohm                      (d)  $(0.02 + j0)$  ohm
89. A rectangular metal wave-guide filled with a dielectric material of relative permittivity  $\epsilon_r = 4$  has the inside dimensions  $3.0\text{cm} \times 1.2\text{cm}$ . The cut-off frequency for the dominant mode is  
 (a) 2.5 GHz                      (b) 5.0 GHz                      (c) 10.0 GHz                      (d) 12.5 GHz

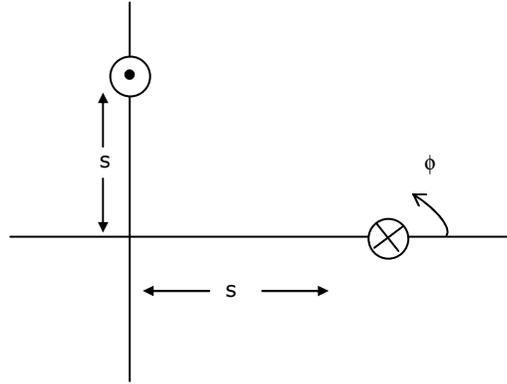90. Two identical antennas are placed in the  $\theta = \frac{\pi}{2}$  plane as shown in figure. The elements have equal amplitude excitation with  $180^\circ$  polarity difference, operating at wavelength  $\lambda$ . The correct value of the magnitude of the far-zone resultant electric field strength normalized with that of a single element, both computed for  $\phi = 0$ , is



- (a)  $2 \cos\left(\frac{2\pi s}{\lambda}\right)$       (b)  $2 \sin\left(\frac{2\pi s}{\lambda}\right)$       (c)  $2 \cos\left(\frac{\pi s}{\lambda}\right)$       (d)  $2 \sin\left(\frac{\pi s}{\lambda}\right)$