

$$1. (c) \frac{d^2y}{dt^2} + \left(\frac{dy}{dt}\right)^2 = y^4 = a^{-4}$$

Order = 2

∴ Highest derivative is $\frac{d^2y}{dt^2}$.

2. (a) Alternative (x) is correct choice.

3. (b) Given function, $f(t) = \sin^2 t + \cos 2t$

or $f(t) = \sin^2 t + 2 \cos^2 t - 1$

or $f(t) = \sin^2 t + \cos^2 t + \cos^2 t - 1$

or $f(t) = 1 + \cos^2 t - 1$

or $f(t) = \cos^2 t$

or $f(t) = \frac{\cos 2t + 1}{2}$


or $f(t) = \frac{1}{2} \cos 2t + \frac{1}{2}$

$$\begin{array}{cc} \downarrow & \downarrow \\ f = \frac{1}{\omega} & f = 0 \end{array}$$

Therefore, f has frequency components at 0 and $\frac{1}{\pi}$ Hz.

Hence alternative (b) is the correct choice.

4. (c) Given current = 2A

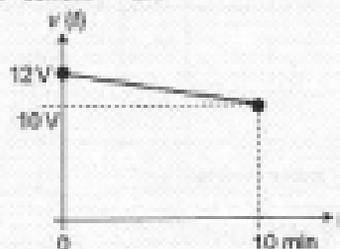

$$\begin{aligned} \text{Energy} &= \int_0^{10 \times 60} V(t) I(t) dt \\ &= \int_0^{10 \times 60} 2 V(t) dt \end{aligned}$$

$$V(t) = \frac{12 - 10}{-10 \times 60} (t - 600) + 10$$

$$= 2 \int_0^{600} -\frac{2}{600} (t - 600) + 10 dt \dots (1)$$

After solving this equation we get

$$\text{Energy} = 13200 \text{ J}$$

$$= 13.2 \text{ kJ}$$

5. (c) The concentration of dopant atoms in an n -type silicon crystal is $4 \times 10^{19} \text{ cm}^{-3}$.

6. (c) Full form of TTL and CMOS in reference to logic families are :

TTL → Transistor Transistor Logic

CMOS → Complementary Metal Oxide Semiconductor

7. (a) The given discrete time sequence

$$x(n) = \left(\frac{1}{3}\right)^n u(n) - \left(\frac{1}{2}\right)^n u[-n-1]$$

$$\text{For the term } \left(\frac{1}{3}\right)^n u(n) \leftrightarrow \frac{1}{1 - \frac{1}{3} z^{-1}}$$

$$\text{ROC } \left| \frac{z^{-1}}{3} \right| < 1 \text{ or } |z| > \frac{1}{3}$$

$$\text{for the term } \left(\frac{1}{2}\right)^n u[-n-1] \leftrightarrow \frac{1}{1 - \frac{1}{2} z^{-1}}$$

$$\text{ROC } \left| \frac{z^{-1}}{2} \right| > 1 \text{ or } |z| < 2$$

Hence the ROC of the given discrete sequence is

$$\frac{1}{2} < |z| < 2$$


Hence alternative (a) is the correct choice.

8. (d) The given magnitude plot



The above figure represents lead-lag compensator.

9. (c) The given response

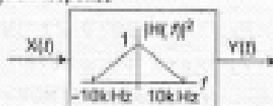

Given, $X(t) = 1 \times 10^{-10}$ W/Hz

$$|H(f)|^2 = 1$$

$$Y(t) = ?$$

We know that,

$$\begin{aligned} Y(t) &= 2\pi \int |H(f)|^2 \times f \, df \\ &= 2\pi \int |H(f)|^2 \cdot 1 \times 10^{-10} \, df \\ &= 1 \times 10^{-10} \times 2\pi \int_0^{10^4} 1 \, df \\ &= 2\pi \times 10^{-10} = \frac{2\pi^2}{2\pi} = 10^{-9} \text{ W} \end{aligned}$$

10. (a) The given metallic waveguides



P : Coaxial



Q : Cylindrical



R : Rectangular

coaxial waveguide has no cut-off frequency.

11. (d) Probability of getting head = $\frac{1}{2}$

$$\text{Probability of getting tail} = \frac{1}{2}$$

$$n = 10$$


$$\text{Number of success} = 2$$

Probability of getting head in only first 2 tosses

$$\begin{aligned} &= {}^{10}C_2 \left(\frac{1}{2}\right)^2 \left(\frac{1}{2}\right)^8 \\ &= {}^{10}C_2 \left(\frac{1}{2}\right)^{10} \end{aligned}$$

Option (d) is correct.

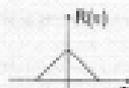12. (b) If the power spectral density of stationary random process is a sinc squared function of frequency then the shape of its auto correlation will be triangular as shown in option (b).



13. (d) $f(z) = c_0 + c_1 z^{-1} + F(z) = \frac{-5z}{z^2}$

$$\oint \frac{1+f(z)}{z} dz \quad c: |z| = 1$$

Poles at $z = 0$

By Cauchy's integral formula

$$\oint \frac{F(z)}{z-0} dz = 2\pi i F'(0)$$

Here

$$F(z) = 1 + f(z), F'(z) = f'(z)$$

$$\begin{aligned} \oint \frac{1+f(z)}{z} dz &= 2\pi i f'(0) \\ &= 2\pi i (1 + c_1) \end{aligned}$$

Hence alternative (d) is the correct choice.

14. (a) The given figure



Given that 60V source is absorbing power, it means current enters in the 60V source. Let the current enter in 60V source is I_B .

KCL at point B, we get

$$I + I_B = 12 \quad \dots(i)$$

Now, this problem is further solved by applying Hit and trial method. From the given options, we conclude that only alternative (a) satisfy the equation (i).


15. (a) From the Einstein relation

$$\begin{aligned} \frac{D_p}{\mu_p} &= \frac{D_n}{\mu_n} \\ &= \frac{kT}{q} \\ &= V_T = 26mV \end{aligned}$$

The ratio of mobility to the diffusion constant is $\frac{1}{V_T}$ or V_T^{-1} .

16. (d) INTR is internally generated interrupt. This interrupt is maskable and vectored. This interrupt can be delayed or rejected.

17. (c) The given network

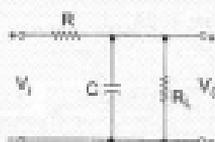

The given transfer function

$$\frac{V_2(s)}{V_1(s)} = \frac{1}{2 + sCR} \quad \dots(ii)$$

From given network

$$V_o(s) = V_i(s) \frac{R_L \parallel \frac{1}{Cs}}{R + R_L \parallel \frac{1}{Cs}}$$

or

$$\frac{V_o(s)}{V_i(s)} = \frac{R_L}{R + R_L + R_L Cs}$$

$$= \frac{1}{\frac{R + R_L}{R_L} + RCs}$$

On comparing equation (i) and (ii) we get

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{\frac{R + R_L}{R_L} + RCs}$$

$$\frac{R + R_L}{R_L} = 2$$

$$R + R_L = 2R_L$$

$$\boxed{R_L = R}$$

Hence alternative (c) is the correct choice.

18. (c) Given $A = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$

and $B = \begin{bmatrix} p \\ q \end{bmatrix}$

For controllability, $C = [B : AB]$

$$AB = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} p \\ q \end{bmatrix}$$

$$= \begin{bmatrix} p \\ q \end{bmatrix}$$

Then $C = \begin{bmatrix} p & p \\ q & q \end{bmatrix}$

Rank of C \neq Rank of A hence system is uncontrollable.

Hence alternative (c) is the correct choice.

19. (c) The given message signal

$$m(t) = \cos(2\pi f_m t)$$

frequency of carrier signal
= f_c

Let $c(t) = \cos(2\pi f_c t)$

Now, DSB-SC modulated signal

$$s(t) = m(t)c(t)$$

or $s(t) = \cos(2\pi f_m t) \cos(2\pi f_c t)$

or $s(t) = \frac{1}{2} [\cos 2\pi (f_m + f_c)t + \cos 2\pi (f_m - f_c)t]$

The single side-band (SSB) signal is given by

$$s(t) = \frac{1}{2} \cos [2\pi (f_m + f_c)t]$$

or $s(t) = \cos [2\pi (f_c + f_m)t]$

20. (d) 21. (c)

22. (d) $f(x) = \frac{\sin x}{x}$ at $x = \pi$

$$\sin x = \sin(\pi - x) = -\sin(x - \pi)$$

$$= -f(x) = -\frac{\sin(x - \pi)}{x - \pi}$$

$$= -\frac{1}{x - \pi} \left[(x - \pi) - \frac{(x - \pi)^2}{2!} + \frac{(x - \pi)^3}{3!} - \dots \right]$$

$$f(x) = -1 + \frac{(x - \pi)^2}{2!} - \frac{(x - \pi)^4}{4!} + \dots$$

... (i) Option (d) is correct.

23. (b) $\vec{\nabla} = \nabla \times \vec{A}$

From Stokes theorem

$$\int_C \vec{F} \cdot d\vec{r} = \int_A (\nabla \times \vec{F}) \cdot d\vec{S}$$

So, we have $\oint_C \vec{A} \cdot d\vec{r} = \iint_{S_C} \vec{\nabla} \cdot \vec{A} \cdot d\vec{S}$

Option (b) is correct.

24. (b) $F(x) = L\{f(t)\}$

$$L\left\{\int_0^t f(t) dt\right\} = \frac{F(s)}{s}$$

Option (b) is correct choice.

25. (a) P. $\frac{dy}{dx} = \frac{y}{x}$

$$\Rightarrow \int \frac{1}{y} dy = \int \frac{1}{x} dx$$

$$\log y = \log xc$$

$$y = xc$$

i.e. Straight line

Q. $\frac{dy}{dx} = -\frac{y}{x}$

$$\log y = -\log x + \log c$$

$$\log y = \log cx$$

$$y = \frac{c}{x}$$

$$\Rightarrow xy = c$$

i.e. Hyperbola

R. $\frac{dy}{dx} = \frac{x}{y}$

or $y dy = x dx$

$$\Rightarrow y^2 = x^2 + c$$

i.e. Hyperbola

S. $\frac{dy}{dx} = -\frac{x}{y}$

$$\Rightarrow y^2 = x^2 + c$$

i.e. Circles

P - 2, Q - 3, R - 3, S - 1

Hence alternative (a) is the correct choice.

26. (d) $A = \begin{bmatrix} -1 & 3 & 8 \\ -3 & -1 & 6 \\ 0 & 0 & 3 \end{bmatrix}$

$$\text{trace } A = -1 + (-1) + 3 = 1$$

$$|A| = 3(1 + 9) = 30$$


\therefore Sum of eigen values = trace A.

For option (d), sum of eigen values

$$= 3 - 1 + 3j - 1 - 3j = 1$$

So option (d) is correct choice.

27. (b) The given circuit

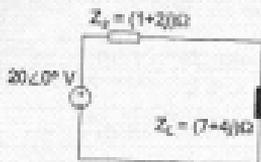

Given,

$$V = 20 \text{ V}_{\text{rms}}$$

$$Z_T = (1+2j) \Omega$$

$$Z_L = (7+4j) \Omega$$

$P_{\text{Reactive (Load)}} = ?$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z_{\text{eq}}}$$

$$= \frac{V_{\text{rms}}}{Z_T + Z_L}$$

or

$$I_{\text{rms}} = \frac{20\text{V}}{1+2j+7+4j}$$

$$= \frac{20}{8+6j}$$

$$= \frac{20}{\sqrt{8^2+6^2}}$$


$$= \frac{20}{10} = 2 \text{ Amp.}$$

Now, $P_{\text{Reactive (Load)}} = I_{\text{rms}}^2 \times X_L$


$$= 2^2 \times 4$$

$$= 16 \text{ VAR}$$

28. (b) The given circuit

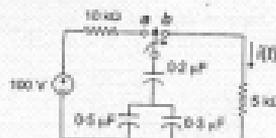

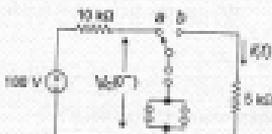For $t < 0$: i.e. when switch was on position a for a long time it mean all the capacitors are replaced by open circuit as shown below :



From above figure $V_C(0^-) = V_C(0^+) = 100\text{V}$ (since current is zero) for $t > 0$: i.e. when switch is moved to position (b).

Equivalent capacitance is given by

$$C_{\text{eq}} = (0.3+0.5) \parallel 0.2 \mu\text{F}$$

or $C_{\text{eq}} = \frac{0.8 \times 0.2}{0.8+0.2} \mu\text{F}$

or $C_{\text{eq}} = 0.16 \mu\text{F}$

The circuit for this is shown below :



Now, applying KVL in the above circuit, we get

$$V_C(t) + (t) 5000 = 0 \quad \left\{ \begin{array}{l} \therefore (t) = C \frac{dV_C(t)}{dt} \\ \text{or } (t) = 0.16 \times 10^{-6} \frac{dV_C(t)}{dt} \end{array} \right.$$

$$V_C(t) + 5000 - 0.16 \times 10^{-6} \frac{dV_C(t)}{dt} = 0$$

$$\frac{dV_C(t)}{dt} + \frac{1}{5000 \times 0.16 \times 10^{-6}} V_C(t) = 0$$

$$I.F. = e^{-1250t}$$

$$V_C(t) = Ae^{-1250t} \quad \dots (1)$$

Since at $t = 0$,

$$V_C(0^+) = 100$$

gives $100 = A$

$$V_C(t) = 100e^{-1250t}$$

$$i(t) = C \frac{dV_C(t)}{dt}$$


or $i(t) = -0.16 \times 10^{-6} \times 100 \times (1250)e^{-1250t}$

or $i(t) = 20e^{-1250t} \text{ mA}$

Hence alternative (b) is the correct choice.

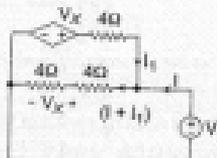29. (b) For maximize power to R_L , R_1 should be equal to R_{eq}

Calculation for R_{eq} . Equivalent circuit is shown below :



$$V = 8I + 8I_1 \quad \dots (1)$$

$$-V_X + 4I_1 + 8I + 8I_1 = 0 \quad \dots (2)$$

$$V_X = 4I + 4I_1 = \frac{V}{2}$$

$$-4I - 4I_1 + 4I_1 + 8I + 8I_1 = 0$$

$$4I + 8I_1 = 0$$

or $I_1 = -\frac{I}{2}$

Now, $V = 8I - \frac{8}{2}I = 4I$

Therefore,

$$R_{\text{eq}} = \frac{V}{I} = 4\Omega$$

30. (a) Given $\frac{dI}{dt} + \frac{R}{L}I = \frac{V_0}{L}(1 + B \sin \omega t)$

$$I.F. = e^{-\frac{R}{L}t}$$

$$I(t)e^{-\frac{R}{L}t} = \frac{V_0}{L} \int e^{-\frac{R}{L}t} (1 + B \sin \omega t) dt + C$$

$$= \frac{V_0}{L} \int e^{-\frac{R}{L}t} + B \sin \omega t dt + C$$

$$V_{GS} e^{R_1 t} = \frac{V_0}{R} \left[\frac{R_1}{L} e^{R_1 t} - B \cos t \right] + C$$

$$i(t) = \frac{V_0}{R} - \frac{V_0}{L} B e^{-R_1 t} \cos t + C e^{-R_1 t}$$

at $t = 0, i(0) = \frac{V_0}{R}$


Now, $\frac{V_0}{R} = \frac{V_0}{R} - \frac{V_0}{L} B + C$

which gives, $C = \frac{R_1 V_0}{L}$


Hence, $i(t) = \frac{V_0}{R} - \frac{V_0}{L} B e^{-R_1 t} \cos t + \frac{R_1 V_0}{L} e^{-R_1 t}$

For steady state value $i(t) = \frac{V_0}{R}$

31. (d) The given circuit

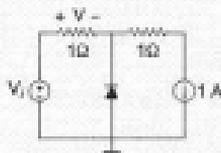


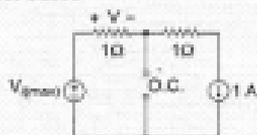The given diode is ideal. When V_1 is positive the diode gets reverse biased



Here, $V = 1V$

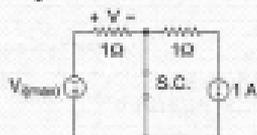
When V_1 is negative the diode becomes short circuited



Here, $V = -V_{1(max)}$

Hence alternative (d) is the correct choice.

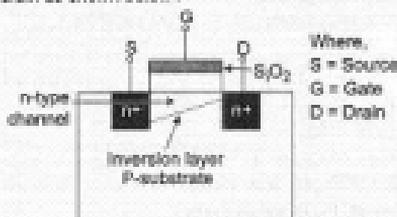32. (d) In an n-channel MOSFET operating in the active region. The inversion charge decreases from source to drain as shown below:




Where,
S = Source
G = Gate
D = Drain

When a voltage V_{DS} (i.e. voltage between drain and source) is applied between source and drain, with $V_{GS} = V_0$ (V_{GS} = voltage between gate and source and V_0 is the threshold voltage) the horizontal and vertical components of the electrical field due to the source-drain

voltage and gate-to-substrate voltage interact, causing conduction to occur along the channel. The horizontal component of electric field is associated with drain-to-source voltage (i.e. $V_{DS} > 0$) is responsible for sweeping the electron in the channel from the source towards drain. As the voltage from source to drain increases it means inversion charge decreases from source to drain. However the channel potential increases from source to drain.

Hence alternative (d) is the correct choice.

33. (a) The given circuit

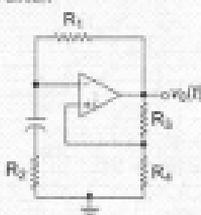


In an astable multivibrator, the value of peak voltage say, V_{max} is fixed i.e. not changed by changing the value of R_2 and C but time going $+V_{max}$ and $-V_{max}$ is changed. It means frequency changes. Hence alternative (a) is the correct choice.

34. (d) The given circuit

$$V_A = 5V$$

$$I_C = \frac{10 - 5}{5} = 1mA$$

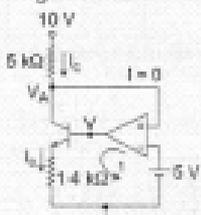


Applying KVL in loop 1, we get

$$V_0 = 0.8 + 1.4 \times 1$$

$$V_0 = 2V$$

and negative feedback.

35. (b) The given circuit

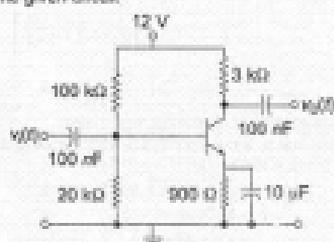


From given circuit, first off as we will draw thevenin equivalent circuit.

$$V_{th} = V_{CC} \times \frac{R_2}{R_1 + R_2}$$

$$\begin{aligned}
 &= 12 \times \frac{20}{20 + 100} = 2V \\
 R_{Th} &= \frac{20 \times 100}{20 + 100} \\
 &= \frac{100}{6} = \frac{50}{3} \text{ k}\Omega
 \end{aligned}$$

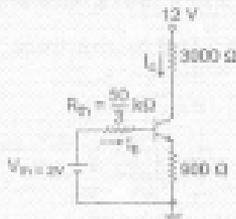The thevenin equivalent of the given circuit is shown below.




Hence, $V_0 = -150 \text{ I} \times 3\text{k}\Omega$ —(1)

and $I = \frac{V_1}{3\text{k}\Omega}$

$$\begin{aligned}
 V_0 &= -150 \times \frac{3\text{k}\Omega}{3\text{k}\Omega} = V_1 \\
 &= -150 V_1 \\
 &= -150 [A \cos 20t + B \sin 10^4 t]
 \end{aligned}$$

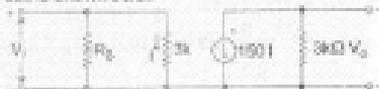Now the h-parameter model of the thevenin equivalent circuit is shown below



Hence alternative (b) is the correct choice.

36. (d) The given logic equation

$$\left[x + z \left\{ \bar{y} + (\bar{z} + \bar{x}) \right\} \right] \left\{ \bar{x} + \bar{z} (x + y) \right\} = 1$$

given if $x = 1$, then

$$\left[1 + z \left\{ \bar{y} + (\bar{z} + \bar{y}) \right\} \right] \left\{ \bar{1} + \bar{z} (1 + y) \right\} = 1$$

or $\left[1 + z \left\{ \bar{y} + \bar{z} \right\} \right] \left\{ 0 + \bar{z} \right\} = 1$

or $\left[\bar{z} + z \bar{y} \right] \left\{ \bar{z} \right\} = 1$

or $\left[\bar{z} + 0 \left\{ \bar{y} + \bar{z} \right\} \right] = 1$

or $\bar{z} = 1$

or $z = 0$

Hence alternative (d) is the correct choice.

37. (c) Let the inputs are A and B, and Y is the output.

● For 2-input AND gate, $Y = AB$



From above figure

$$Y = \bar{A}S + AB$$


or $Y = AB - \text{AND gate}$ (When $S = 0$)

Thus, we need one 2 x 1 Muximum to realize 2-input AND gate

● For 3-input EX-OR gate,

$$Y = A\bar{B} + B\bar{A}$$

or $Y = A \oplus B$

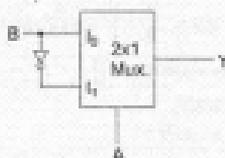


From above figure

$$Y = \bar{A}B + A\bar{B}$$

or $Y = A \oplus B$

Hence alternative (c) is the correct choice.

38. (c) The given figure :

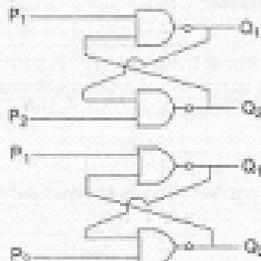

● For NAND gate latch

Initially P_1, P_2 inputs are 0, 1

$$Q_1 = \bar{P}_1 Q_2$$

and $Q_2 = \bar{P}_2 Q_1$

gives $Q_1 = 1$

and $Q_2 = 0$

After few seconds P_1, P_2 inputs becomes 1, 1

$$Q_1 = \bar{P}_1 Q_2$$

and $Q_2 = \bar{P}_2 Q_1$

gives $Q_1 = 1$

and $Q_2 = 0$

● For NOR gate latch

Initially P_1, P_2 inputs are 0, 1

$$Q_1 = \sqrt{P_1 + Q_2}$$

and $Q_2 = \sqrt{P_2 + Q_1}$

gives $Q_1 = 1$

and $Q_2 = 0$


After few seconds P_1, P_2 inputs becomes 1, 1

$$Q_1 = \sqrt{P_1 + Q_2}$$

and gives $Q_2 = \sqrt{P_2 + Q_1}$

and $Q_1 = 0$ (i.e. indeterminate condition)
and $Q_2 = 0$ (i.e. indeterminate condition)
Hence alternative (c) is the correct choice.

39. (a)

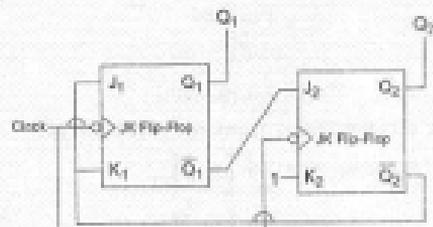

$$J_1 = \overline{Q_2} \quad K_1 = \overline{Q_2} \quad \text{FF-1}$$

$$J_2 = \overline{Q_1} \quad K_2 = 1 \quad \text{FF-2}$$

Seq. 11, 10, 00, 11, 10

Step I $Q_1 Q_2 = 11$

$$J_1 = T = 0 \quad K_1 = 0 \quad \text{No change}$$

$$K_2 = 1 \quad J_2 = T = 0 \quad \text{Reset}$$

$$Q_1 Q_2 = 10$$

Step II $J_1 = \overline{0} = 1$

$$K_1 = 1 \quad \text{Comp}$$

$$J_2 = 0 \quad K_2 = 1$$

Then $Q_1 Q_2 = 00$

Step III $J_1 = 1$

$$K_1 = 1$$

$$J_2 = 1 \quad K_2 = 1$$

$$Q_1 Q_2 = 11$$

Hence option (a) correct

For option (b)

$$Q_1 Q_2 = 01$$

$$J_1 = 0 \quad K_1 = 0$$

$$J_2 = 1 \quad K_2 = 1$$

Hence $Q_1 Q_2 = 00$

Then option (b) is not correct

For option (c)

$$Q_1 Q_2 = 00$$

Next $Q_1 Q_2 = 11$

Next $Q_1 Q_2 = 10$

But given 01 (c) is not correct

For option (d)

$$Q_1 Q_2 = 01$$

Next $Q_1 Q_2 = 10$


Next $Q_1 Q_2 = 00$

Next $Q_1 Q_2 = 11$

But given 10 (d) is not correct

40. (a)

41. (b) From given figure

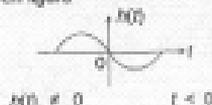

$$N(t) \neq 0 \quad t < 0$$

Hence system is non causal
For Bounded input

$$y(t) \leq \left| \int_{-\infty}^t x(t-\tau) h(2\tau) d\tau \right|$$

$$\text{or } y(t) \leq |x(t-\tau)| \int_{-\infty}^t |h(2\tau)| d\tau < \infty$$

Hence system is bounded output

42. (b)

43. (b)

$$G(s) = \frac{s^2 - 2s + 2}{s^2 + 2s + 2}$$



$$M(s) = \frac{K(s^2 - 2s + 2)}{s^2 + 2s + 2 + K(s^2 - 2s + 2)}$$

$$\text{or } M(s) = \frac{K(s^2 - 2s + 2)}{2s^2 + 4}$$

$$\text{for } 1 + G(s) = 0 \quad (s) = 0$$

$$1 + \frac{K(s^2 - 2s + 2)}{s^2 + 2s + 2} = 0$$

$$K = - \left[\frac{s^2 + 2s + 2}{s^2 - 2s + 2} \right]$$

for breakaway points

$$\frac{dK}{ds} = 0$$

$$= - \left[\frac{(s^2 - 2s + 2)(2s + 2) - (s^2 + 2s + 2)(2s - 2)}{(s^2 - 2s + 2)^2} \right]$$

$$= 0$$

$$2(s^2 - 2s + 2)(s + 1) - 2(s^2 + 2s + 2)(s - 1) = 0$$

$$s^3 - 2s^2 + 2s + s^2 - 2s + 2 - s^3 - 2s^2 - 2s + s^2 + 2s + 2 = 0$$

$$-2s^2 + 4 = 0$$

$$s = \pm \sqrt{2}$$

$$\text{Roots of pole: } s^2 + 2s + 2 = 0$$

$$s = \frac{-2 \pm \sqrt{4 - 8}}{2} = \frac{-2 \pm 2j}{2}$$

$$= -1 \pm j$$

$$\text{Roots of zero: } s^2 - 2s + 2 = 0$$

$$s = \frac{2 \pm \sqrt{4 - 8}}{2}$$

$$= 1 \pm j$$



$$\text{Angle of dep} = \angle \phi_1 + \angle \phi_2 + \angle \phi_3$$

$$= 90 - 45 + 0$$

$$= 45^\circ$$

44. (a)

$$H(s) = \frac{s^2 + 1}{s^2 + 2s + 1}$$

$$x(t) = \sin(t + 1)$$

$$\omega = 1$$

$$H(\omega) = \frac{-\omega^2 + 1}{-\omega^2 + 2\omega + 1}$$

at $\omega = 1$

$$H(\omega = 1) = \frac{-1+1}{-1+2+1} = 0$$

Hence $y(t)$ is zero for all value of ω .

45. (a) Steady State Value = -2

Input = Unit Step Response

for unit step $SSV = \lim_{s \rightarrow 0} F(s)$

and for under damped $\zeta < 1$

only $\frac{-3.82}{s^2 + 1.915 + 1.91}$

$$\begin{aligned} \omega_n &= \sqrt{1.91} \\ 2\zeta\omega_n &= 1.91 \\ \zeta &= \frac{1.91}{2\sqrt{1.91}} \\ &= \frac{\sqrt{1.91}}{2} < 1 \end{aligned}$$

and $SSV = \lim_{s \rightarrow 0} \frac{-3.82}{s^2 + 1.915 + 1.91} = \frac{-3.82}{1.91} = -2$

48. (b) (Also product of eigen values = det A.)

s^2	1	4	9	16	25
k	1	2	3	4	5
$P(X=k)$	0.1	0.2	0.4	0.2	0.1
PK	0.1	0.4	1.2	0.8	0.5

μ_k = Mean calculated by student = 3.5

σ_k^2 = Variance calculated by teacher = 1.6

Now, Mean $\mu = \sum_{k=1}^5 P_k k = 10.1 + 0.4 + 1.2 + 0.8 + 0.5 = 3$

Variance = $\sum_{k=1}^5 P_k k^2 - \mu^2$
 $\sigma^2 = (0.1 + 1.6 + 10.8 + 14.4 + 12.5) - (3)^2 = 39.4 - 9 = 30.4$

Both student and teacher are wrong.

So, option (b) is correct choice.

47. (c) $m(t) = \frac{1}{2} \cos \omega_1 t - \frac{1}{2} \sin \omega_2 t$

$\Rightarrow m_1 = \frac{1}{2}, m_2 = \frac{1}{2}$

$s(t) = [1 + m(t)] \cos \omega_c t$

We have $P_s = P_c \left[1 + \frac{m^2}{2} \right]$

$\eta = \left[\frac{P_s - P_c}{P_c} \right] \times 100$

$$m = \sqrt{m_1^2 + m_2^2} = \sqrt{\frac{1}{4} + \frac{1}{4}} = \frac{1}{\sqrt{2}}$$

$$P_s = P_c \left[1 + \frac{1}{2} \right] = P_c \left[\frac{3}{2} \right]$$

$$4P_s = 6P_c$$

$$\Rightarrow 4P_s - P_c = P_c \quad \dots (1)$$

$$\eta = \frac{P_{sM} \times 100}{SP_c} = \frac{4}{1}$$

or $\eta = \frac{1}{5} \times 100 = 20\%$

40. (b) Given SNR $\gg 1$, bandwidth = B, capacity C₁

We have, $C = B \ln \left[1 + \frac{S}{N} \right]$

$$C_1 = B \ln \left[1 + \frac{S}{N} \right]$$

$$C_2 = B \ln \frac{S}{N}$$

and if $\frac{S}{N}$ doubled

$$C_2 = B \ln \left[1 + 2 \frac{S}{N} \right]$$

$$C_2 = B \ln 2 \frac{S}{N}$$

$$C_2 = B \ln 2 + B \ln \frac{S}{N}$$

$$C_2 = B + C_1$$

49. (b) $\vec{B} = B_0 \left[\frac{x}{x^2 + y^2} \hat{i} - \frac{y}{x^2 + y^2} \hat{j} \right]$

We have, $H = \frac{B}{\mu}$


$$\nabla \times H = J$$

$$\nabla \times H = \begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ -\frac{B_0}{\mu} \frac{y}{x^2 + y^2} & \frac{B_0}{\mu} \frac{x}{x^2 + y^2} & 0 \end{vmatrix}$$

$$\nabla \times H = \hat{i} \left[\frac{\partial}{\partial y} \frac{B_0}{\mu} \frac{x}{x^2 + y^2} - \frac{\partial}{\partial x} \left(-\frac{B_0}{\mu} \frac{y}{x^2 + y^2} \right) \right] + \hat{j} \left[0 - \frac{\partial}{\partial x} \left(-\frac{B_0}{\mu} \frac{x}{x^2 + y^2} \right) - \frac{\partial}{\partial y} \left(\frac{B_0}{\mu} \frac{y}{x^2 + y^2} \right) \right]$$

$$\nabla \times H = -\frac{B_0}{\mu} \cdot \frac{2}{(x^2 + y^2)} \hat{k} \neq 0$$

50. (d)

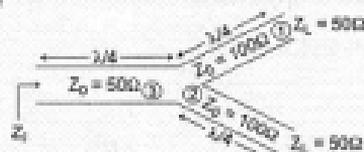

We have $Z_1 = Z_0 \left[\frac{Z_L + Z_0 \tan \beta_L}{Z_0 + Z_L \tan \beta_L} \right]$

Branch (1)

$$\beta_L = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}$$

$$= \frac{\pi}{2}$$

$$Z_1 = Z_0 \left[\frac{Z_L + Z_0 j \tan \frac{\pi}{2}}{Z_0 + Z_L j \tan \frac{\pi}{2}} \right]$$

$$Z_1 = \frac{Z_0 - Z_0}{Z_L}$$

$$= \frac{100 - 100}{50} = 200$$

Branch (2) $Z_1 = 200$

Then for Branch (3)

$$Z_1 = \frac{50 \times 50}{100}$$

$$= 25 \Omega \cdot \frac{200 \times 200}{400} = 100 \Omega$$

Overall, $Z_1 = \frac{Z_0 Z_0}{Z_L} = \frac{50 \times 50}{100} = 25 \Omega$

51. (b)

$$n = 1 \times 10^{17}$$

$$x_p = 0.1 \mu\text{m}$$

$$x_p = 1.0 \mu\text{m}$$

$$n_p = 1.4 \times 10^{19} \text{ cm}^{-3}$$

$$V_T = 26 \text{ mV}$$

$$i_p = 12$$

$$n_0 = 8.85 \times 10^{-14} \text{ F} \cdot (\text{m}^{-1})$$

$$V_0 = \frac{kT}{q} \ln \left[\frac{N_p N_D}{n_i^2} \right]$$

$$\frac{kT}{q} = V_T$$

We know that

$$x_p N_D = x_n N_p$$

$$N_p = \frac{x_n}{x_p} N_D$$

$$= \frac{0.1}{1.0} \times 10^{17} = 10^{16}$$

$$V_0 = 26 \times 10^{-3} \ln \left[\frac{10^{16} \times 10^{17}}{(1.4 \times 10^{10})^2} \right]$$

$$= 0.76 \text{ Volt}$$

52. (b)

$$E = -\frac{q}{\epsilon} = -\frac{q}{\epsilon_0 \epsilon_r}$$


$$= -\frac{1.6 \times 10^{-19}}{8.85 \times 10^{-14} \times 12} \times 1 \times 10^{17} \times 0.1$$

$$\times 10^{-6} \times 100$$

$$= 0.15 \text{ MV cm}^{-1}$$

53. (c)

54. (c)

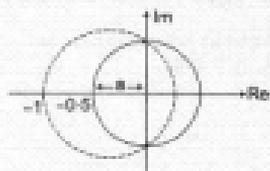

Given $a = 0.5$

$$\text{GM} = 20 \log \frac{1}{a}$$

$$= 20 \log_{10} \frac{1}{0.5}$$

$$= 6 \text{ dB}$$

For PM = $180 - \angle \phi$

$\angle \phi = 90$ from figure

Hence PM = $180 - 90 = 90^\circ$

55. (c) $\left(\frac{S}{N} \right)_{\text{dB}} = 43.5 \text{ dB}$

$$\left(\frac{S}{N} \right)_{\text{dB}} = 1.8 + 6n = 43.5$$

$$n = 7$$

$$\Delta = \frac{2m\gamma}{L} = \frac{2 \times 5}{2^7} = 0.07$$

$m_p = 5$

Option (c) is correct

56. (b)

$\Delta_1 = 0.05 \text{ V}$ for positive value

$\Delta_0 = 0.1 \text{ V}$ for negative value

$$L_1 = \frac{2m\gamma_1}{\Delta_1} = \frac{5}{0.05} = 100$$

$$L_2 = \frac{2m\gamma_2}{\Delta_2} = \frac{3}{0.1} = 30$$


$$L = L_1 + L_2 = 130 = 2^n$$

$$(\text{SNR})_{\text{dB}} = 1.72 + 6.02 n$$

$$= 1.72 + 6.02 \times 7$$

$$= 43.86 \text{ dB}$$

57. (c) The given circuit

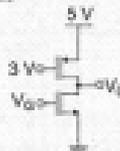

In n -MOS circuit p -MOS is connected to supply voltage while n -MOS is connected to ground voltage.

given $V_T = 1 \text{ V}$ for both type MOSFET

For n -MOS

Given $V_{Tn} = 1 \text{ V}$

and V_G is small increase in 1 volt

Hence $V_{GS} - V_T = 0$


or slightly greater than zero. Then n -MOS is in triode region.

For p -MOS $V_{GS} = 3 - 5 = -2 \text{ volt}$

which is more negative to V_{TP} . Hence it is in saturation region.

Hence alternative (c) is the correct choice.

58. (d) Given $V_{DS} = 1.5$ volt

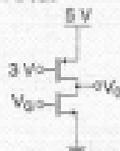

From transistor (1)

$$V_{DS} = 1V$$

$$V_{GS} - V_{TS} = 1.5 - 1 = 0.5V$$

Hence the transistor (1) is in saturation.

$$\text{Then, } I_D = \mu C_{ox} \frac{W}{L} \left[(V_{GS} - V_{TS}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$\mu C_{ox} \frac{W}{L} = 1 \text{ mA}$$

$$I_D = \frac{1}{2} (1.5 - 1)^2 = \frac{1}{8} \text{ mA}$$

and from transistor (2)

$$I_D = \mu C_{ox} \frac{W}{L} \left[(V_{GS} - V_{TP}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$\frac{1}{8} = \frac{1}{2} \left[(2 - 1) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$\text{or } \frac{1}{8} = V_{DS}^2 - 4V_{DS} + 1$$

$$\text{Hence } V_{DS} = 1 - \frac{\sqrt{3}}{2}$$

$$V_O = 5 - V_{DS}$$

$$\text{or } V_O = 5 - 1 + \frac{\sqrt{3}}{2} = 4 + \frac{\sqrt{3}}{2}$$

59. (b) The given 7 segment display




Here the inputs are P_1 and P_2 and outputs are a, b, c, d, e, f, g. In order to solve this problem we have to calculate g in terms of P_1 and P_2 .

Inputs		outputs						
P_1	P_2	a	b	c	d	e	f	g
0	0	1	1	1	1	1	1	0
0	1	1	0	1	1	0	1	1
1	0	1	0	1	1	0	1	1
1	1	1	0	0	1	1	1	1

● K-map for g




● K-map for b

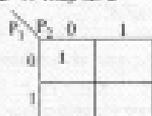

$$g = P_1 + P_2$$

● K-map for d

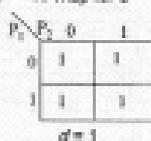

$$d = 1$$


$$b = \overline{P_1} \overline{P_2}$$

● K-map for c



$$c = \overline{P_1} \overline{P_2}$$

● K-map for e

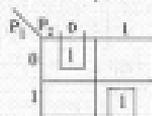

$$e = \overline{P_1} \overline{P_2} + \overline{P_1} P_2$$

Since

$$g = P_1 + P_2$$

so either alternative (b) or (d) will be correct

Now, $c + e = \overline{P_1} \overline{P_2} + \overline{P_1} P_2 + P_1 P_2$

$$= \overline{P_1} \overline{P_2} + \overline{P_1} P_2 (1 + P_1)$$

$$= \overline{P_1} \overline{P_2} + \overline{P_1} P_2 \quad (\text{since } 1 + \overline{P_1} = 1)$$

$$= \overline{P_1} \overline{P_2} + P_1 P_2$$

$$(\text{since } A + \overline{A}B = A + B \text{ so, } \overline{P_1} \overline{P_2} + P_1 P_2 = \overline{P_1} + \overline{P_2})$$


$$= \overline{P_1} + \overline{P_2}$$

$$= 1 + \overline{P_2} \quad (\text{since } \overline{P_1} + \overline{P_2} = 1)$$

$$= 1 = d \quad (\text{since } 1 + \overline{P_2} = 1)$$

Therefore, alternative (b) is the correct choice.

60. (a)

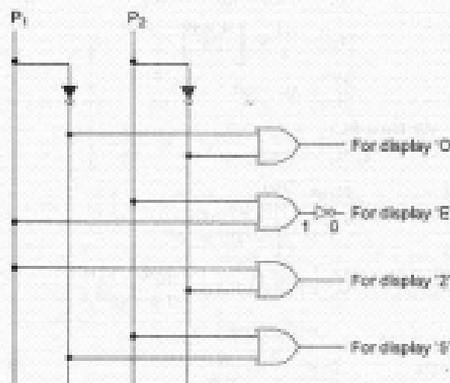

Thus minimum number of 3-NOT gates and 4-OR gates are required to design the logic of the driver.

Hence alternative (a) is the correct choice.