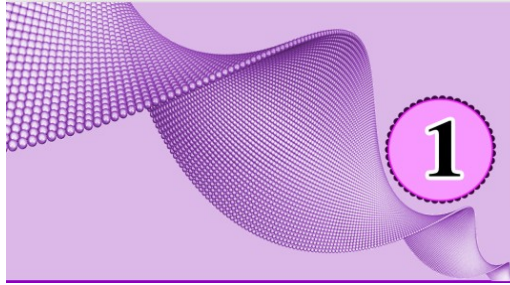



# PHYSICS - X- PART-2




## 1

## Effects of Electric Current

### Arrangement of Resistors in Circuits

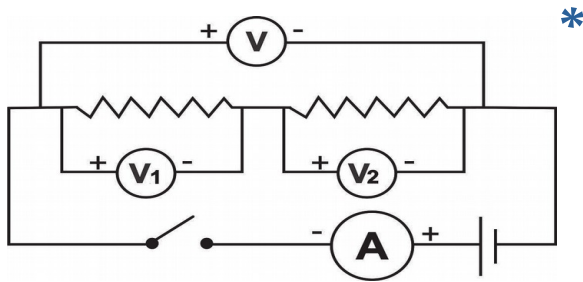


\*

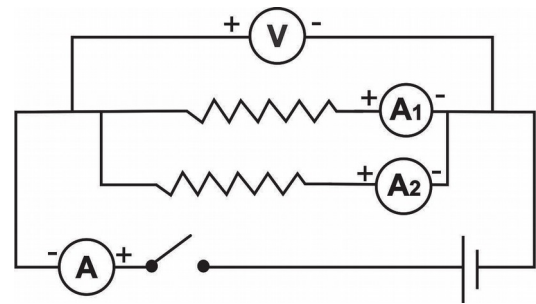
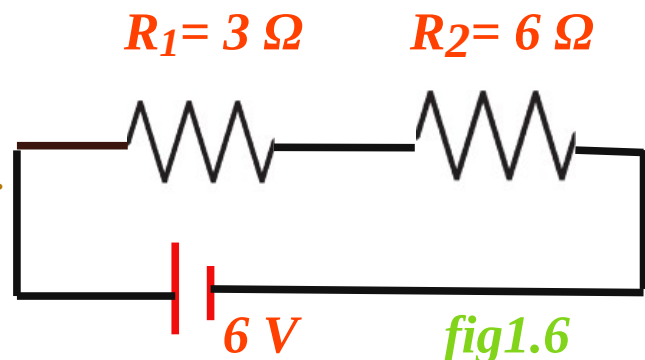
### 1. Series Connection

When a circuit is completed by connecting the resistors one after the other, it is called series connection.



**Effective resistance,  $R = R_1 + R_2$**

Effective resistance is the sum of the resistance of all the resistors when they are connected in series.

Ex. 1 ( Fig.1.6 )

$$R_1 = 3 \Omega$$

$$R_2 = 6 \Omega$$

Effective resistance,  $R = R_1 + R_2$

$$R = 3 \Omega + 6 \Omega$$

$$R = 9 \Omega$$


**When resistors are connected in series,**

- \* The potential difference gets divided
- \* The current through each resistor will be the same.
- \* The effective resistance increases.

## 2. Parallel Connection


Effective resistance,  $1/R = 1/R_1 + 1/R_2$

$$R = \frac{R_1 \times R_2}{R_1 + R_2}$$

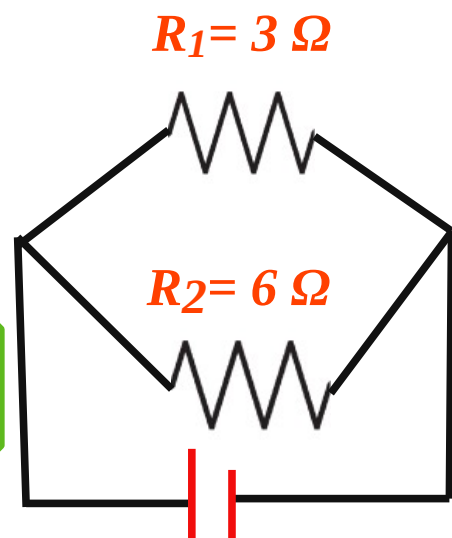

6 V

fig1.7

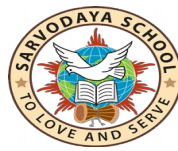

**Ex. 2 ( Fig.1.7 )**

$$R_1 = 3 \Omega$$

$$R_2 = 6 \Omega$$

Effective resistance,

$$R = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R = \frac{3 \Omega \times 6 \Omega}{3 \Omega + 6 \Omega}$$

$$R = \underline{2 \Omega}$$

**When resistors are connected in Parallel,**

- \* The potential difference in each resistors are same.
- \* Current through each resistors are different.
- \* The effective resistance decreases.

If resistors of the same value are connected in parallel, then  $R = \frac{r}{n}$ , where n is the number of resistors and r is the resistance of one resistor.

**Complete the following table**

Resistors in series	Resistors in parallel
<ul style="list-style-type: none"> <li>• Effective resistance increases</li> </ul>	<ul style="list-style-type: none"> <li>•</li> </ul>
<ul style="list-style-type: none"> <li>•</li> </ul>	<ul style="list-style-type: none"> <li>• The current through each resistor is different. It gets divided as per the value of resistors.</li> </ul>
<ul style="list-style-type: none"> <li>• The potential difference across each resistor is different. It gets divided as per the value of resistors.</li> </ul>	<ul style="list-style-type: none"> <li>•</li> </ul>
<ul style="list-style-type: none"> <li>•</li> </ul>	<ul style="list-style-type: none"> <li>• Each resistor can be controlled by using separate switches.</li> </ul>

## Heating Effect of Electricity- Uses


- Name the part in which electrical energy changes into heat energy.
  - **Heating coils**
- Which material is used to make this part?
  - **Nichrome** (Nichrome is an alloy of nickel, chromium and iron)
- What are the peculiarities of such substances?
  - **High resistivity**
  - **Ability to remain in red hot condition for a long time without getting oxidised**
  - **High melting point**
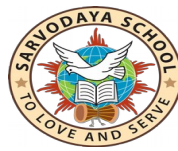
## Safety fuse



Safety fuse is a device that works on the heating effect of electric current.

- \* Which material is used to make fuse wire?
  - Fuse wire, an alloy of tin and lead,
- \* What are the peculiarities of fuse wire?
  - **low melting point.**



**\* Which are the circumstances that cause high electric current, leading to the melting of fuse wire?**

**-Short Circuit and Overloading**

**\* How is the fuse wire connected to a circuit?**

**- In series.**

### Short Circuit

*If the positive and the negative terminals of a battery or the two wires from the mains come into contact without the presence of a resistance in between, they are said to be short-circuited.*

### Overloading


*A circuit is said to be overloaded if the total power of all the appliances connected to it is more than what the circuit can withstand.*

### Amperage

*Amperage (A) is the ratio of the power of an equipment to the voltage applied. Amperage increases with the thickness of the conductor.*

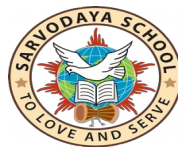**\* When a fuse wire is included in a household wiring, what are the precautions to be taken?**

- *The ends of the fuse wire must be connected firmly at appropriate points.*
- *The fuse wire should not project out of the carrier base.*
-



### WORKSHEET - 1

• You know that according to Joule's Law, more heat will be produced when electric current is increased. What happens to the fuse wire due to this?

-----

• When heat is generated, why does the fuse wire melt?

-----

• When the fuse wire melts, the circuit is broken. What happens to the current in the circuit?

-----

• Why is the fuse used in a circuit called safety fuse? Explain.

-----

### Electric power

\* The amount of energy consumed by an electrical appliance in unit time is its power.

\* The unit of power is watt (W)


$$\text{Power, } P = \frac{\text{Work}}{\text{time}} = \frac{H}{t}$$

$$P = VI$$

$$P = I^2 R$$

$$P = V^2 / R$$

$$\text{Amperage} = \frac{\text{Wattage}}{\text{Voltage}} = \frac{W}{V}$$

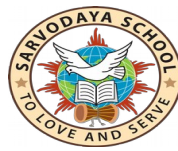**WORKSHEET - 2**

**1, An appliance of power 540 W is used in a branch circuit. If the voltage is 230 V, what is its amperage?**

**2, A heating appliance has a resistance of 115  $\Omega$ . If 2 A current flows through it, what is the power of the appliance?**

**3, 22 A current of 0.4 A flows through an electric bulb working at 230 V. What is the power of the bulb?**

**4, An electric heater conducts 4 A current when 60 V is applied across its terminals. What will be the current if the potential difference is 120 V?**

**5, Three resistors of 2  $\Omega$  , 3  $\Omega$  and 6  $\Omega$  are given in the class.**

**(a) What is the highest resistance that you can get using all of them?**

**(b) What is the least resistance that you can get using all of them?**

**(c) Can you make a resistance 4.5  $\Omega$  using these three? Draw the circuit.**

**6, What is the current if 12  $\Omega$  and 4  $\Omega$  resistors are connected in parallel and 12 V potential difference is applied?**

**7, 10 resistors of 2  $\Omega$  each are connected in parallel. Calculate the effective resistance.**