# KITE VICTERS ONLINE CLASS 04-06-2021 PHYSICS - X-PART-2 CLASS 02 Image: Constraint of the second se

# Ohm's Law

\* When temperature remains constant, the current through a conductor is directly proportional to the potential difference between its ends.

\* In other words the ratio of potential difference to the current is a constant. V / I = a constant

\* This constant is the resistance of the conductor. This is indicated by the letter R.



\* Resistors are conductors used to include a particular resistance in a circuit. Its symbol is \_\_\_\_\_\_

```
Unit of resistance = Unit of voltage / Unit of current
= volt / ampere
* volt/ampere is ohm. The symbol of this is Ω (Greek letter omega).
```

### **Rheostat**

\* Rheostat is a device used to regulate the current in a circuit by changing the resistance gradually.

\* The symbol of a rheostat is





## Resistance

\* Resistance is a measure of the opposition to current flow in an electrical circuit.

\*Write down the factors affecting the resistance of a conductor

- Area of cross section (thickness)
- Nature of the material
- · Length of the conductor
- Temperature of the conductor

### <u>Assignment</u>

\* Make a simple circuit with two 1.5V cells, a 3V bulb and a switch.

a) Illuminate the bulb with a cell, and observe the light intensity of the bulb.

b) Connect the cells in series and illuminate the bulb, and observe the light intensity of the bulb.