

KENDRIYA VIDYALAYA BHU IST SHIFT


CLASS-XII. SUB- PHYSICS
MONTHLY TEST(SEPTEMBER)

Total Marks : 40


* Choose The Right Answer From The Given Options.[1 Marks Each]

[7]

- The value of mutual inductance can be increased by.
(A) decreasing N
(B) increasing N
(C) winding the coil on wooden frame
(D) winding the coil on china clay
- Which of the following are not units of self inductance?
(A) Weber/m²
(B) Ohm-second
(C) Joule-ampere
(D) Joule-ampere-2
- The number of turns in an air core solenoid of length 25cm and radius 4cm is 100. Its self inductance will be.
(A) $5 \times 10^{-4}H$ (B) $2.5 \times 10^{-4}H$ (C) $5.4 \times 10^{-3}H$ (D) $2.5 \times 10^{-3}H$
- Two circular coils can be arranged in any of the three situations shown in the figure. Their mutual inductance will be.

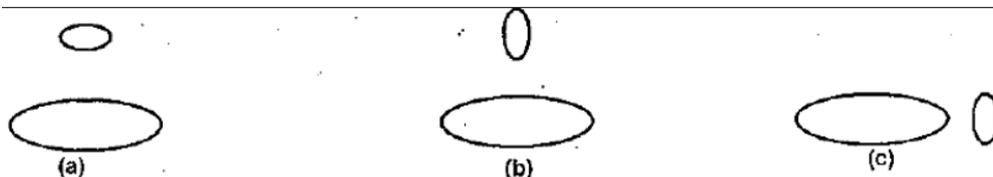

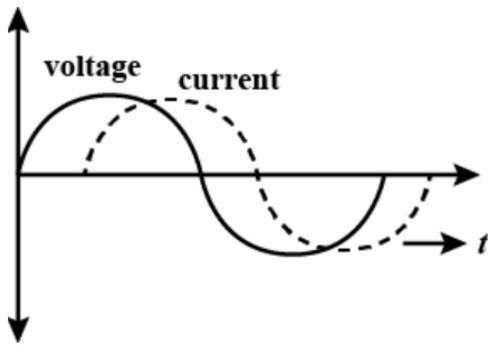- maximum in situation (A)
 - maximum in situation (B)
 - maximum in situation (C)
 - the same in all situations
- The AC produced in India changes its direction in every:
(A) $\frac{1}{100}$ second (B) 100 second (C) 50 second (D) None of these
 - The diagram given show the variation of voltage and current in an AC circuit. The circuit contains.



(A) Only a resistor

(B) Only a pure inductor

(C) Only a capacitor

(D) A capacitor and an inductor

7. When the frequency of AC is doubled, the impedance of an LCR series circuit:

(A) is halved

(B) is doubled

(C) increases

(D) decreases

* a statement of Assertion (A) is followed by a statement of Reason (R). [1]

Choose the correct option.

8. For two statements are given-one labelled Assertion (A) and the other labelled Reason (R). Select the correct answer to these questions from the codes (a), (b), (c) and (d) as given below.

a. Both A and R are true and R is the correct explanation of A.

b. Both A and R are true but R is not the correct explanation of A.

c. A is true but R is false.

d. A is false and R is also false.


Assertion: A bulb connected in series with a solenoid is connected to A.C. source. If a soft iron core is introduced in the solenoid, the bulb will glow brighter.

Reason: On introducing soft iron core in the solenoid, the inductance decreases.


* Given Section consists of questions of 2 marks each. [10]

9. Use Lenz's law to determine the direction of induced current in the situations described by Fig.

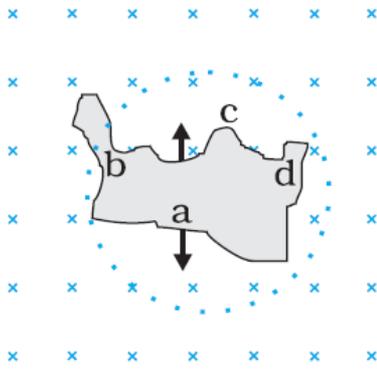a. A wire of irregular shape turning into a circular shape;



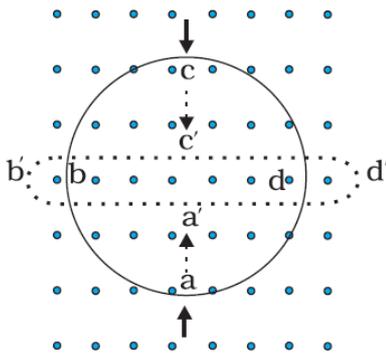b. A circular loop being deformed into a narrow straight wire.



10. Current in a circuit falls from 5.0A to 0.0A in 0.1s. If an average emf of 200V induced, give an estimate of the self-inductance of the circuit.
11. A $15.0\mu F$ capacitor is connected to a 220V, 50Hz source. Find the capacitive reactance and the current (rms and peak) in the circuit. If the frequency is doubled, what happens to the capacitive reactance and the current?
12. A lamp is connected in series with a capacitor. Predict your observations for dc and ac connections. What happens in each case if the capacitance of the capacitor is reduced?
13. A 100Ω resistor is connected to a 220V, 50Hz ac supply.
 - a. What is the rms value of current in the circuit?
 - b. What is the net power consumed over a full cycle?

*** Given Section consists of questions of 3 marks each.**

[12]

14.
 - a. Define mutual inductance.
 - b. A pair of adjacent coils has a mutual inductance of 1.5 H. If the current in one coil changes from 0 to 20 A in 0.5 s, what is the change of flux linkage with the other coil?
15.
 - i. Define self-inductance. Write its SI units.
 - ii. A long solenoid with 15 turns per cm has a small loop of area 2.0 cm^2 placed inside the solenoid normal to its axis. If the current carried by the

solenoid changes steadily from 2.0 A to 4.0 A in 0.1 s, what is the induced emf in the loop while the current is changing?

16. Two concentric circular coils, one of small radius r_1 and the other of large radius r_2 , such that $r_1 \ll r_2$, are placed co-axially with centres coinciding. Obtain the mutual inductance of the arrangement.

17. A resistance R and a capacitor C are connected in series to a source $V = V_0 \sin \omega t$.


Find:

- The peak value of the voltage across the (i) resistance and (ii) capacitor.
- The phase difference between the applied voltage and current. Which of them is ahead?

*** Given Section consists of questions of 5 marks each.**

[10]

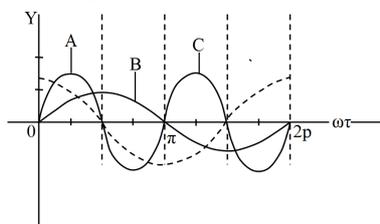18. A device 'X' is connected to an ac source $V = V_0 \sin \omega t$. The variation of voltage, current and power in one cycle is show in the following graph:



- Identify the device 'X'.
- Which of the curves, A, B and C represent the voltage, current and the power consumed in the circuit? Justify your answer.
- How does its impedance vary with frequency of the ac source? Show graphically.
- Obtain an expression for the current in the circuit and its phase relation with ac voltage.

19. A series LCR circuit with $L = 0.12\text{H}$, $C = 480\text{nF}$, $R = 23\Omega$ is connected to a 230V variable frequency supply.

- What is the source frequency for which current amplitude is maximum. Obtain this maximum value.
- What is the source frequency for which average power absorbed by the circuit is maximum. Obtain the value of this maximum power.
- For which frequencies of the source is the power transferred to the circuit half the power at resonant frequency? What is the current amplitude at these frequencies?
- What is the Q-factor of the given circuit?
